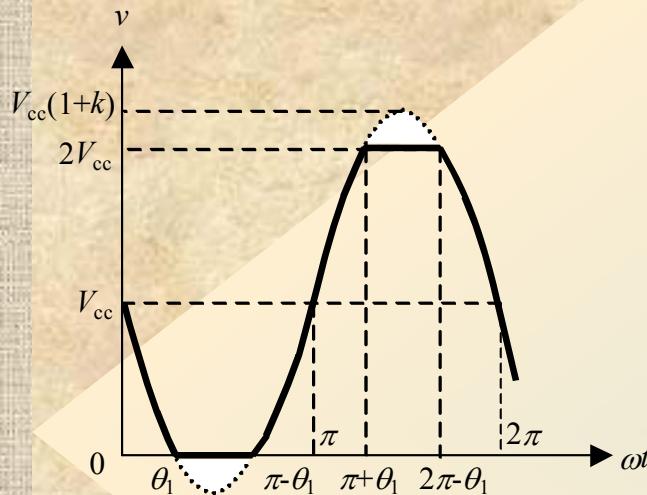


## **LECTURE 4. HIGH-EFFICIENCY POWER AMPLIFIER DESIGN**

- 4.1. Overdriven Class B**
- 4.2. Class F circuit design**
- 4.3. Inverse Class F**
- 4.4. Class E with shunt capacitance**
- 4.5. Class E with parallel circuit**
- 4.6. Class E with transmission lines**
- 4.7. Broadband Class E circuit design**
- 4.8. Practical high efficiency RF and microwave power amplifiers**

## 4.1. Overdriven Class B

**In overdriven Class B, voltage and current waveforms have increased amplitudes with the same peak values as in conventional Class B**



**for DC voltage:**

$$V_0 = V_{cc}$$

**for fundamental voltage :**

$$V_1 = \frac{2V_{cc}}{\pi} \left( \frac{\theta_1}{\sin \theta_1} + \cos \theta_1 \right)$$

**for odd voltage components,  $n = 3, 5, \dots$  :**

$$V_n = \frac{2V_{cc}}{\pi} \left[ \frac{\sin(\theta_1 - n\theta_1)}{(1-n)\sin \theta_1} - \frac{\sin(\theta_1 + n\theta_1)}{(1+n)\sin \theta_1} + \frac{2\cos n\theta_1}{n} \right]$$


**for even voltage components,  $n = 2, 4, \dots$  :**  $V_n = 0$

**for DC current:**  $I_0 = \frac{I_s}{\pi} \left( \frac{\pi}{2} - \theta_1 + \tan \frac{\theta_1}{2} \right)$

**for fundamental current:**  $I_1 = \frac{I_s}{\pi} \left( \frac{\theta_1}{\sin \theta_1} + \cos \theta_1 \right)$

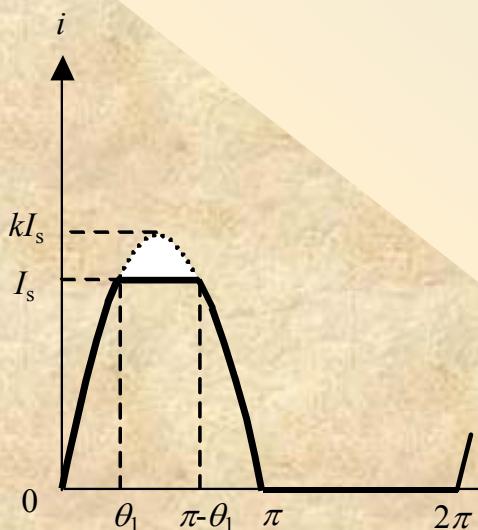**for odd current components,  $n = 3, 5, \dots$  :**

$$I_n = \frac{I_s}{\pi} \left[ \frac{\sin(\theta_1 - n\theta_1)}{(1-n)\sin \theta_1} - \frac{\sin(\theta_1 + n\theta_1)}{(1+n)\sin \theta_1} + \frac{2\cos n\theta_1}{n} \right]$$



## 4.1. Overdriven Class B

$$P_1 = \frac{V_1 I_1}{2} = \frac{V_{cc} I_s}{\pi^2} \left( \frac{\theta_1}{\sin \theta_1} + \cos \theta_1 \right)^2$$

- fundamental output power

$$P_0 = V_0 I_0 = \frac{V_{cc} I_s}{\pi} \left( \frac{\pi}{2} - \theta_1 + \tan \frac{\theta_1}{2} \right)$$

- DC output power

**Out-of-band impedances :**

$$Z_n = \frac{2V_{cc}}{I_s} = R_L, \quad \text{for odd } n$$

$$Z_n = 0, \quad \text{for even } n$$

**where  $R_L$  is load resistance**

**Collector efficiency**  
:



$$\eta = \frac{P_1}{P_0} = \frac{1}{\pi} \frac{\left( \frac{\theta_1}{\sin \theta_1} + \cos \theta_1 \right)^2}{\frac{\pi}{2} - \theta_1 + \tan \frac{\theta_1}{2}}$$

**For**  $\lim_{\theta_1 \rightarrow 0} \frac{\theta_1}{\sin \theta_1} = \lim_{\theta_1 \rightarrow 0} \frac{\theta_1'}{\sin' \theta_1} = \lim_{\theta_1 \rightarrow 0} \frac{1}{\cos \theta_1} = 1 \quad \rightarrow \quad \eta = \frac{8}{\pi^2} = 81\%$

- maximum collector efficiency for square voltage and current waveforms

Analyzing  $\eta$  on extremum gives  $\eta = 88.6\%$  for optimum angle  $\theta_1 = 32.4^\circ$

## 4.2. Class F circuit design

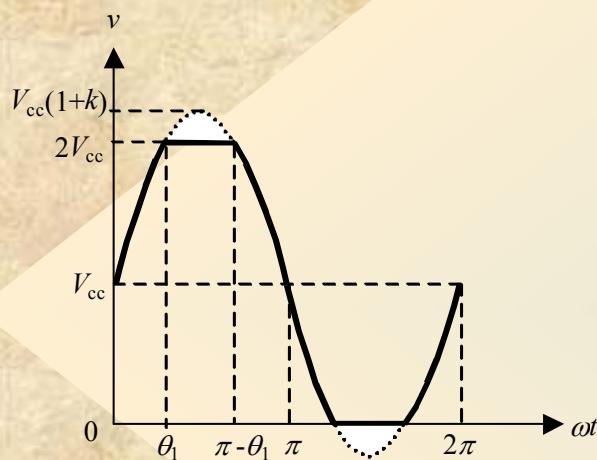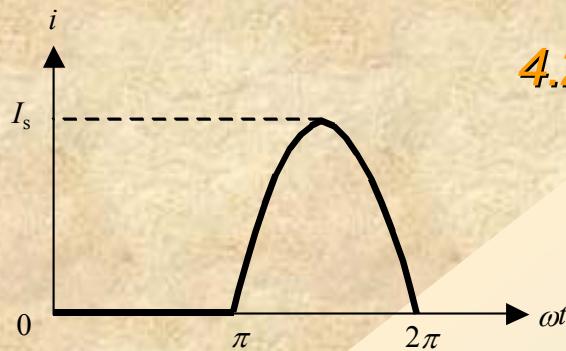

$$I_1 = \frac{I_s}{2} \quad - \text{fundamental current component}$$



$$V_1 = \frac{4V_{cc}}{\pi} \quad - \text{fundamental voltage component when } \theta_1 \rightarrow 0$$

$$P_1 = \frac{V_{cc} I_s}{\pi} \quad - \text{fundamental output power}$$

$$P_0 = \frac{V_{cc} I_s}{\pi} \quad - \text{DC output power}$$

$$\eta = \frac{P_1}{P_0} = 100\% \quad - \text{collector efficiency}$$


**Ideal voltage and current waveforms:**

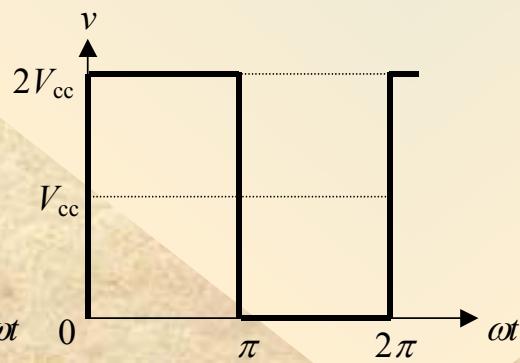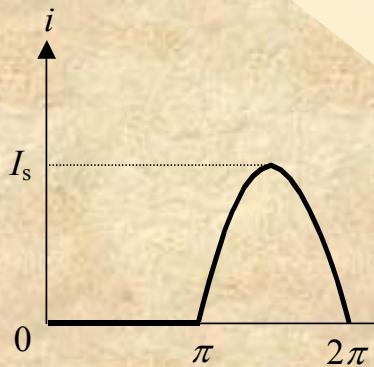

**Harmonic impedance conditions:**

$$\left\{ \begin{array}{l} Z_1 = R_L = \frac{8}{\pi} \frac{V_{cc}}{I_s} \\ Z_n = 0 \quad \text{for even } n \\ Z_n = \infty \quad \text{for odd } n \end{array} \right.$$
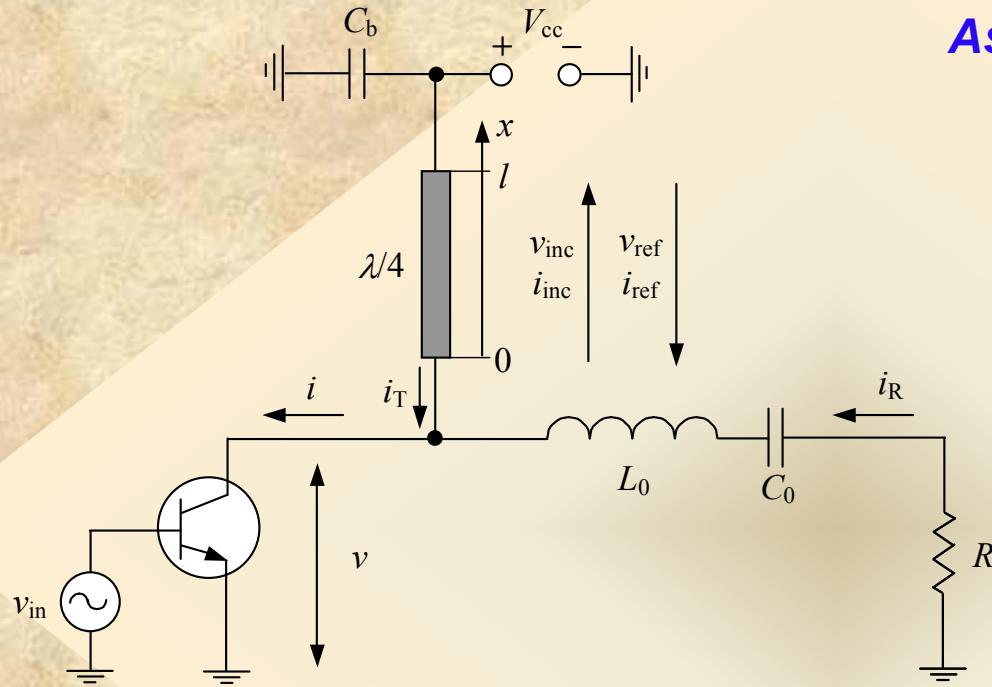
## 4.2. Class F circuit design: quarterwave transmission line



**Assumptions for transistor:**

- **ideal switch:**  
**no parasitic elements**
- **half period is on,**  
**half period is off:**  
**50% duty cycle**

**Assumptions for load:**

- **purely sinusoidal current:**  
**ideal  $L_0C_0$ -circuit tuned at fundamental**


$$i(\omega t) = I_R \sin \omega t \quad - \text{load current}$$

$$v(\omega t) = 2V_{cc} - v(\omega t + \pi) \quad - \text{collector voltage}$$


$$i_T(\omega t) = i_T(\omega t + \pi) = I_R |\sin \omega t| \quad - \text{transmission-line current}$$

$$i(\omega t) = I_R(\sin \omega t + |\sin \omega t|) \quad - \text{collector current}$$
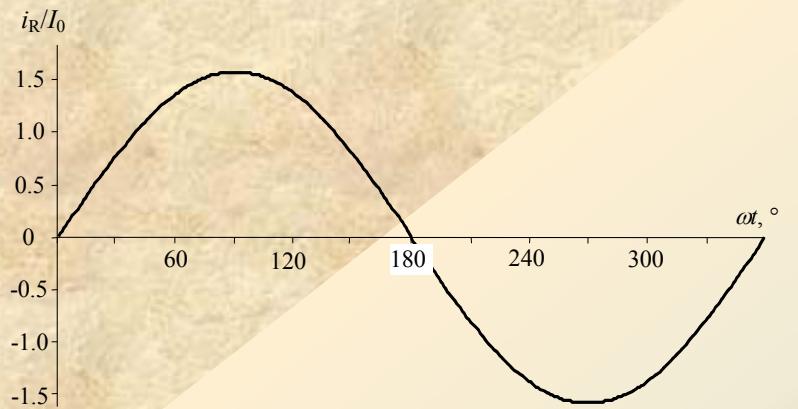
## 4.2. Class F circuit design: quarterwave transmission line




*sinusoidal load current*

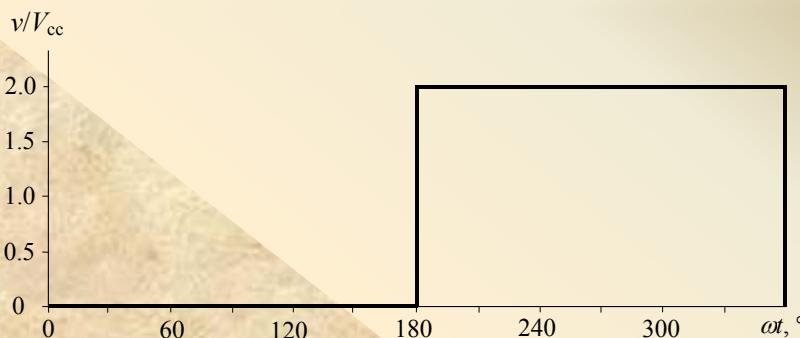


*rectangular collector voltage*

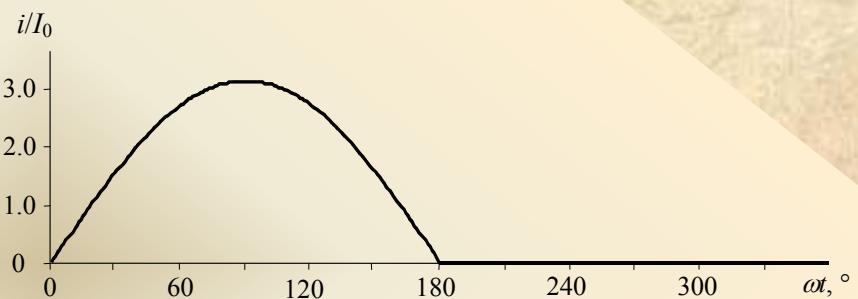*collector current consisting of fundamental and even harmonics*



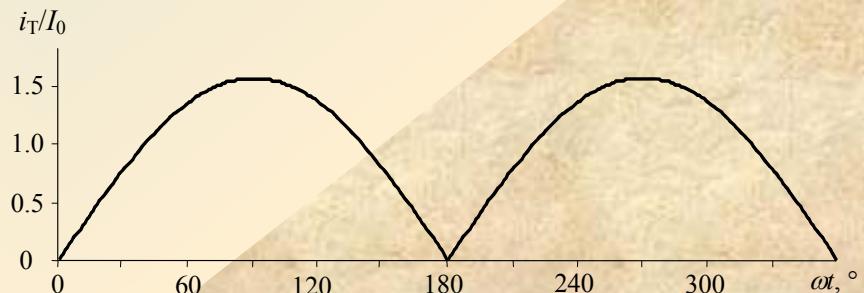*transmission-line current consisting of even harmonics*



## 4.2. Class F circuit design



**For maximally flat waveforms:**

**optimum values:**



$$V_1 = \frac{9}{8} V_{cc}$$

$$V_3 = \frac{1}{8} V_{cc}$$

**collector voltage**

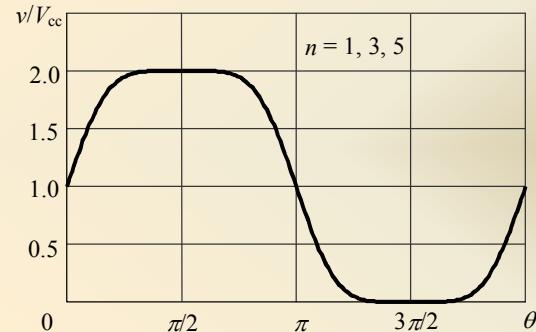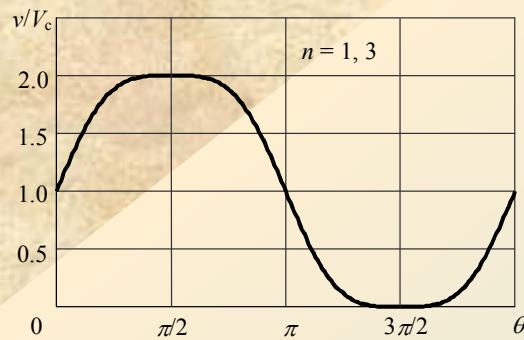

**collector current**

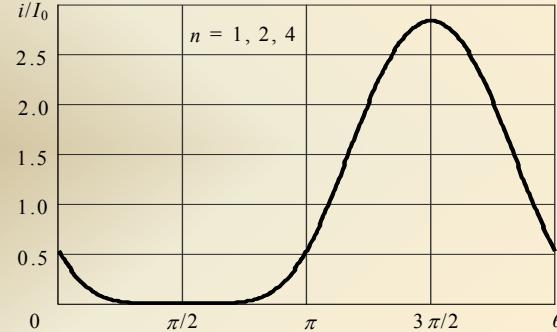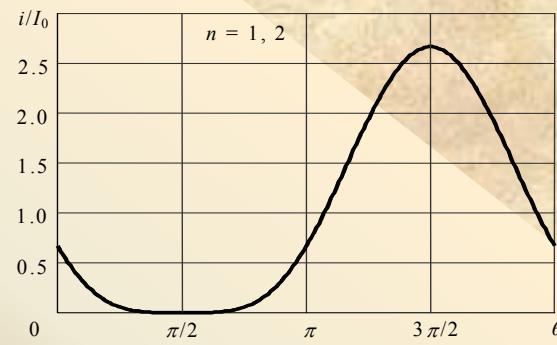


**optimum values:**

$$I_1 = \frac{4}{3} I_0$$

$$I_2 = \frac{1}{3} I_0$$

Current harmonic components	Voltage harmonic components				
	1	1, 3	1, 3, 5	1, 3, 5, 7	1, 3, 5, ..., $\infty$
1	$1/2 = 0.500$	$9/16 = 0.563$	$75/128 = 0.586$	$1225/2048 = 0.598$	$2/\pi = 0.637$
1, 2	$2/3 = 0.667$	$3/4 = 0.750$	$25/32 = 0.781$	$1225/1536 = 0.798$	$8/3\pi = 0.849$
1, 2, 4	$32/45 = 0.711$	$4/5 = 0.800$	$5/6 = 0.833$	$245/288 = 0.851$	$128/45\pi = 0.905$
1, 2, 4, 6	$128/175 = 0.731$	$144/175 = 0.823$	$6/7 = 0.857$	$7/8 = 0.875$	$512/175\pi = 0.931$
1, 2, 4, ..., $\infty$	$\pi/4 = 0.785$	$9\pi/32 = 0.884$	$75\pi/256 = 0.920$	$1225\pi/4096 = 0.940$	$1 = 1.000$
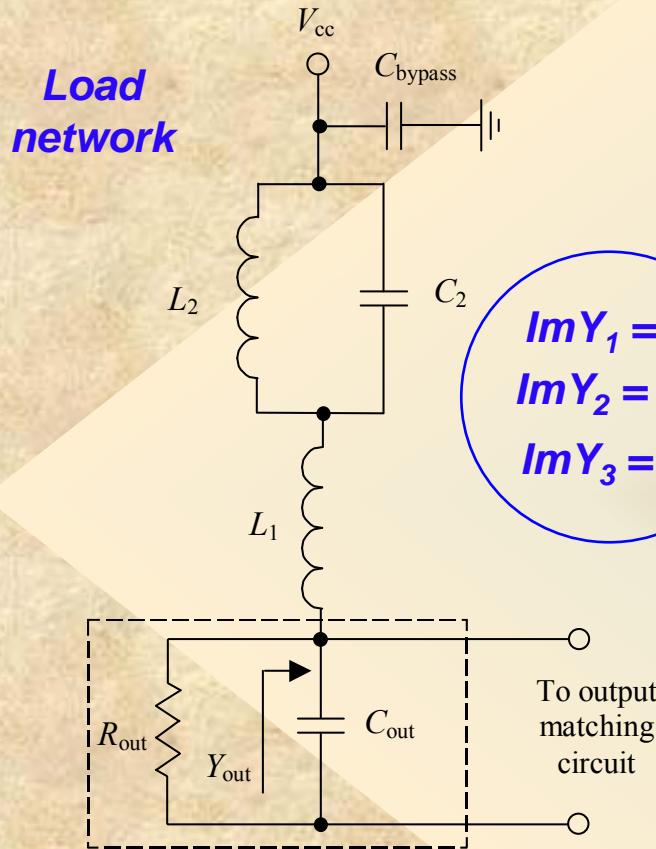
## 4.2. Class F circuit design: second current and third voltage harmonic peaking



**Circuit parameters**

$$L_1 = \frac{1}{6\omega_0^2 C_{out}}, \quad L_2 = \frac{5}{3}L_1, \quad C_2 = \frac{12}{5}C_{out}$$

**Output susceptance:**


$$\text{Im}(Y_{out}) = j\omega C_{out} - j \frac{1 - \omega^2 L_2 C_2}{\omega L_1 (1 - \omega^2 L_2 C_2) + \omega L_2}$$

**Three harmonic impedance conditions:**


$$\begin{cases} (1 - \omega_0^2 L_1 C_{out})(1 - \omega_0^2 L_2 C_2) - \omega_0^2 L_2 C_{out} = 0, \\ L_1 (1 - 4\omega_0^2 L_2 C_2) + L_2 = 0, \\ (1 - 9\omega_0^2 L_1 C_{out})(1 - 9\omega_0^2 L_2 C_2) - 9\omega_0^2 L_2 C_{out} = 0, \end{cases}$$

**$S_{21}$  simulation ( $f_0 = 500$  MHz)**

$S_{21}, \text{dB}$

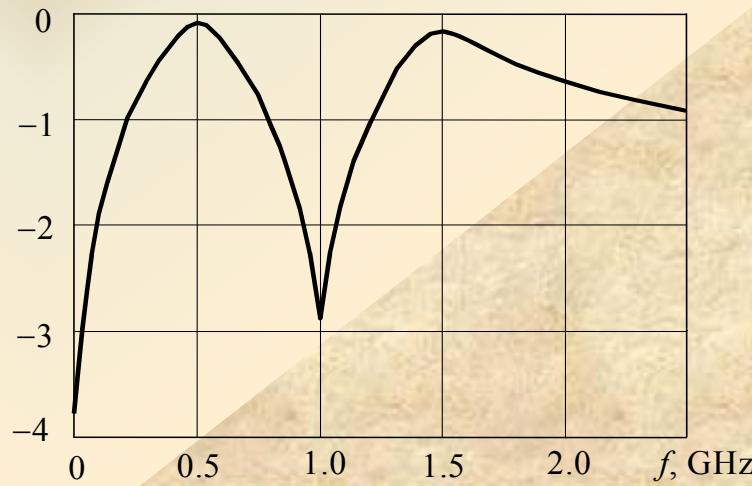
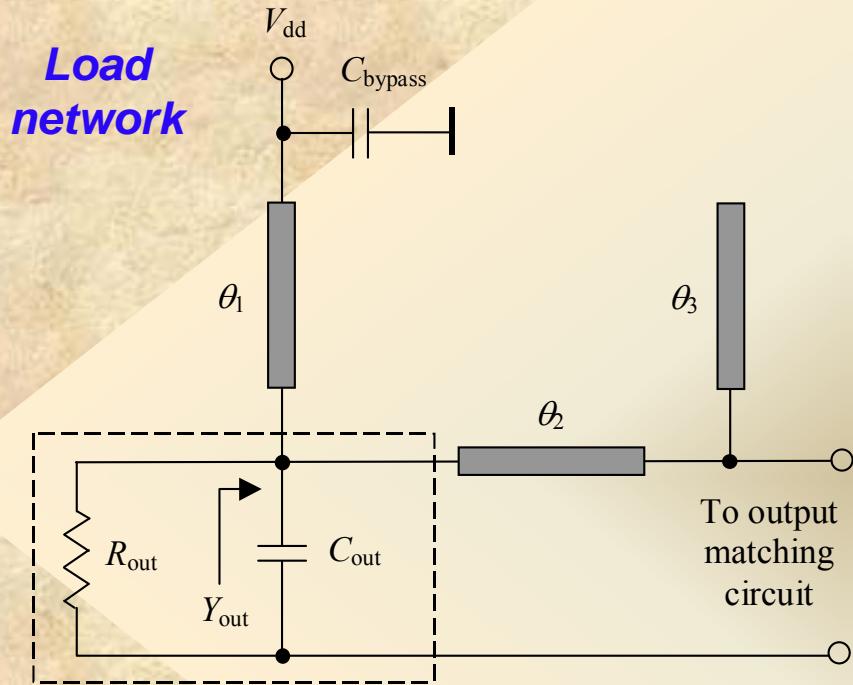
## 4.2. Class F circuit design: even current and third voltage harmonic peaking



**Circuit parameters:**

$$\theta_1 = \frac{\pi}{2}, \quad \theta_3 = \frac{\pi}{6}$$

$$\theta_2 = \frac{1}{3} \tan^{-1} \left( \frac{1}{3Z_0 \omega C_{\text{out}}} \right)$$


**Harmonic impedance conditions:**

$$\text{Im } Y_1 = 0$$

$$\text{Im } Y_{\text{even}} = \infty$$

$$\text{Im } Y_3 = 0$$


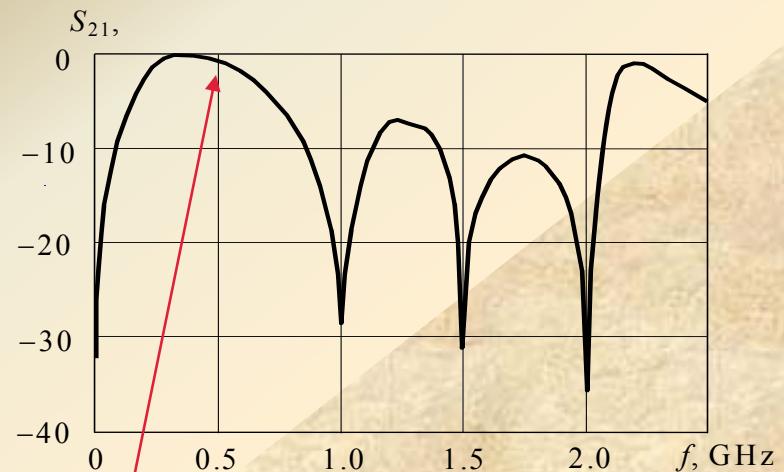
**$S_{21}$  simulation ( $f_0 = 500$  MHz)**




**Requires additional impedance matching at fundamental**

## 4.2. Class F circuit design
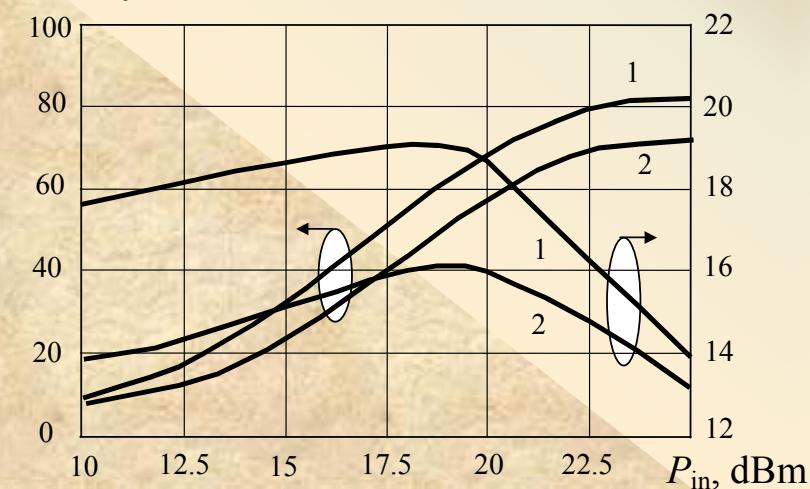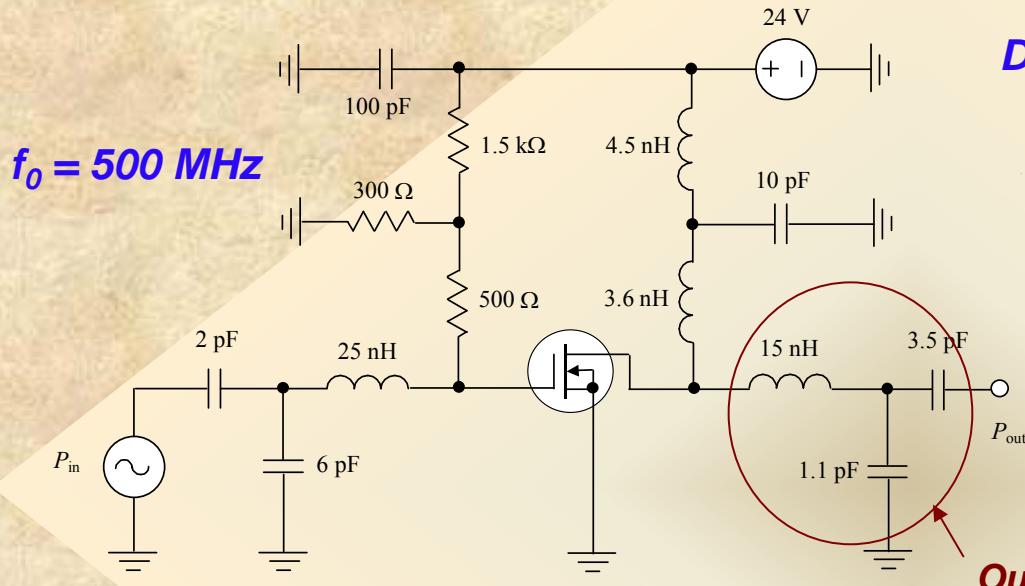
### Class F power amplifier with lumped elements



Drain voltage and current waveforms

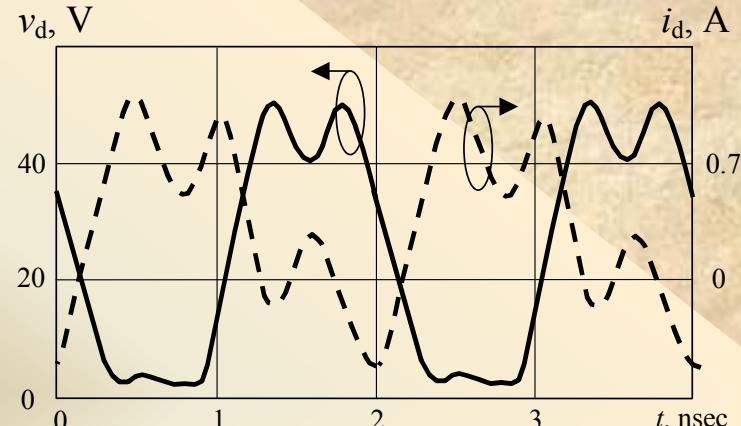

Output matching



LDMOSFET:  
gate length 1.25 um  
gate width 7x1.44 mm

1 - inductance Q-factor =  $\infty$   
efficiency > 82%,  
linear power gain > 16 dB


2 - inductance Q-factor = 30  
efficiency < 71%,  
linear power gain > 14 dB

## 4.2. Class F circuit design
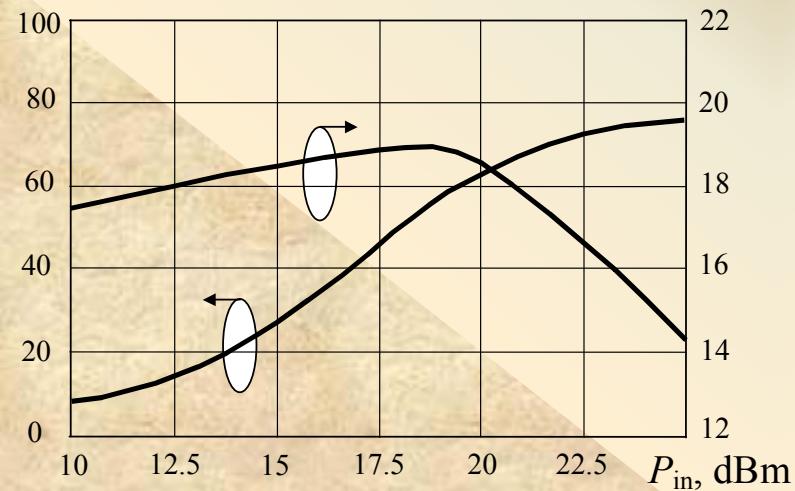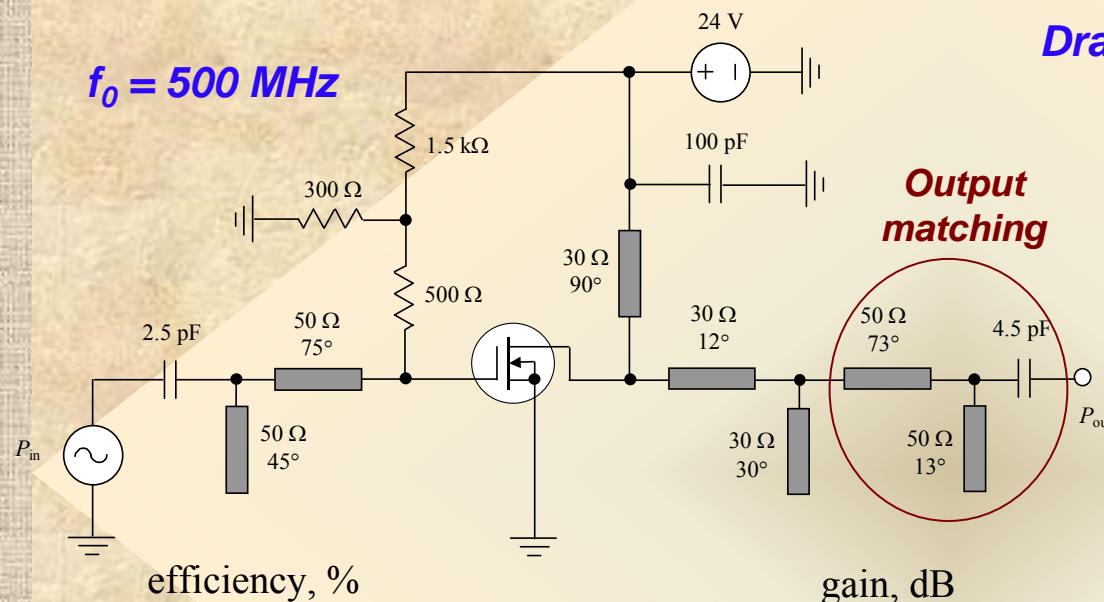
### Class F power amplifier with transmission lines



Drain voltage and current waveforms

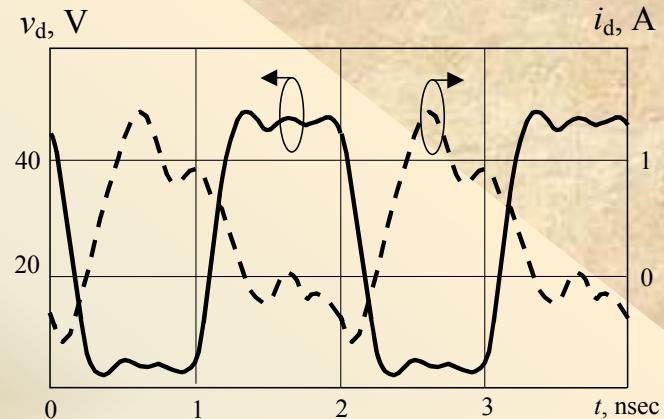

LDMOSFET:  
gate length 1.25 um  
gate width 7x1.44 mm

T-matching circuit for output impedance transformation

Output power - 39 dBm or 8 W


Collector efficiency - 76%

Linear power gain > 16 dB

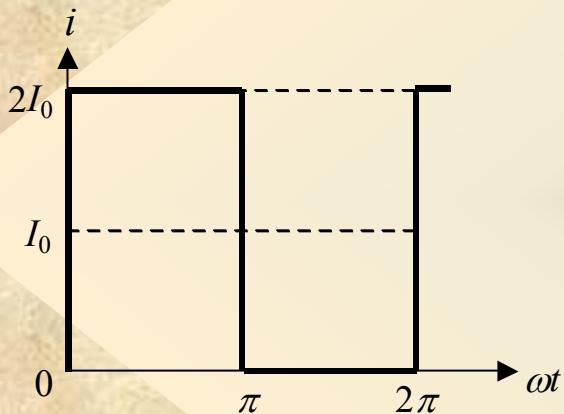
### 4.3. Inverse Class F

*Concept of inverse Class F mode was introduced for low voltage power amplifiers designed for monolithic applications (less collector current)*

*Dual to conventional Class F  
with mutually interchanged  
current and voltage  
waveforms*


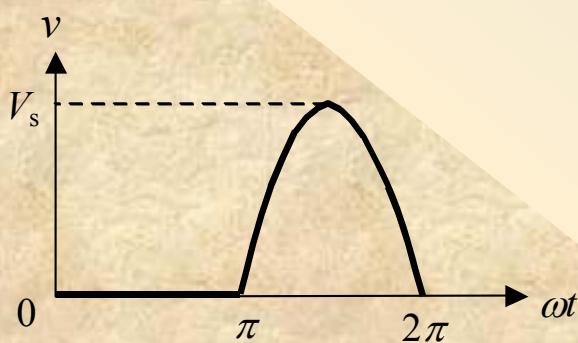
$$\begin{aligned} I_1 &= \frac{4I_0}{\pi} && \text{- fundamental current} \\ V_1 &= \frac{V_s}{2} = \frac{\pi}{2} V_{cc} && \text{- fundamental voltage} \\ P_1 &= \frac{V_s I_0}{\pi} && \text{- fundamental output power} \\ P_0 &= V_{cc} I_0 = \frac{V_s I_0}{\pi} && \text{- DC output power} \\ \eta &= \frac{P_1}{P_0} = 100\% && \text{- ideal collector efficiency} \end{aligned}$$



*Harmonic impedance conditions:*

$$\left\{ \begin{array}{l} Z_1 = R_L = \frac{\pi}{8} \frac{V_s}{I_0} \\ Z_n = 0 \quad \text{for odd } n \\ Z_n = \infty \quad \text{for even } n \end{array} \right.$$

### 4.3. Inverse Class F

**Optimum load resistances for different classes**

**Load resistance in Class B :**

$$R_L^{(B)} = \frac{V_{cc}}{I_1}$$

**Load resistance in Class F :**

$$R_L^{(F)} = \frac{4}{\pi} \frac{V_{cc}}{I_1} = \frac{4}{\pi} R_L^{(B)}$$

**Load resistance in inverse Class F :**


$$R_L^{(\text{invF})} = \frac{\pi}{2} \frac{V_{cc}}{I_1} = \frac{\pi^2}{8} R_L^{(F)} = \frac{\pi}{2} R_L^{(B)}$$

**Load resistance in inverse Class F is the highest (1.6 times larger than in Class B)**



**Less impedance transformation ratio and easier matching procedure**
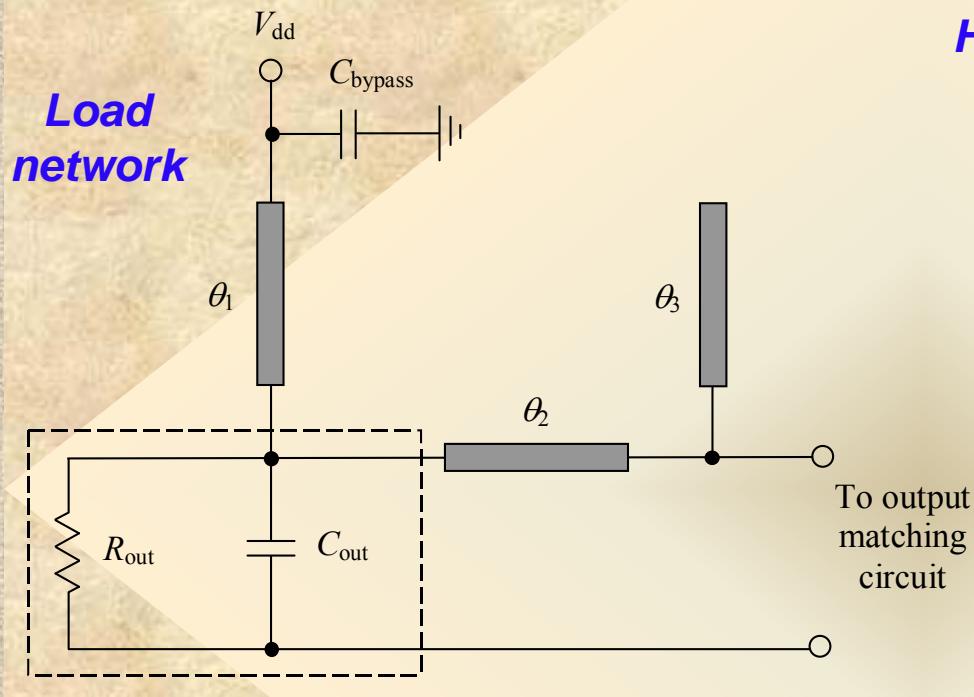
### 4.3. Inverse Class F: second current and third voltage harmonic peaking



**Circuit parameters:**


$$\theta_1 = \frac{\pi}{3}, \quad \theta_3 = \frac{\pi}{4}$$

$$\theta_2 = \frac{1}{2} \tan^{-1} \left[ \left( 2Z_0 \omega C_{\text{out}} - \frac{1}{\sqrt{3}} \right)^{-1} \right]$$

**Harmonic impedance conditions:**

$$\begin{aligned} \text{Im } Y_1 &= 0 \\ \text{Im } Y_2 &= 0 \\ \text{Im } Y_3 &= \infty \end{aligned}$$


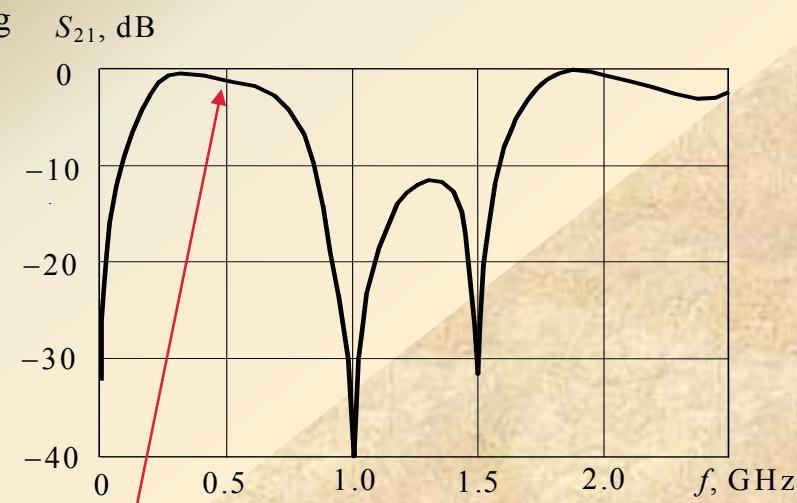
**$S_{21}$  simulation ( $f_0 = 500$  MHz)**




**Requires additional impedance matching at fundamental**

## 4.3. Inverse Class F
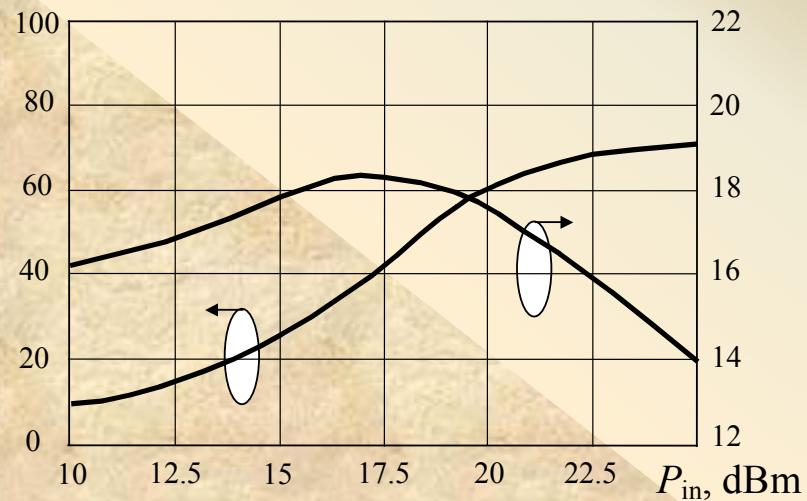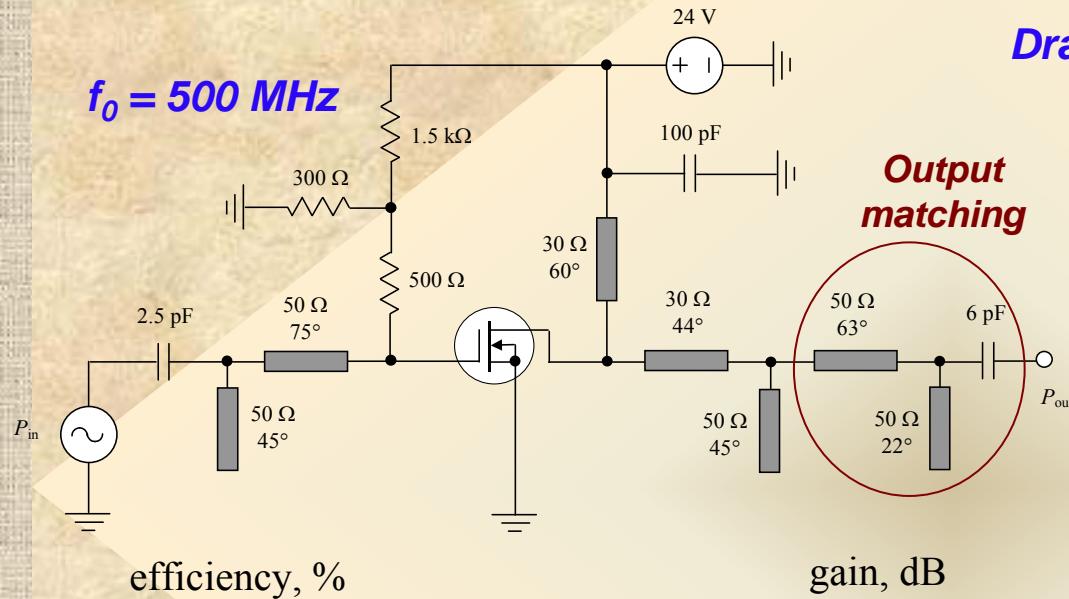
### Inverse Class F power amplifier with transmission lines



Drain voltage and current waveforms

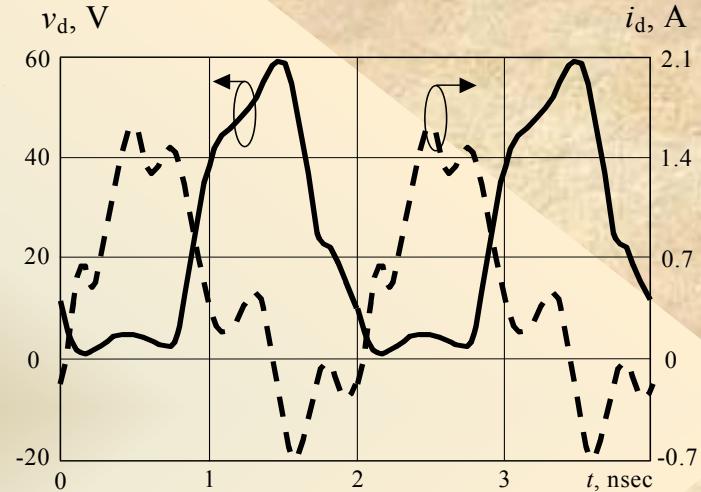

LDMOSFET:  
gate length 1.25 um  
gate width 7x1.44 mm

T-matching circuit for output impedance transformation

Output power - 39 dBm or 8 W


Collector efficiency - 71%

Linear power gain > 16 dB


## 4.3. Inverse Class F

### Inverse Class F power amplifier with transmission lines


$f_0 = 500 \text{ MHz}$

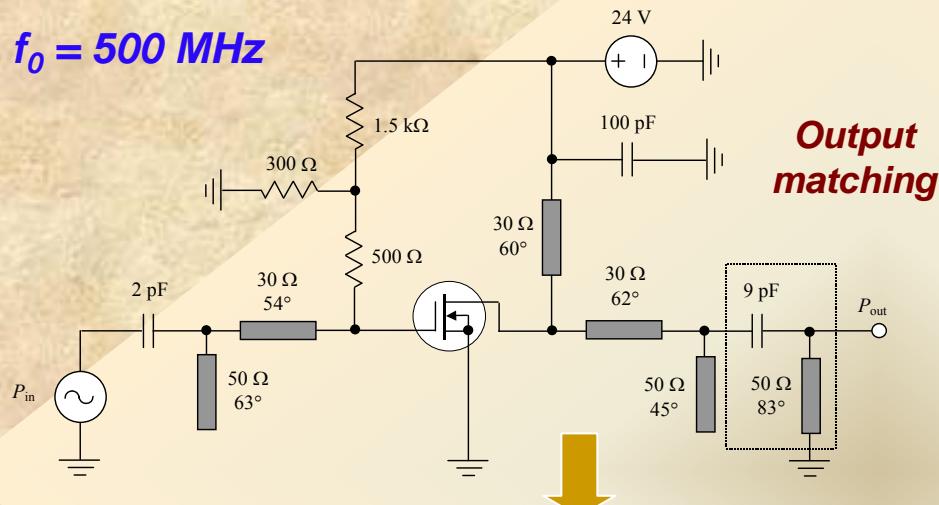


Output matching

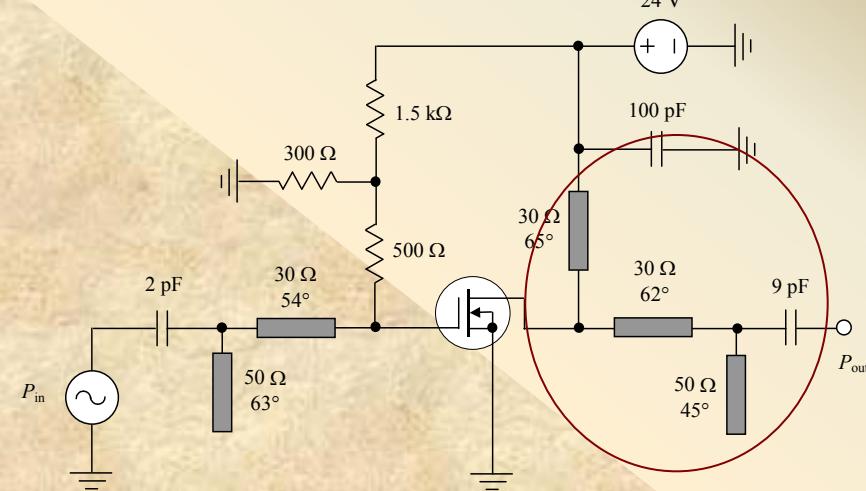


Load network with output matching

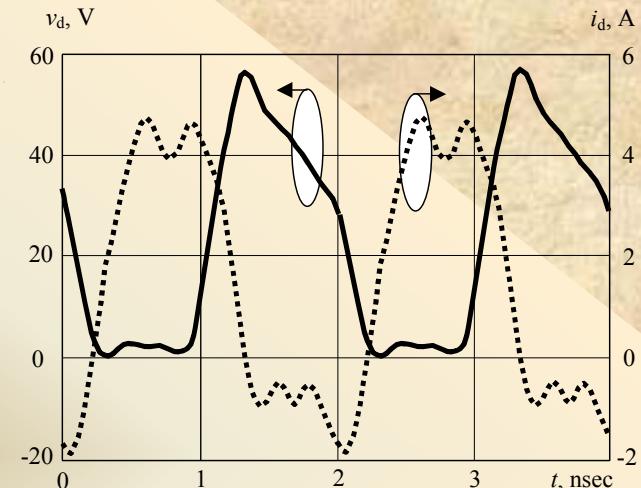

efficiency, %

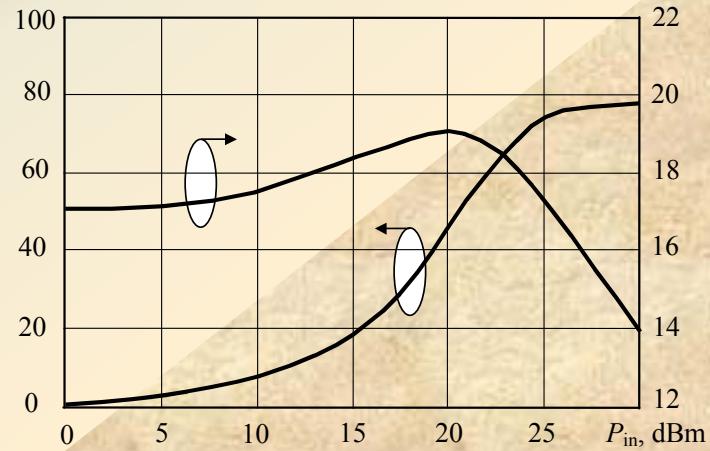

#### 4.4. Class E with shunt capacitance

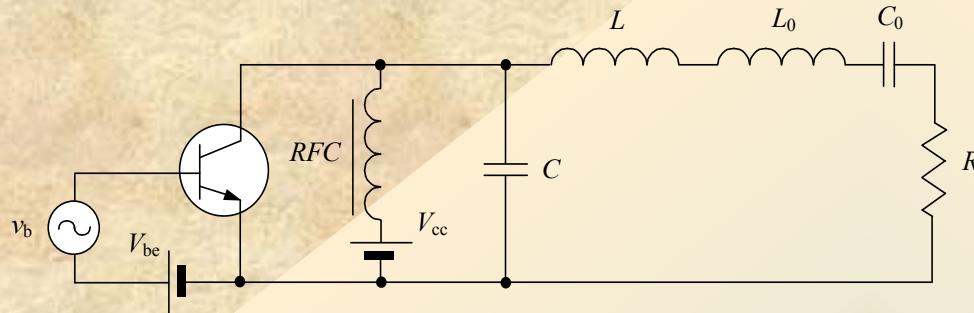

*In Class E power amplifiers, transistor operates as on-to-off switch and ideal shapes of current and voltage waveforms do not overlap simultaneously resulting in 100% efficiency*


*Unlike Class F power amplifiers analyzed in frequency domain as their voltage and current waveforms contain either in-phase or out-of-phase harmonics, Class E power amplifiers are analyzed in time domain as their current and voltage waveforms contain harmonics having specified different phase delays depending on load network configuration*

*Basic circuit of Class E power amplifier with shunt capacitance consists of series inductance  $L$ , capacitor  $C$  shunting transistor, series fundamentally tuned  $L_0C_0$  resonant circuit, RF choke to supply DC current and load  $R$*

*Shunt capacitor  $C$  can represent intrinsic device output capacitance and external circuit capacitance*

*Active device is considered as ideal switch to provide instantaneous device switching between its on-state and off-state operation conditions*

## 4.4. Class E with shunt capacitance

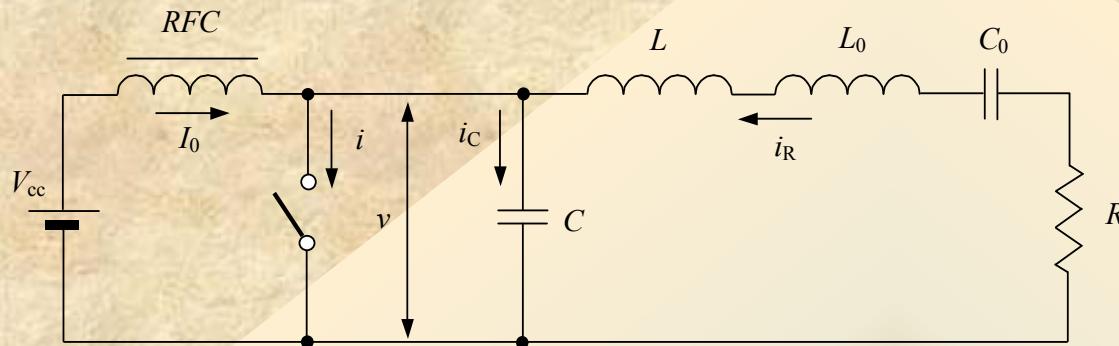

**Optimum voltage conditions across switch:**

$$\left. v(\omega t) \right|_{\omega t=2\pi} = 0$$


$$\left. \frac{dv(\omega t)}{d\omega t} \right|_{\omega t=2\pi} = 0$$

**Idealized assumptions for analysis:**

- transistor has zero saturation voltage, zero on-resistance, infinite off-resistance and its switching action is instantaneous and lossless
- total shunt capacitance is assumed to be linear
- RF choke allows only DC current and has no resistance
- loaded quality factor  $Q_L$  of series fundamentally tuned resonant  $L_0C_0$ -circuit is infinite to provide pure sinusoidal current flowing into load
- reactive elements in load network are lossless
- for optimum operation 50% duty cycle is used

$$i_R(\omega t) = I_R \sin(\omega t + \varphi) \quad - \text{sinusoidal current flowing into load}$$

## 4.4. Class E with shunt capacitance

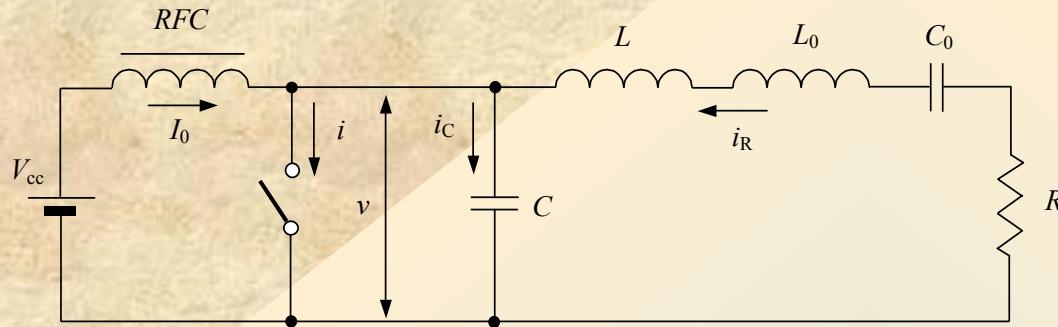

**Optimum voltage conditions across switch:**

$$v(\omega t) \Big|_{\omega t=2\pi} = 0$$

$$\frac{dv(\omega t)}{d\omega t} \Big|_{\omega t=2\pi} = 0$$

$0 \leq \omega t < \pi$  - switch is on  $\Rightarrow i_C(\omega t) = \omega C \frac{dv(\omega t)}{d\omega t} = 0$

$$\Rightarrow i(\omega t) = I_0 + I_R \sin(\omega t + \varphi) \quad \text{or using initial condition} \quad i(0) = 0$$

when  $I_0 = -I_R \sin \varphi$   $\rightarrow$   $i(\omega t) = I_R [\sin(\omega t + \varphi) - \sin \varphi]$


$\pi \leq \omega t < 2\pi$  - switch is off  $\Rightarrow i(\omega t) = 0 \Rightarrow i_C(\omega t) = I_0 + I_R \sin(\omega t + \varphi)$

$$\Rightarrow v(\omega t) = \frac{1}{\omega C} \int_{\pi}^{\omega t} i_C(\omega t) d\omega t = -\frac{I_R}{\omega C} [\cos(\omega t + \varphi) + \cos \varphi + (\omega t - \pi) \sin \varphi]$$

From first optimum condition:  $\varphi = \tan^{-1} \left( -\frac{2}{\pi} \right) = -32.482^\circ$

$$\Rightarrow v(\omega t) = \frac{I_0}{\omega C} \left( \omega t - \frac{3\pi}{2} - \frac{\pi}{2} \cos \omega t - \sin \omega t \right)$$

## 4.4. Class E with shunt capacitance

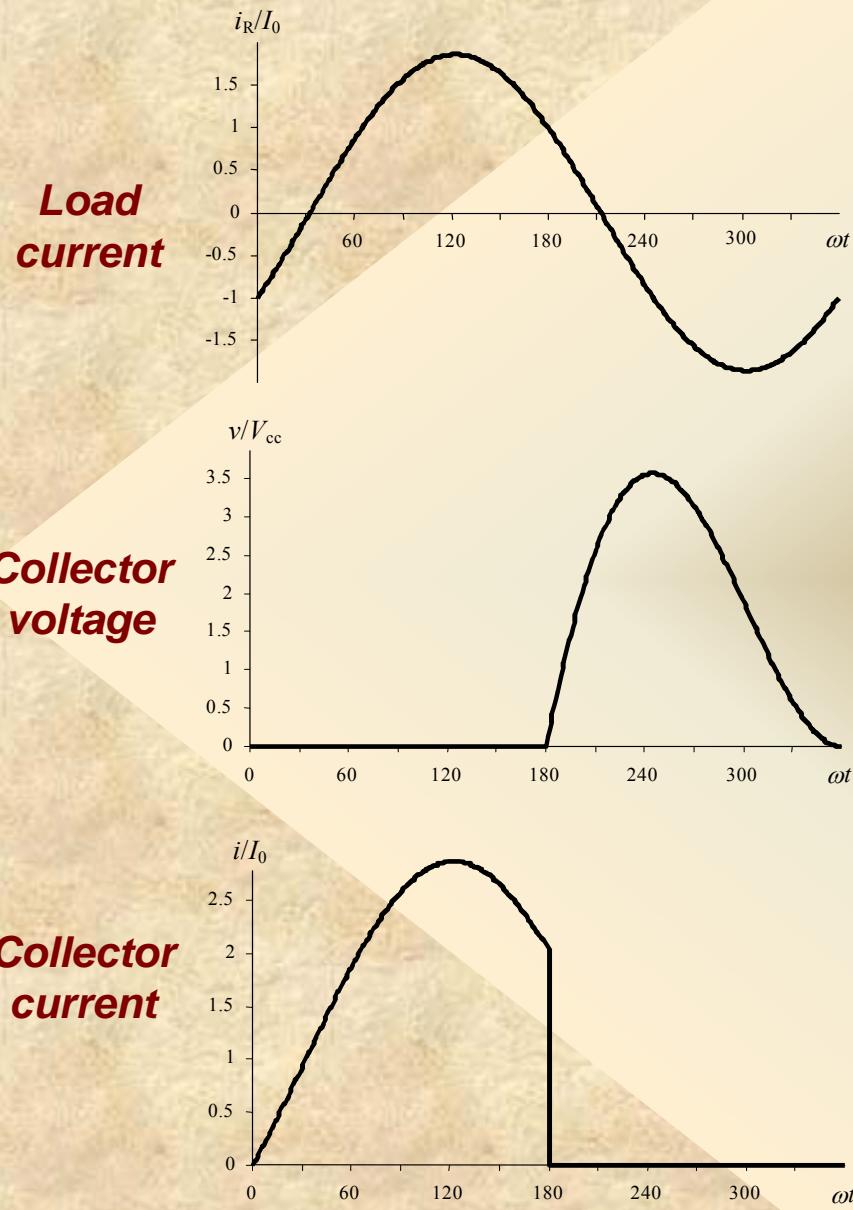

**Optimum circuit parameters :**


$$L = 1.1525 \frac{R}{\omega} \quad \text{- series inductance}$$

$$C = 0.1836 \frac{1}{\omega R} \quad \text{- shunt capacitance}$$




$$R = 0.5768 \frac{V_{cc}^2}{P_{out}} \quad \text{- load resistance}$$

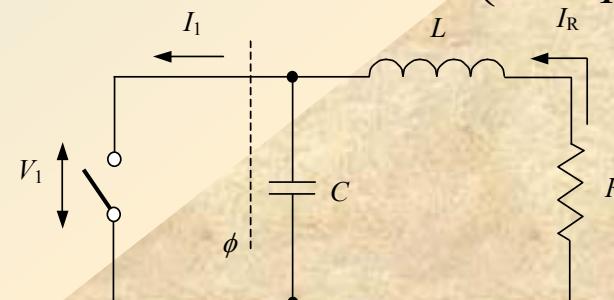**Optimum phase angle at fundamental seen by switch :**

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right) - \tan^{-1}\left(\frac{\omega CR}{1 - \frac{\omega L}{R}\omega CR}\right)$$



## 4.4. Class E with shunt capacitance

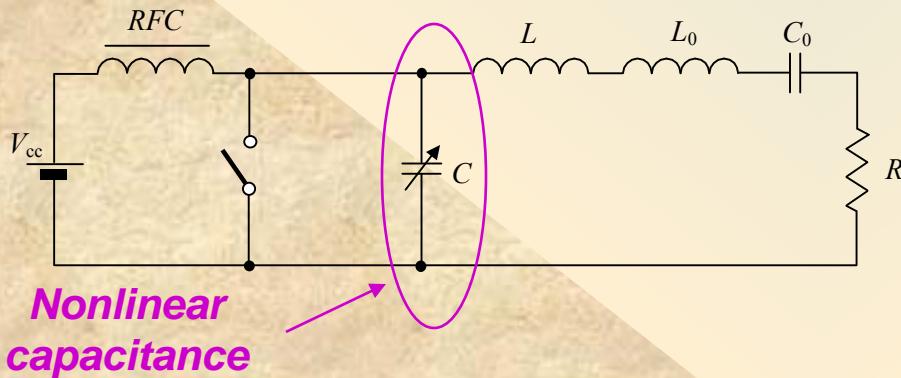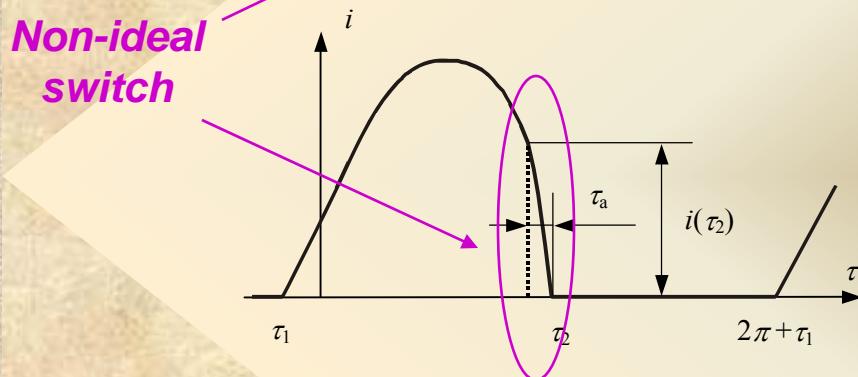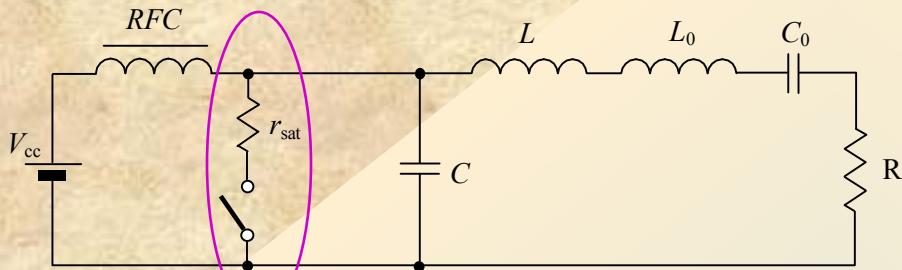

**Power loss due to non-zero saturation resistance**

$$P_{\text{sat}} \cong \frac{8}{3} \frac{r_{\text{sat}} P_{\text{out}}^2}{V_{\text{cc}}^2} \cong 3 \frac{r_{\text{sat}}}{R}$$


**Power loss due to finite switching time**

$$P_{\text{a}} \cong \frac{\tau_{\text{a}}^2}{12}$$

where  $\tau_{\text{a}} = 0.35$  or  $20^\circ$   
Only 1%

For nonlinear capacitances represented by abrupt junction collector capacitance with  $\gamma = 0.5$ , peak collector voltage increases by 20%

## 4.5. Class E with parallel circuit

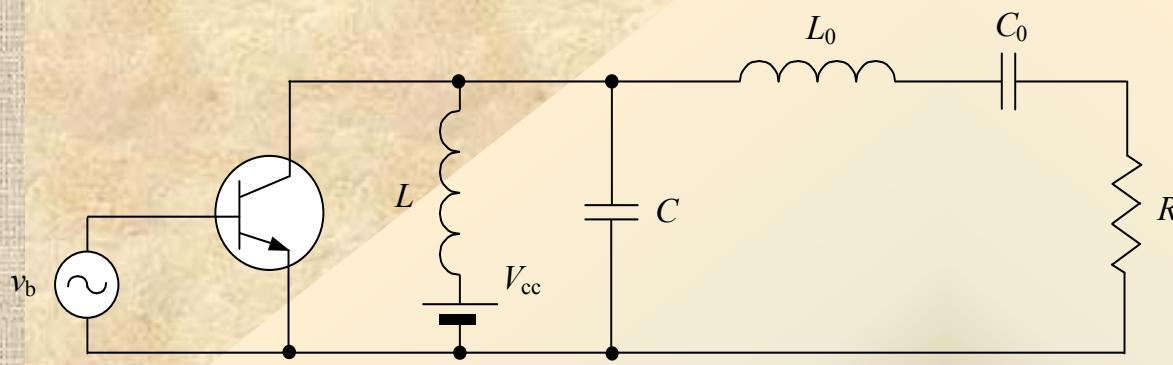

**Optimum voltage conditions across switch:**


$$v(\omega t) \Big|_{\omega t=2\pi} = 0$$

$$\frac{dv(\omega t)}{d\omega t} \Big|_{\omega t=2\pi} = 0$$

$$i_R(\omega t) = I_R \sin(\omega t + \varphi) \quad - \text{sinusoidal current in load}$$

- basic circuit of Class E power amplifier with parallel circuit consists of parallel inductance  $L$  supplying also DC current, parallel capacitor  $C$  shunting transistor, series fundamentally tuned  $L_0C_0$  resonant circuit and load  $R$
- shunt capacitor  $C$  can represent intrinsic device output capacitance and external circuit capacitance
- active device is considered as ideal switch to provide instantaneous device switching between its on-state and off-state operation conditions

## 4.5. Class E with parallel circuit

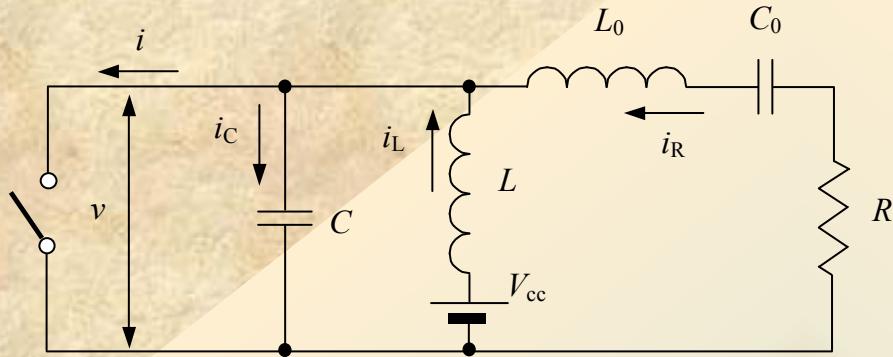

**Optimum voltage conditions across switch:**

$$\left. v(\omega t) \right|_{\omega t=2\pi} = 0$$

$$\left. \frac{dv(\omega t)}{d\omega t} \right|_{\omega t=2\pi} = 0$$

$$0 \leq \omega t < \pi$$

- **switch is on**  $\Rightarrow$   $v(\omega t) = V_{cc} - v_L(\omega t) = 0$  and  $i_C(\omega t) = \omega C \frac{dv(\omega t)}{d\omega t} = 0$

$$i(\omega t) = i_L(\omega t) + i_R(\omega t) = \frac{V_{cc}}{\omega L} \omega t + I_R [\sin(\omega t + \varphi) - \sin \varphi]$$

$$\pi \leq \omega t < 2\pi$$

- **switch is off**  $\Rightarrow$   $i(\omega t) = 0 \Rightarrow i_C(\omega t) = i_L(\omega t) + i_R(\omega t)$

$$\omega C \frac{dv(\omega t)}{d(\omega t)} = \frac{1}{\omega L} \int_{\pi}^{\omega t} [V_{cc} - v(\omega t)] d(\omega t) + i_L(\pi) + I_R \sin(\omega t + \varphi)$$

**under initial conditions**  $v(\pi) = 0$  and  $i_L(\pi) = \frac{V_{cc}\pi}{\omega L} - I_R \sin \varphi$

## 4.5. Class E with parallel circuit

$$\omega^2 LC \frac{d^2 v(\omega t)}{d(\omega t)^2} + v(\omega t) - V_{cc} - \omega L I_R \cos(\omega t + \varphi) = 0 \quad \text{- second-order differential equation}$$



$$\frac{v(\omega t)}{V_{cc}} = C_1 \cos(q\omega t) + C_2 \sin(q\omega t) + 1 - \frac{q^2 p}{1 - q^2} \cos(\omega t + \varphi)$$

**where**  $q = 1/\omega\sqrt{LC}$ ,  $p = \frac{\omega L I_R}{V_{cc}}$  **and coefficients  $C_1$  and  $C_2$  are defined from initial conditions**



**To define three unknown parameters  $q$ ,  $\varphi$  and  $p$ , two optimum conditions and third equation for DC Fourier component are applied resulting to system of three algebraic equations:**

$$v(\omega t) \Big|_{\omega t=2\pi} = 0 \quad \frac{dv(\omega t)}{d\omega t} \Big|_{\omega t=2\pi} = 0 \quad V_{cc} = \frac{1}{2\pi} \int_0^{2\pi} v(\omega t) d\omega t$$





$q = 1.412$	$\varphi = 15.155^\circ$	$p = 1.21$
-------------	--------------------------	------------


## 4.5. Class E with parallel circuit

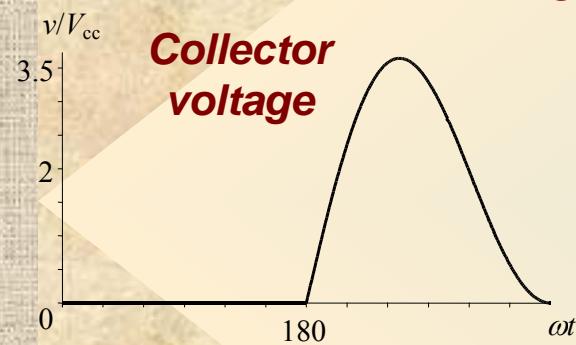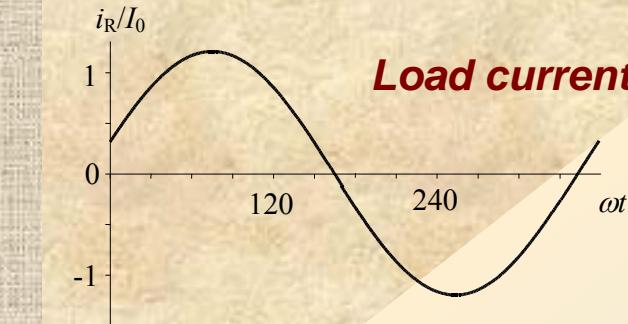

**Current through capacitance**

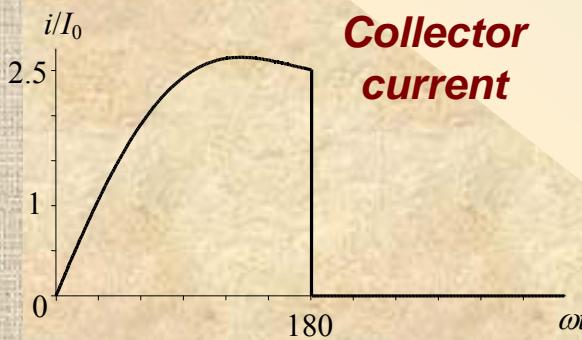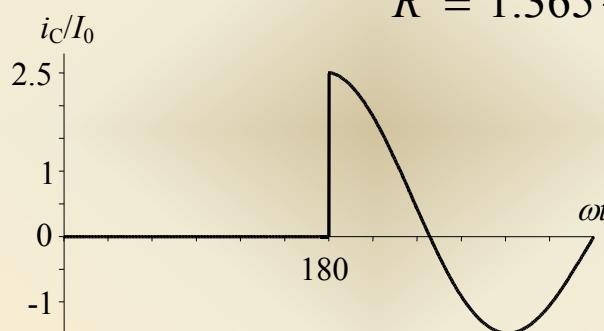

**Current through inductance**

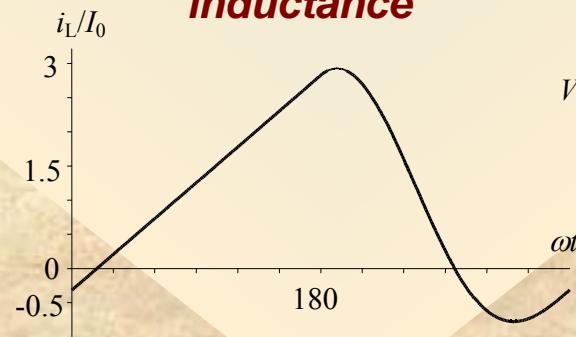

**Optimum circuit parameters :**

$$L = 0.732 \frac{R}{\omega}$$

$$C = \frac{0.685}{\omega R}$$

$$R = 1.365 \frac{V_{cc}^2}{P_{out}}$$


- parallel inductance

- parallel capacitance

- load resistance



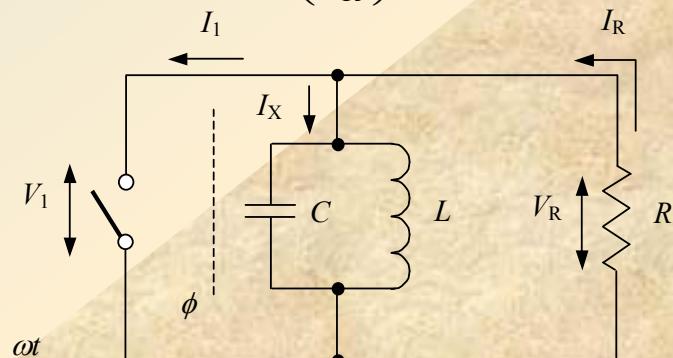
**Optimum phase angle at fundamental seen by switch :**

$$\phi = \tan^{-1} \left( \frac{I_X}{I_R} \right) = 34.244^\circ$$



## 4.6. Class E with transmission lines: approximation
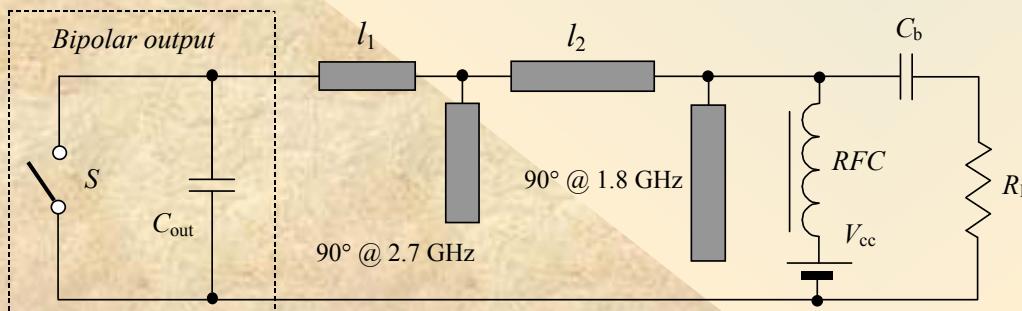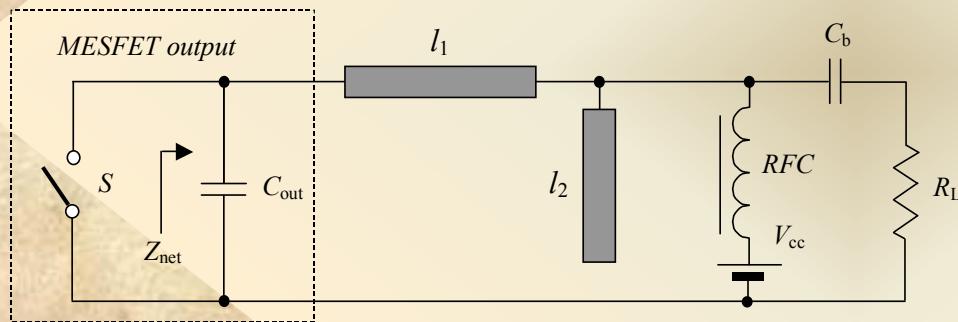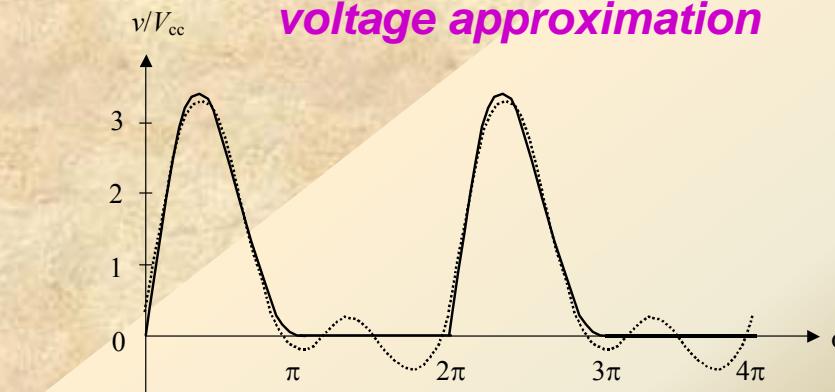
### Two-harmonic collector voltage approximation



**Optimum impedance at fundamental seen by device :**

$$Z_{\text{net}1} = R \left( 1 + j \tan 49.052^\circ \right)$$


- **electrical lengths of transmission lines  $l_1$  and  $l_2$  should be of  $45^\circ$  to provide open circuit seen by device at second harmonic**

- **their characteristic impedances are chosen to provide optimum inductive impedance seen by device at fundamental**


- **for three harmonic approximation, additional open circuit transmission line stub with 90-degree electrical length at third harmonic is required ( 1.5 GHz, 1.5 W, 90% )**

## 4.6. Class E with transmission lines: approximation

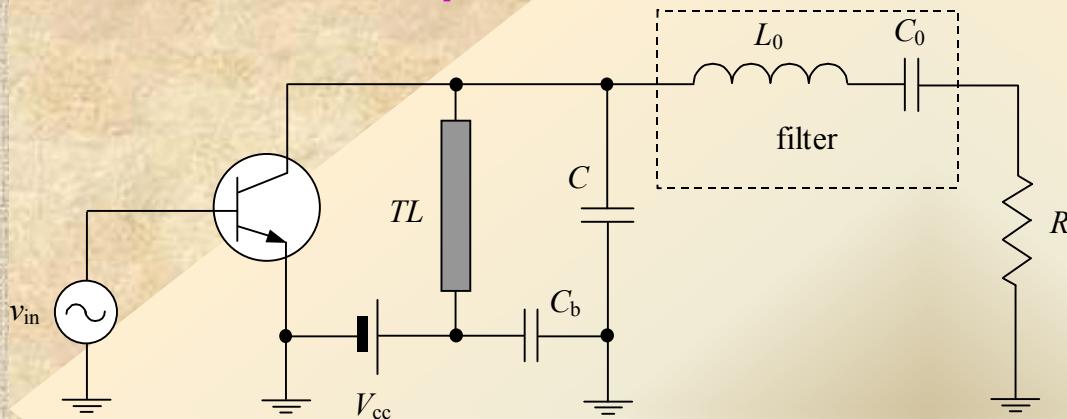
**Transmission-line Class E power amplifier with parallel circuit**



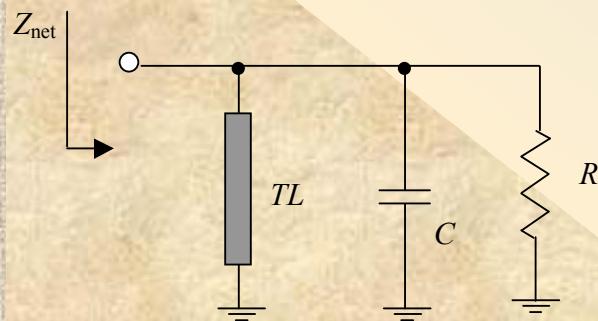**Impedance seen by device at fundamental**



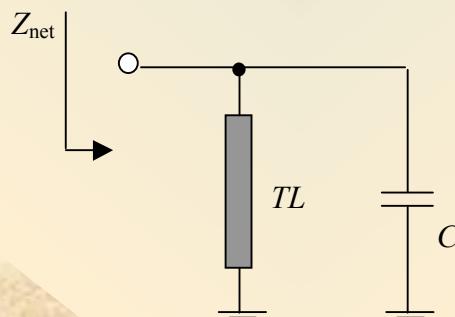**Impedance seen by device at harmonics**



**Optimum impedance at fundamental seen by device :**

$$Z_{\text{net1}} = R / \left( 1 - j \tan 34.244^\circ \right)$$

**Parallel inductance is replaced by transmission line providing optimum inductive reactance at fundamental :**

$$Z_0 \tan \theta = \omega L$$



$$\text{where } L = 0.732 \frac{R}{\omega}$$



**Relationship between optimum transmission line and load parameters :**


$$\tan \theta = 0.732 \frac{R}{Z_0}$$
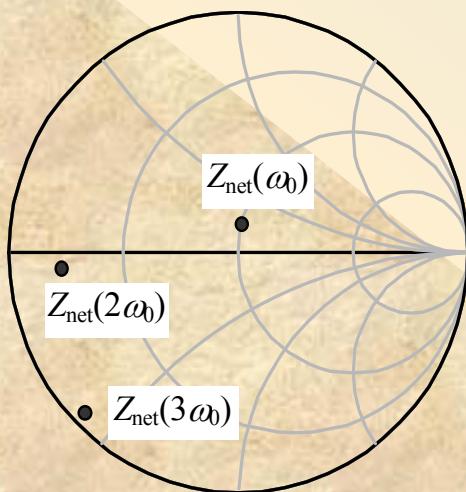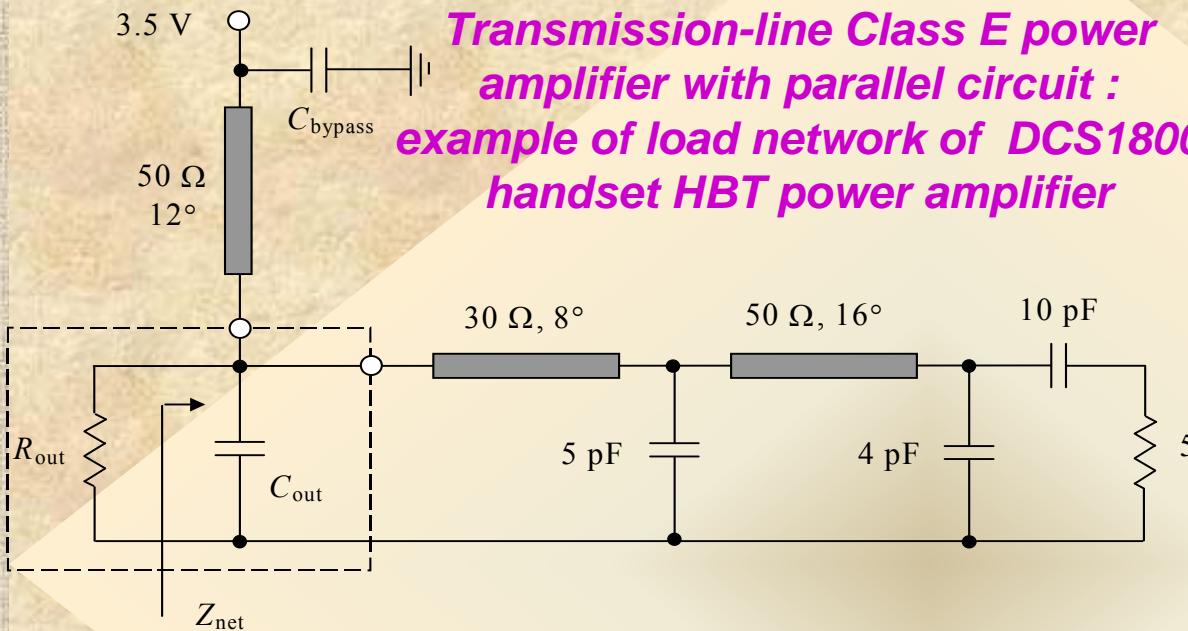
## 4.6. Class E with transmission lines: approximation




- parameters of parallel transmission line is chosen to realize optimum inductive impedance at fundamental
- output matching circuit consisting of series microstrip line with two parallel capacitances should provide capacitive reactances at second and third harmonics

**Collector voltage**

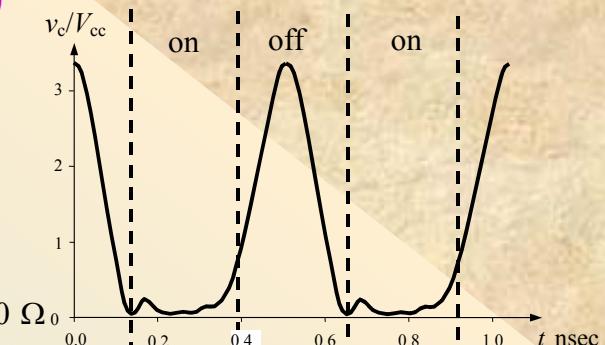


**Collector current**

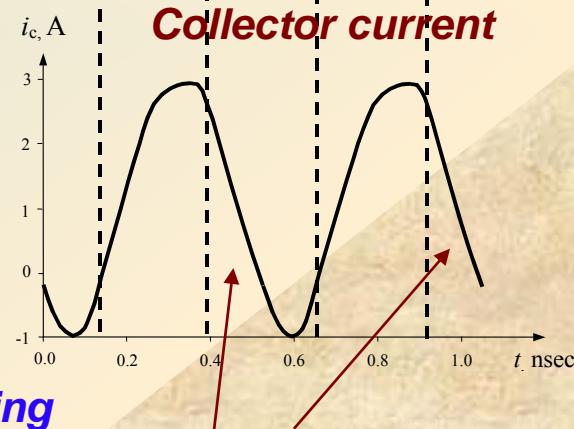

**Current flowing through collector capacitance**



## 4.6. Class E with transmission lines: design example

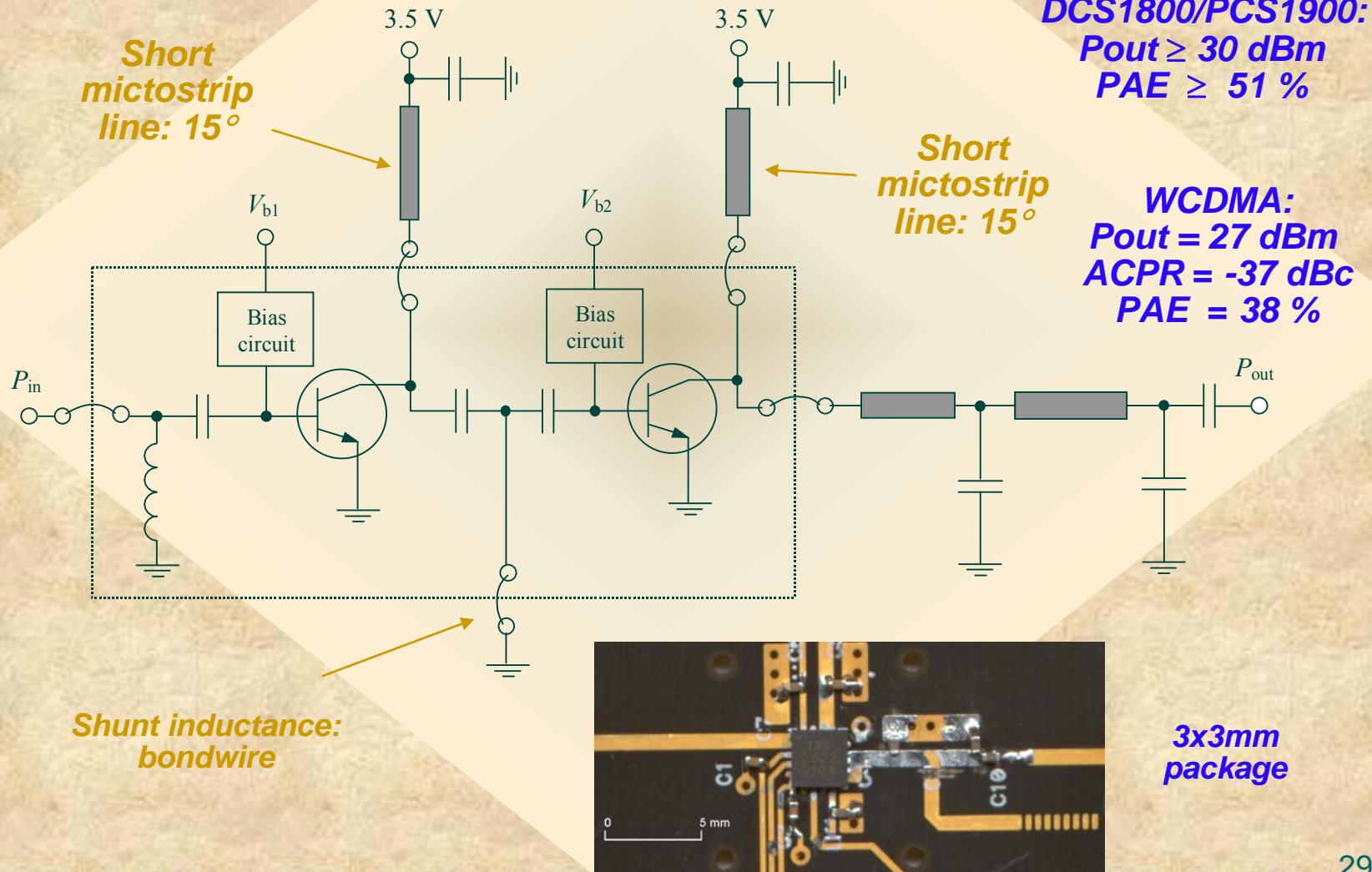1.71-1.98 GHz handset InGaP/GaAs HBT power amplifier:  
two-stage MMIC designed in 2001



## 4.6. Class E with transmission lines: design example
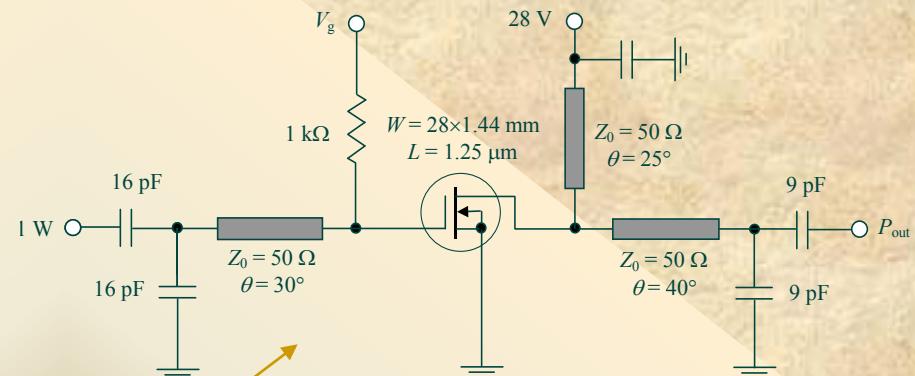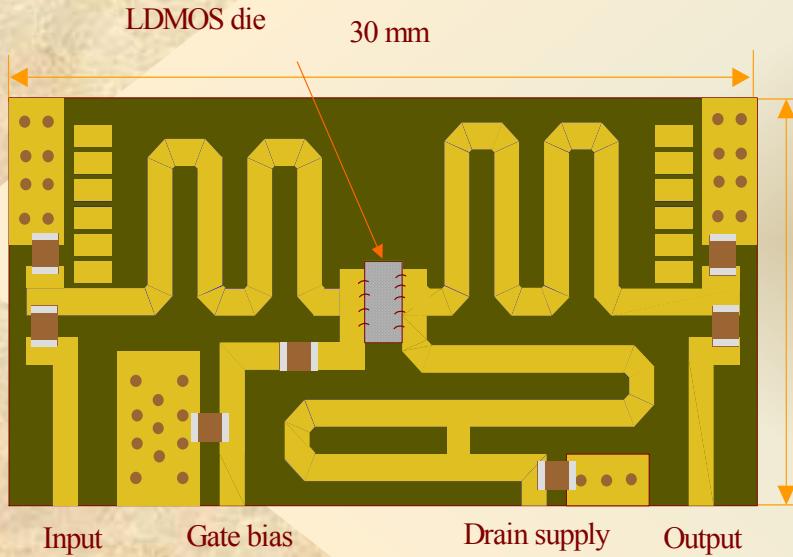
### 28 V single-stage LDMOSFET power amplifier module




**Bandwidth: 480-520 MHz**


**Output power: 20 W**

**Power gain: 15 dB**

**PAE: 67%**

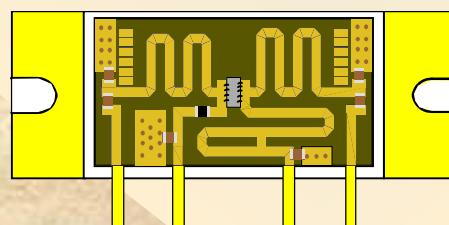
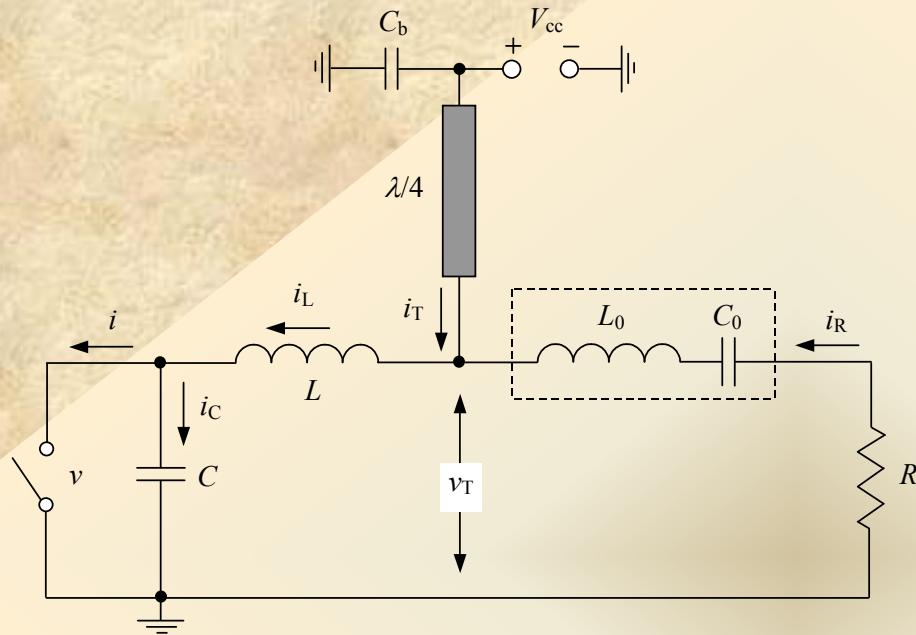
## 4.6. Class E with quarterwave transmission line



**Optimum voltage conditions  
across switch:**

$$\left. \begin{aligned} v(\omega t) &= 0 \\ \frac{dv(\omega t)}{d\omega t} &= 0 \end{aligned} \right|_{\omega t=2\pi}$$

- sinusoidal load current
- 50% duty cycle

$$\frac{d^2 i_C(\omega t)}{d(\omega t)^2} + \frac{q^2}{2} i_C(\omega t) + I_R \sin(\omega t + \varphi) = 0$$

- second-order differential equation

**boundary conditions:**

$$i_C(\omega t) \Big|_{\omega t=\pi} = 2i_R(\pi)$$


$$\left. \frac{di_C(\omega t)}{d(\omega t)} \right|_{\omega t=\pi} = \frac{V_{cc}}{\omega L} - I_R \cos(\varphi)$$

$$p = \frac{\omega L I_R}{V_{cc}} \quad q = 1/\omega \sqrt{LC}$$


$$q = 1.649 \quad p = 1.302 \quad \varphi = -40.8^\circ$$

## 4.6. Class E with quarterwave transmission line


**Load current**

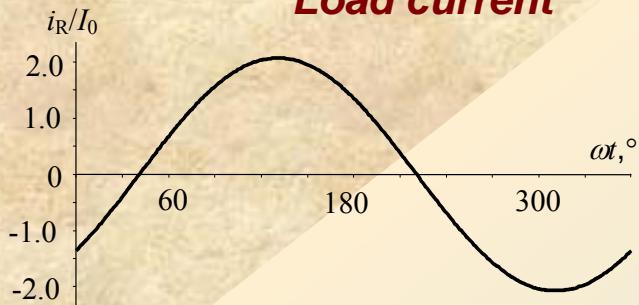

**Collector voltage**

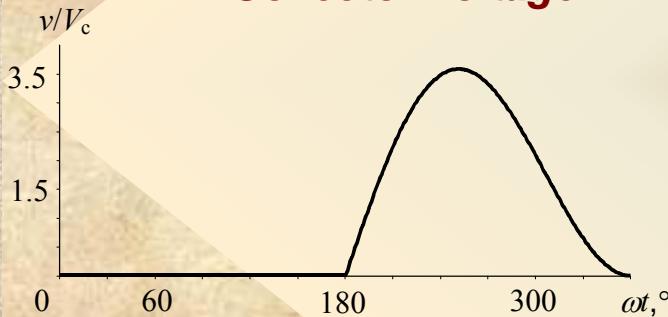

**Collector current**

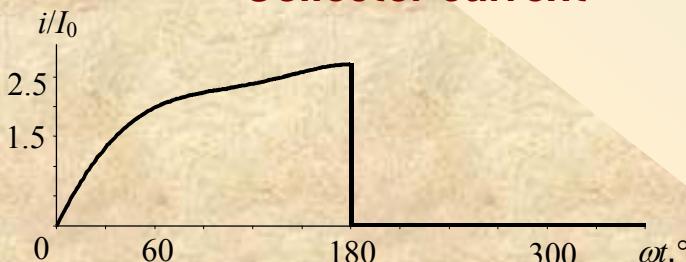

**Optimum circuit parameters :**

$$L = 1.349 \frac{R}{\omega}$$

$$C = \frac{0.2725}{\omega R}$$


$$R = 0.465 \frac{V_{cc}^2}{P_{out}}$$

- series inductance


- shunt capacitance

- load resistance

**Current through capacitance**









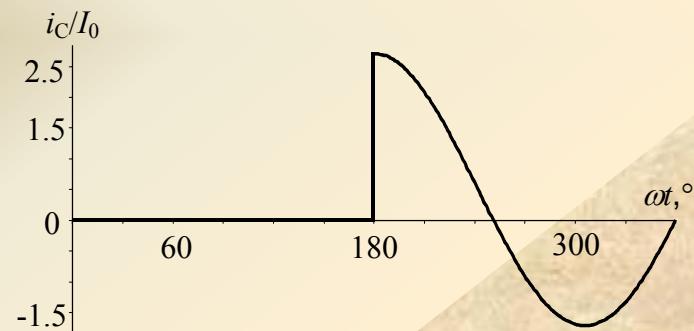


**Current through transmission line**

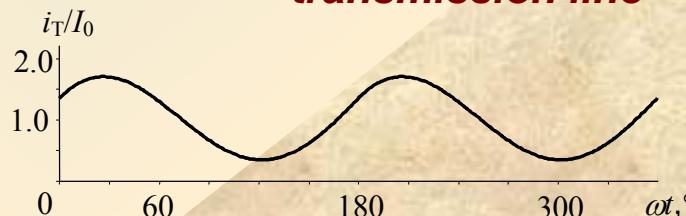


## 4.6. Class E with quarterwave transmission line

*Optimum impedances at fundamental and harmonics for different Class E load networks*

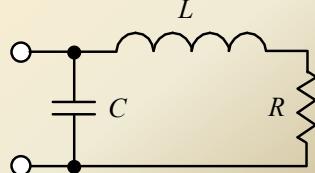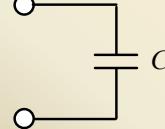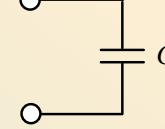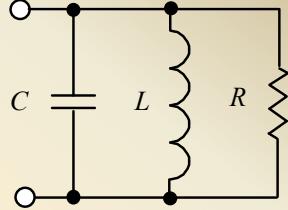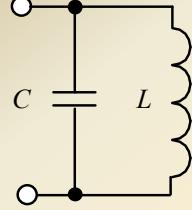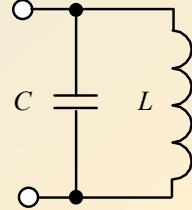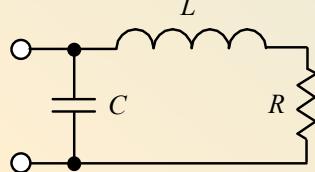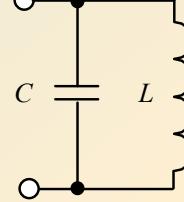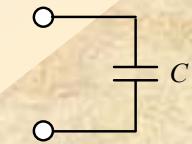
Class E load network	$f_0$ (fundamental)	$2nf_0$ (even harmonics)	$(2n+1)f_0$ (odd harmonics)
Class E with shunt capacitance			
Class E with parallel circuit			
Class E with quarterwave transmission line			

## 4.7. Broadband Class E circuit design

### Reactance compensation load network

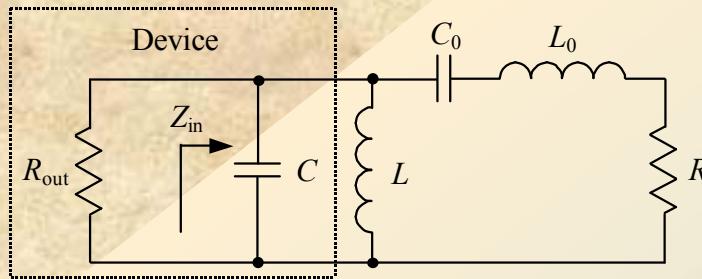

### Reactance compensation principle

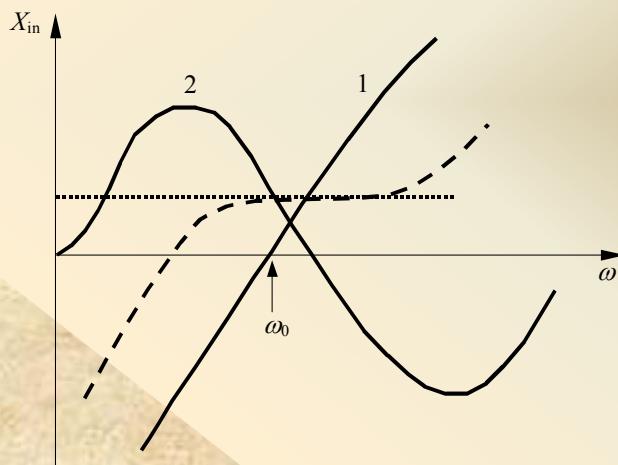

**1 - impedance provided by series  $L_0C_0$  resonant circuit**

**2 - impedance provided by parallel LC resonant circuit**

- summation of reactances with opposite slopes results in constant load phase over broad frequency range**

### Input load network admittance

$$Y_{in} = \left( j\omega C + \frac{1}{j\omega L} + \frac{1}{R + j\omega' L_0} \right)$$

$$\omega' = \omega \left( 1 - \frac{\omega_0^2}{\omega^2} \right) \quad \omega_0 = 1/\sqrt{L_0 C_0}$$

**To maximize bandwidth:**

$$\frac{d \operatorname{Im} Y_{in}(\omega)}{d\omega} \Big|_{\omega=\omega_0} = 0$$

$$C + \frac{1}{\omega^2 L} - \frac{2L_0}{R^2} = 0$$


**Optimum circuit parameters using equations for inductance  $L$  and capacitance  $C$  in Class E mode**

$$L_0 = 1.026 \frac{R}{\omega}$$

$$C_0 = 1/\omega^2 L_0$$

## 4.7. Broadband Class E circuit design
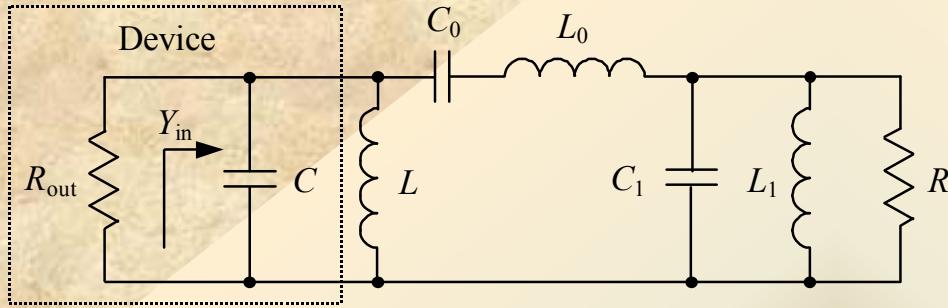
### Double reactance compensation load network




To maximize bandwidth:

$$\frac{dB}{d\omega} \Big|_{\omega=\omega_0} = \frac{d^3B}{d\omega^3} \Big|_{\omega=\omega_0} = 0$$

$$C + \frac{1}{\omega^2 L} - 2 \frac{C_1 R^2 - L_0}{R^2} = 0$$

$$\frac{1}{\omega^2 L} + \frac{C_1 R^2 - L_0}{R^2} - 8\omega^2 L_0 \left[ C_1^2 + \frac{(C_1 R^2 - L_0)(L_0 - 2C_1 R^2)}{R^4} \right] = 0$$

### Load network phase angle

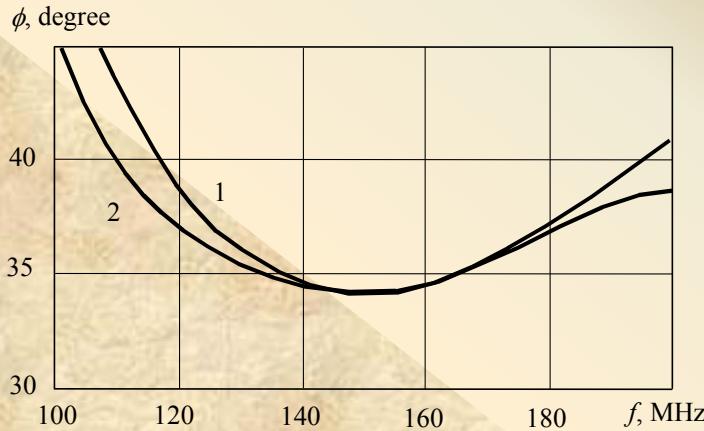

Optimum circuit parameters using equations for inductance  $L$  and capacitance  $C$  in Class E mode

$$L_0 = \frac{R}{\omega} \frac{2}{\sqrt{5} - 1}$$

$$C_0 = \frac{1}{\omega^2 L_0}$$

$$C_1 = \frac{L_0}{R^2} \frac{3 - \sqrt{5}}{2}$$



$$L_1 = \frac{1}{\omega^2 C_1}$$

1 - single reactance compensation load network


2 - double reactance compensation load network

## 4.7. Broadband Class E circuit design
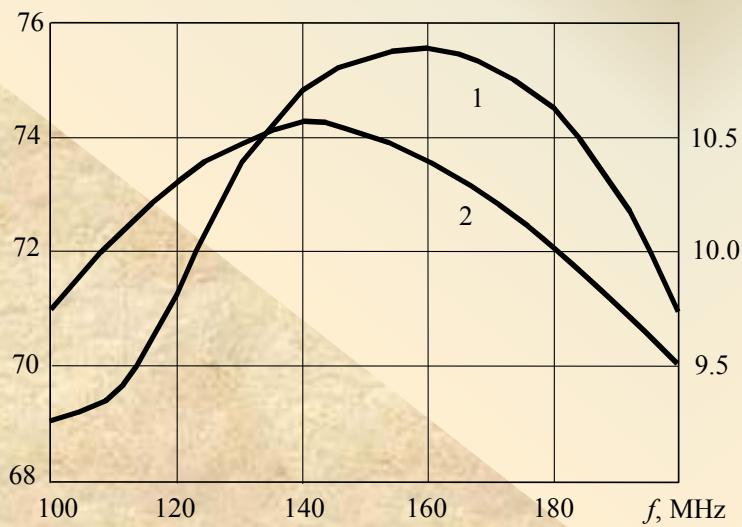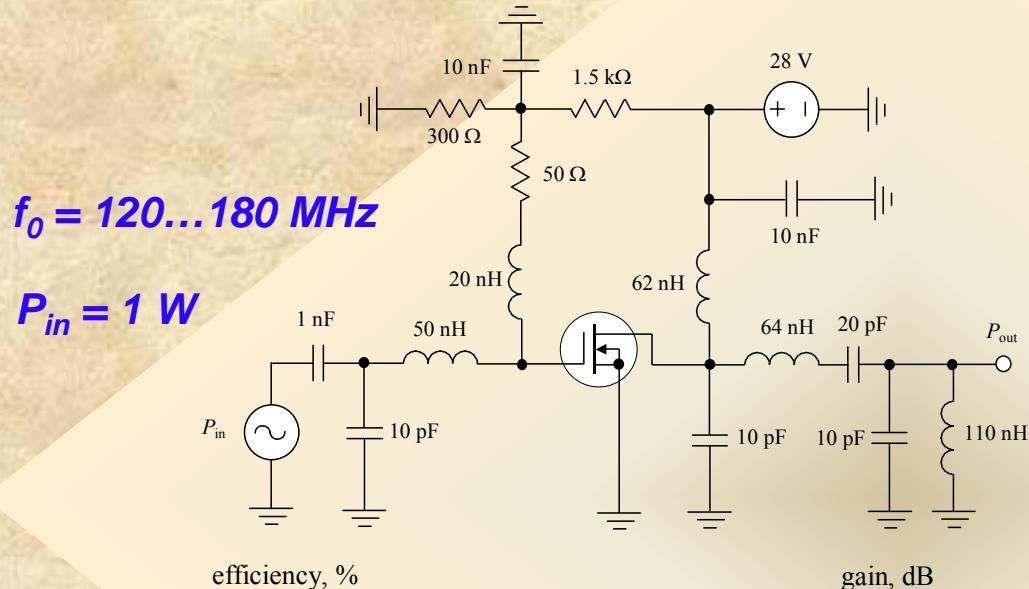
### Broadband Class E power amplifier with double reactance compensation



Drain voltage and current waveforms

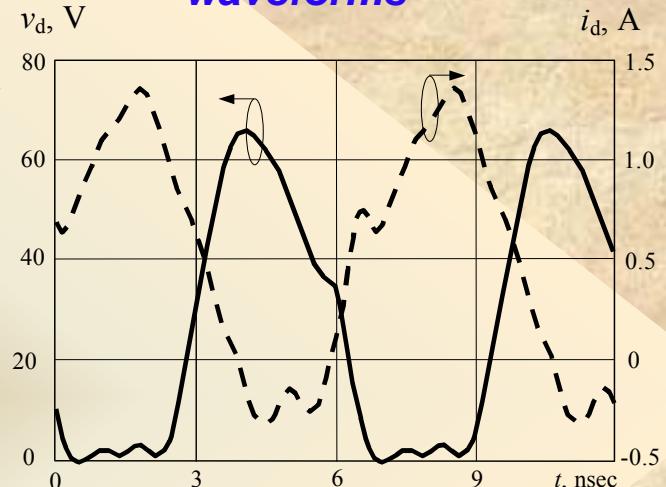

LDMOSFET:  
gate length 1.25 um  
gate width 7x1.44 mm

1 - drain efficiency > 71%

2 - power gain > 9.5 dB


Input power - 1 W

Input VSWR < 1.4

Gain flatness  $\leq \pm 0.3$

## 4.8. Practical high efficiency RF and microwave power amplifiers
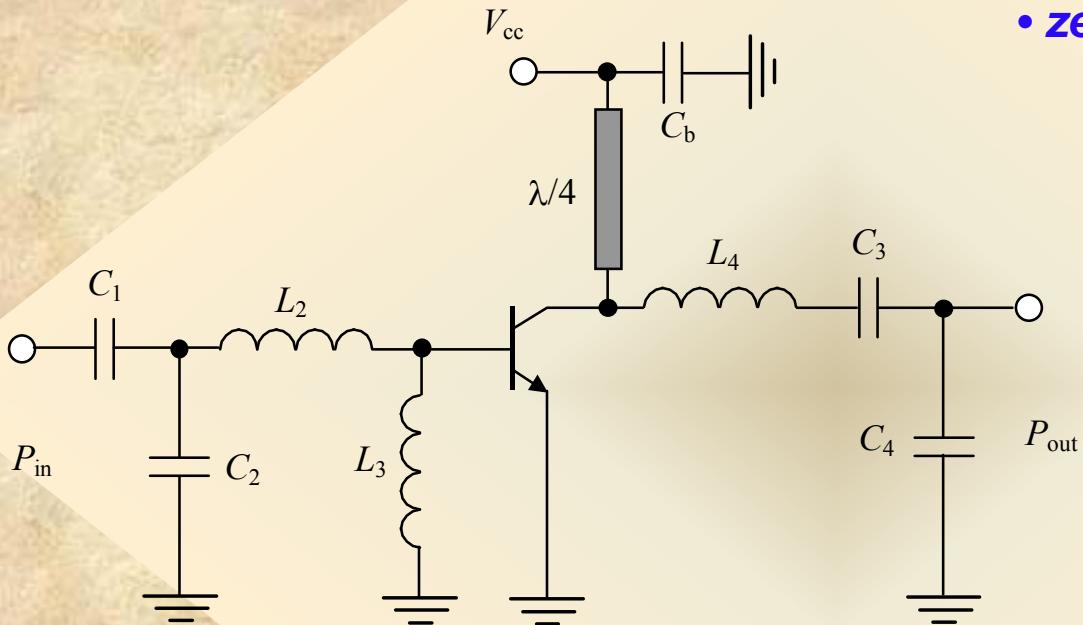
### Typical bipolar RF Class F power amplifier




- zero-volt Class C biasing using RF choke
- T-type input and output matching circuits with parallel capacitance
- quarterwave transmission line in collector to suppress even harmonics
- high-Q series LC circuit to provide high impedance conditions for harmonics

Up to 90% collector efficiency for 10 W at 250 MHz

## 4.8. Practical high efficiency RF and microwave power amplifiers
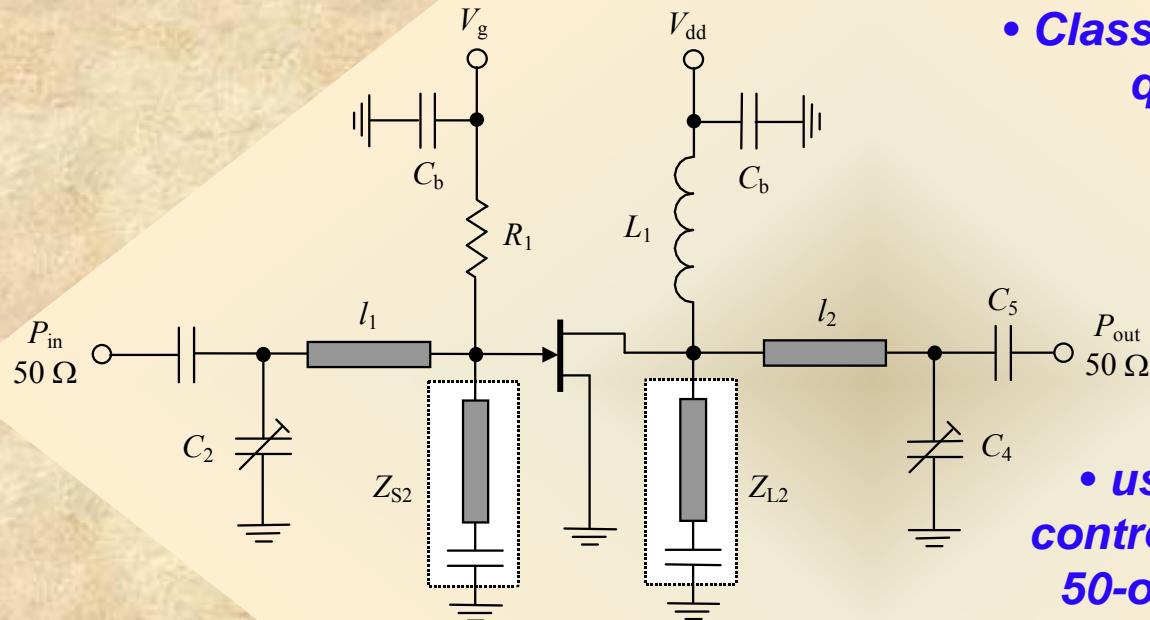
### Harmonic controlled MESFET microwave Class F power amplifier




- Class AB biasing with small quiescent current
- T-type input and output matching circuits with parallel capacitance
- using second harmonic controlled circuits with series 50-ohm microstrip line and capacitance each at device input and output

*Input second-harmonic termination circuit is required to provide input quasi-square voltage waveform minimizing device switching time*

**74% power-added efficiency for 1.4 W at 930 MHz**

## 4.8. Practical high efficiency RF and microwave power amplifiers
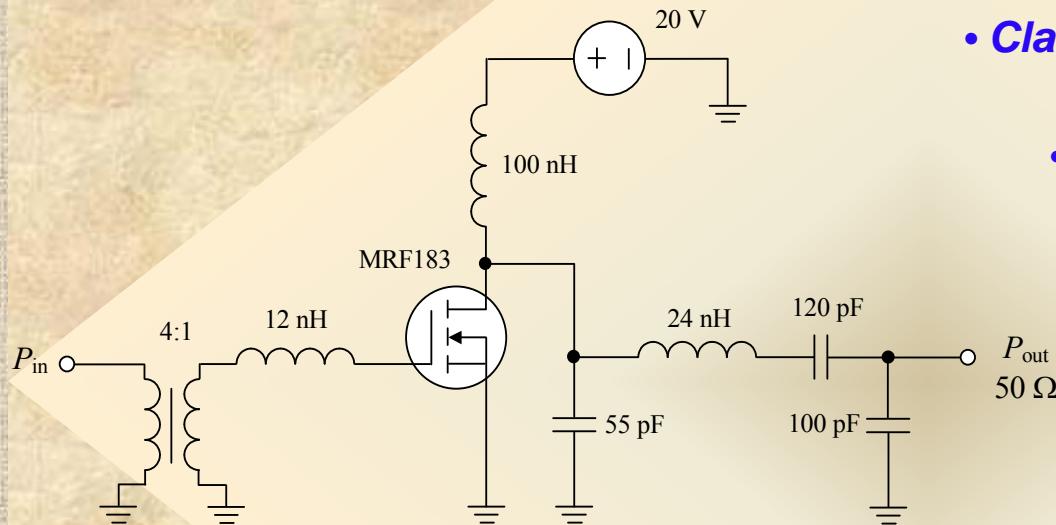
### High power LDMOSFET RF Class E power amplifier



- quality factor of resonant circuit was chosen to be sufficiently low (~ 5) to provide some frequency bandwidth operation and to reduce sensitivity to resonant circuit parameters


- Class B with zero quiescent current
- series inductance and ferrite 4:1 transformer is required to match device input impedance
- L-type output transformer to match optimum 1.5-ohm output impedance to 50-ohm load

- required value of Class E shunt capacitance is provided by device intrinsic 38-pF capacitance and external 55-pF capacitance

70% drain efficiency for 54 W at 144 MHz

## 4.8. Practical high efficiency RF and microwave power amplifiers
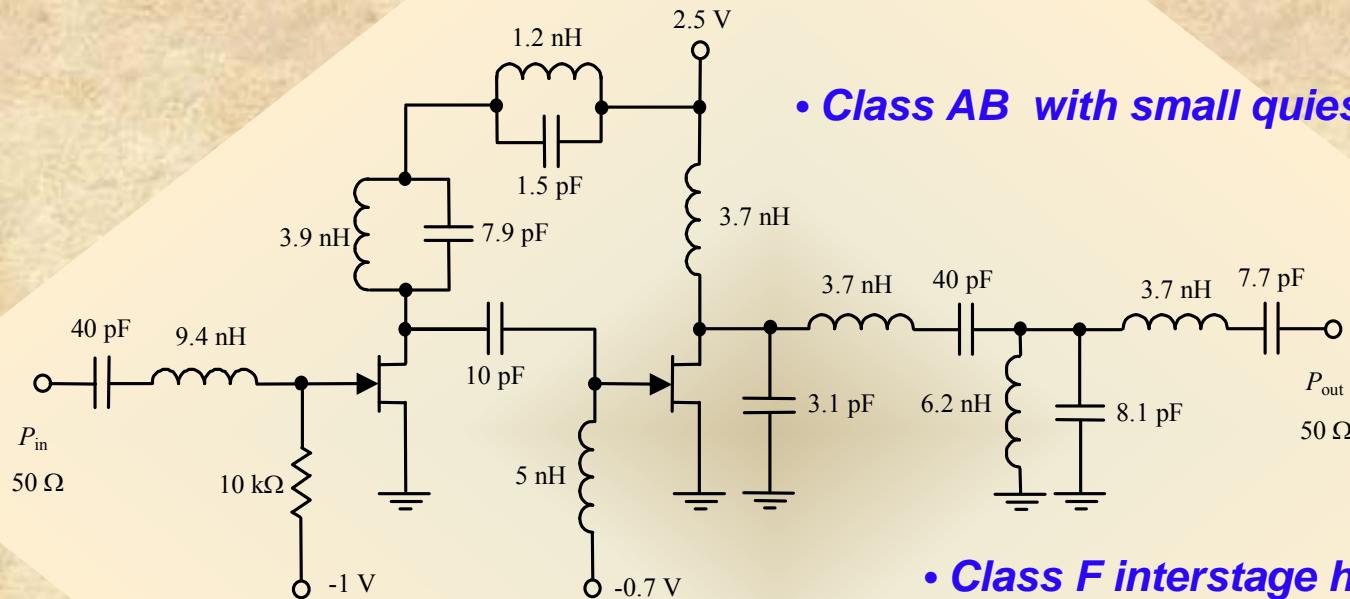
### Low voltage fully integrated MESFET Class E power amplifier



- Class E load network with optimum series inductance and shunt capacitance
  - T-type output matching circuit for impedance transformation to 50-ohm load

• Class AB with small quiescent current



• Class F interstage harmonic controlled circuit using two LC resonant circuits tuned on fundamental and third harmonic to approximate square-wave driving signal

50% power-added efficiency for 24 dBm within 800-870 MHz


## 4.8. Practical high efficiency RF and microwave power amplifiers

### 225-400 MHz 28 V 20 W LDMOSFET Class AB power amplifier: simulations

#### Stability

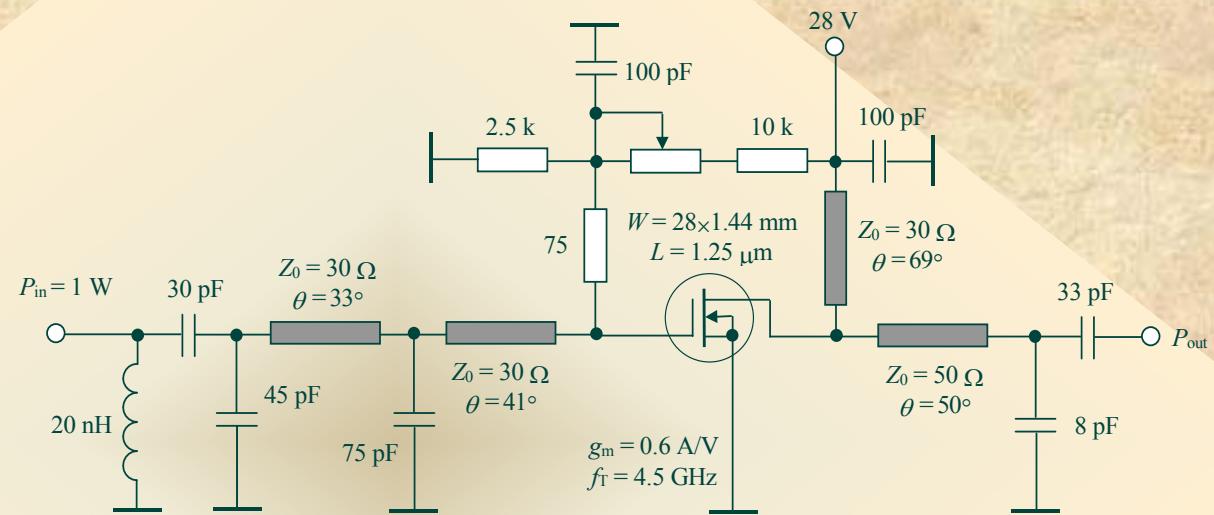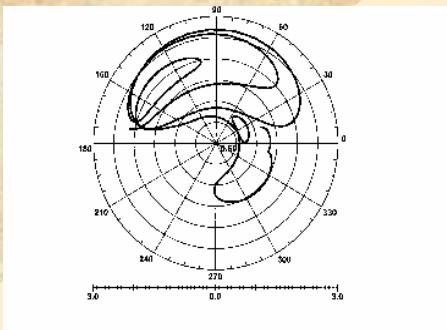

#### Power gain

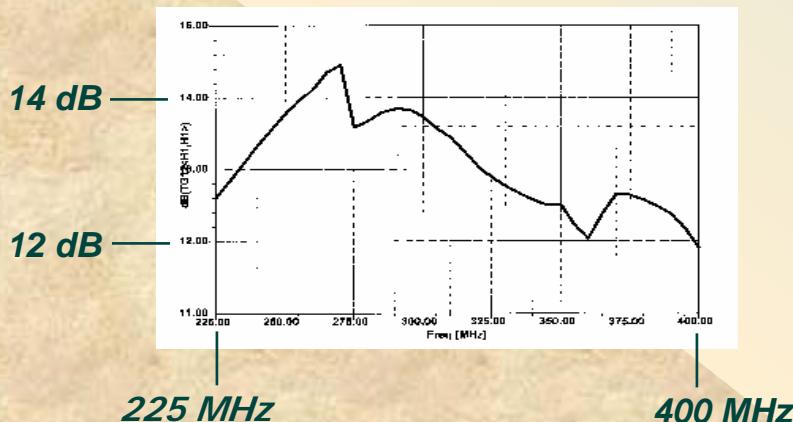

#### Power-added efficiency

