

## ***LECTURE 2. IMPEDANCE MATCHING***

***2.1. Main principles***

***(conjugate matching, maximum delivered power)***

***2.2. Smith chart***

***2.3. Matching with lumped elements***

***2.4. Matching with transmission lines***



***2.5. Determination of active device  
impedances***

***2.6. Types of transmission lines***

***(coaxial line, stripline, microstrip line, slotline,  
coplanar waveguide)***

## 2.1. Main principles

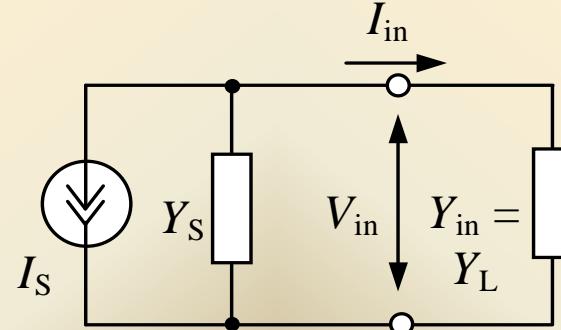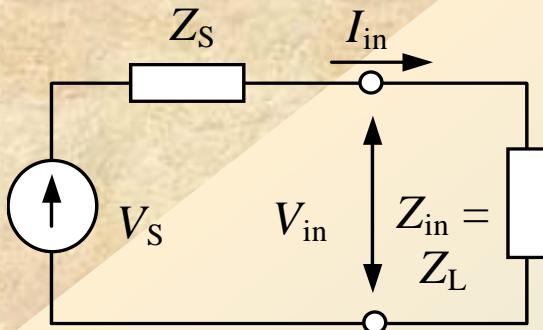**Impedance matching is necessary to provide maximum delivery of RF power to load from source**



$$Z_S = R_S + jX_S - \text{source impedance}$$

$$Z_L = R_L + jX_L - \text{load impedance}$$

$$P = \frac{1}{2} V_{in}^2 \operatorname{Re}\left(\frac{1}{Z_L}\right) = \frac{1}{2} V_S^2 \left| \frac{Z_L}{Z_S + Z_L} \right|^2 \operatorname{Re}\left(\frac{1}{Z_L}\right) \quad - \text{power delivered to load}$$



(substitution of real and imaginary parts of source and load impedances)

$$P = \frac{1}{2} V_S^2 \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$

- power delivered to load as function of circuit parameters

## 2.1. Main principles

For fixed source impedance  $Z_S$ ,  
to maximize output power

$$\frac{\partial P}{\partial R_L} = 0 \quad \frac{\partial P}{\partial X_L} = 0$$

$$P = \frac{1}{2} V_s^2 \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$

$$P = \frac{V_s^2}{8R_S}$$

- maximum power delivered to load

$$\begin{cases} R_S^2 - R_L^2 + (X_L + X_S)^2 = 0 \\ X_L(X_L + X_S) = 0. \end{cases}$$

$$\begin{cases} R_S = R_L \\ X_L = -X_S \end{cases} \quad \text{or} \quad Z_L = Z_S^*$$

- impedance conjugate matching conditions

$$\begin{cases} G_S = G_L \\ B_L = -B_S \end{cases} \quad \text{or} \quad Y_L = Y_S^*$$

- admittance conjugate matching conditions

$$W_L = W_S^*$$

- immitance conjugate matching conditions ( $Z$  or  $Y$ )

## 2.2. Smith chart

**Smith chart represents relationships between load impedance  $Z$  and reflection coefficient  $\Gamma$**

$$\frac{Z}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$$

**with real and imaginary parts of**

$$\frac{R}{Z_0} + j\frac{X}{Z_0} = \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i}$$



$$\frac{Z}{Z_0} = \frac{R}{Z_0} + j\frac{X}{Z_0} \quad \Gamma = \Gamma_r + j\Gamma_i$$

**Equating real and imaginary parts:**

$$\left(\Gamma_r - \frac{R}{R + Z_0}\right)^2 + \Gamma_i^2 = \left(\frac{Z_0}{R + Z_0}\right)^2$$

- **constant-( $R/Z_0$ ) circles: family of circles centered at points  $\Gamma_r = R/(R + Z_0)$  and  $\Gamma_i = 0$  with radii of  $Z_0/(R + Z_0)$**

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{Z_0}{X}\right)^2 = \left(\frac{Z_0}{X}\right)^2$$


- **constant-( $X/Z_0$ ) circles: family of circles centered at points  $\Gamma_r = 1$  and  $\Gamma_i = Z_0/X$  with radii of  $Z_0/X$**

**In admittance form:**


$$\left(\Gamma_r + \frac{G}{G + Y_0}\right)^2 + \Gamma_i^2 = \left(\frac{Y_0}{G + Y_0}\right)^2$$

$$(\Gamma_r + 1)^2 + \left(\Gamma_i + \frac{Y_0}{B}\right)^2 = \left(\frac{Y_0}{B}\right)^2$$

## 2.2. Smith chart

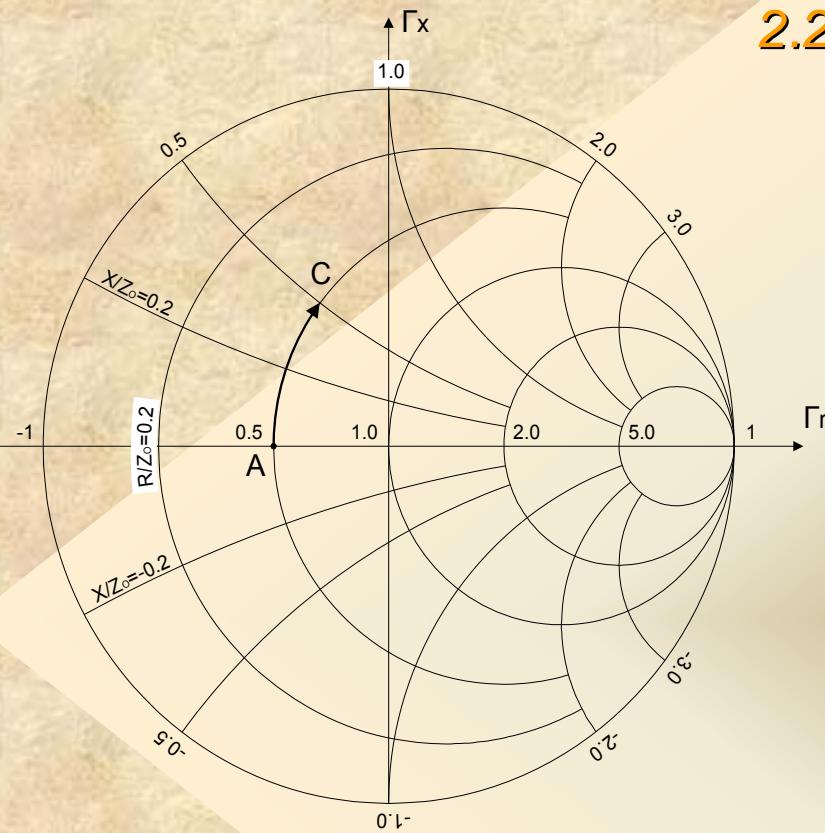


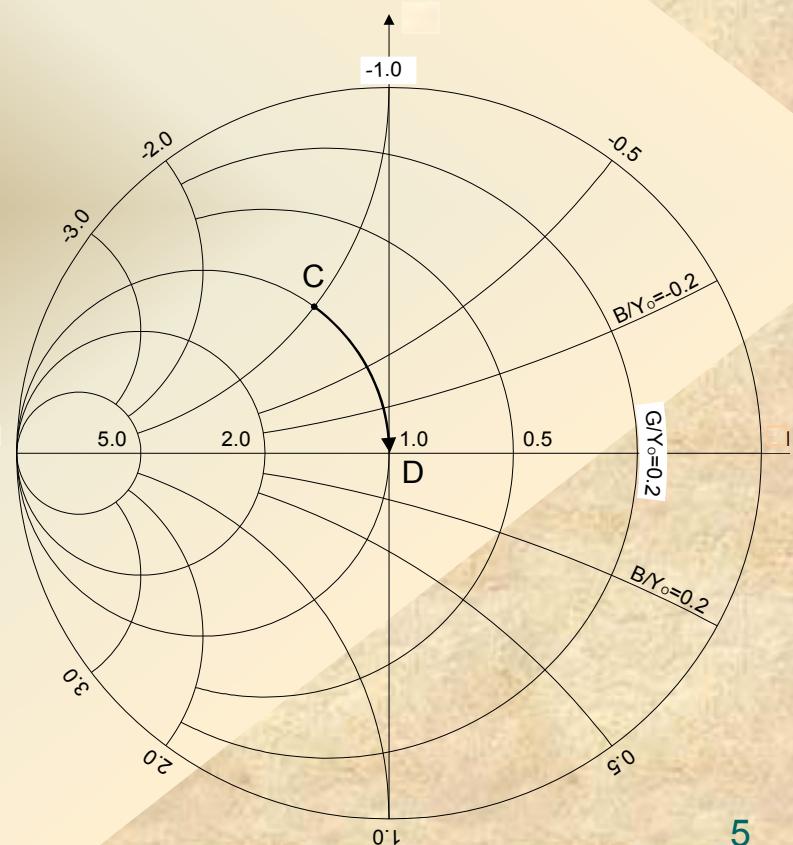At Z Smith chart, curve from point A to point C indicates impedance transformation from resistance  $25 \text{ Ohm}$  to inductive impedance  $(25 + j25) \text{ Ohm}$



At Y Smith chart, curve from point C to point D indicates admittance transformation from inductive admittance  $(20 - j20) \text{ mS}$  to conductance  $20 \text{ mS}$  ( $50 \text{ Ohm}$ )

## 2.2. Smith chart

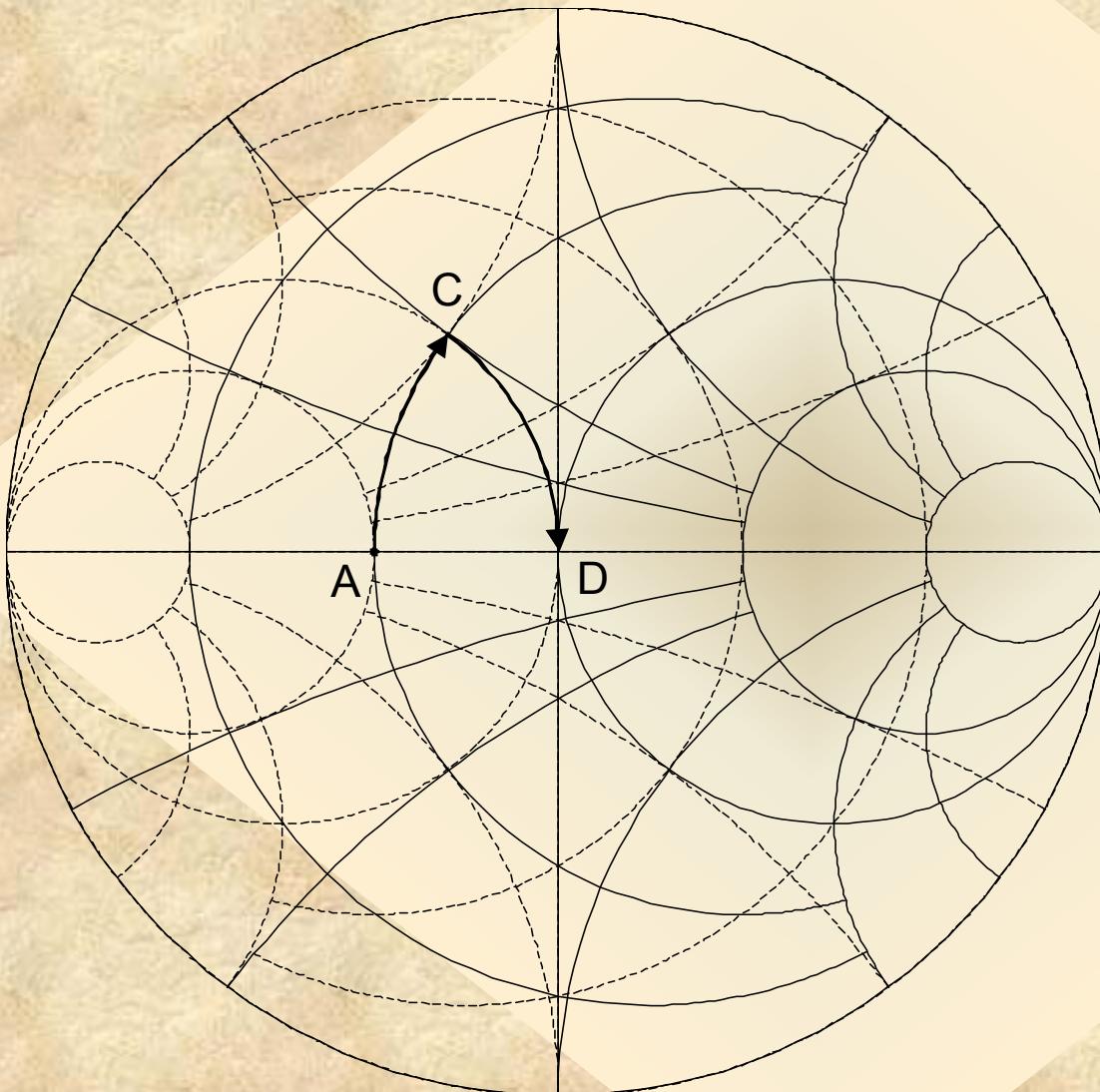


*At combined Z-Y  
Smith chart:*

*Z Smith chart  
provides  
transformation  
from point A to  
point C*


*Y Smith chart  
provides  
transformation  
from point C to  
point D*

## 2.3. Matching with lumped elements

*L-transformer*

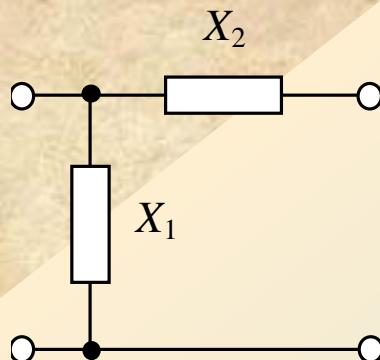

*Impedance parallel and series circuits*

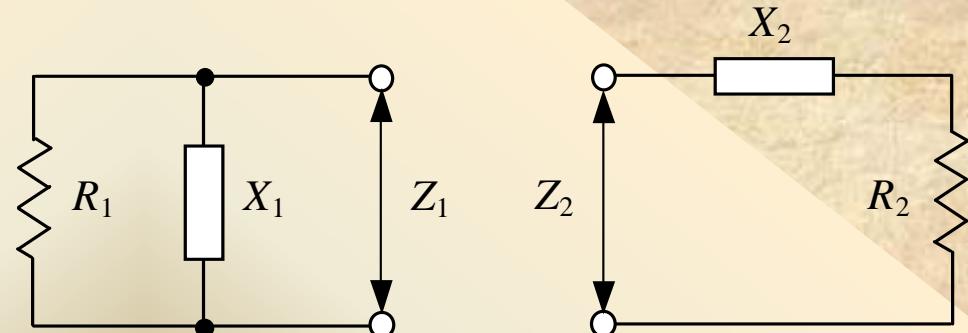

*Equivalence when  $Z_1 = Z_2$ :*

$$R_2 + jX_2 = \frac{R_1 X_1^2}{R_1^2 + X_1^2} + j \frac{R_1^2 X_1}{R_1^2 + X_1^2}$$



$$R_1 = R_2(1 + Q^2) \quad X_1 = X_2(1 + Q^{-2})$$


where  $Q = R_1 / |X_1| = |X_2| / R_2$

- quality factor equal for series and parallel circuits
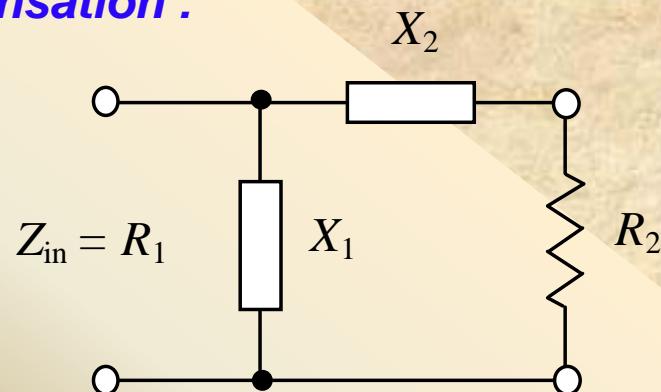
## 2.3. Matching with lumped elements

For conjugate matching with reactance compensation :

$$R_1 = R_2(1 + Q^2)$$
$$X_1 = -X_2(1 + Q^{-2})$$





Input impedance  $Z_{in}$  will be resistive and equal to  $R_1$ , when :

$$\begin{cases} |X_1| = R_1 / Q \\ |X_2| = R_2 Q \\ Q = \sqrt{R_1 / R_2 - 1}. \end{cases}$$

where  $Q = R_1 / |X_1| = |X_2| / R_2$   
- quality factor equal for series and parallel circuits

## 2.3. Matching with lumped elements

### Two L-type matching circuits

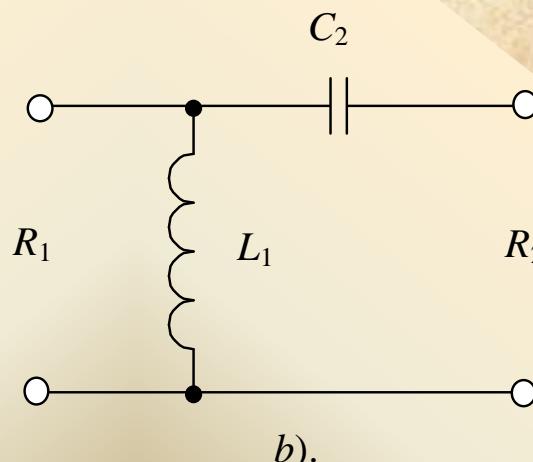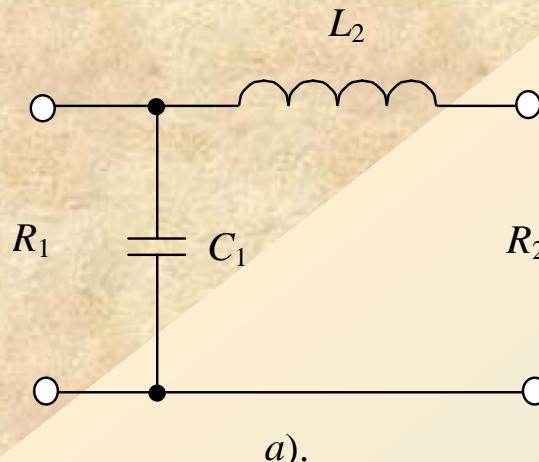


Resistance  $R_1$ , connected to parallel reactive element must be greater than resistance  $R_2$ , connected to series reactive element

$$\left. \begin{array}{l} \omega C_1 = Q / R_1 \\ \omega L_2 = Q R_2 \end{array} \right\} \quad Q = \sqrt{\frac{R_1}{R_2} - 1} \quad \left\{ \begin{array}{l} \omega L_1 = R_1 / Q \\ \omega C_2 = 1 / (Q R_2) \end{array} \right.$$
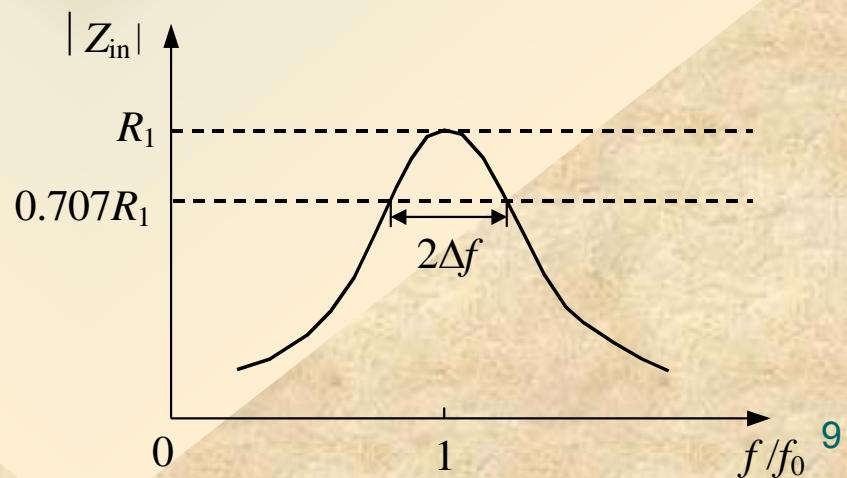
### Bandwidth properties


$$\left\{ \begin{array}{l} Q \cong f_0 / 2\Delta f_0 \\ F_n \cong Q^2 (n^2 - 1) \end{array} \right.$$

where  $F_n$  - out-of-band suppression factor  
 $n$  - harmonic number



## 2.3. Matching with lumped elements


### Connection of two L-transformers

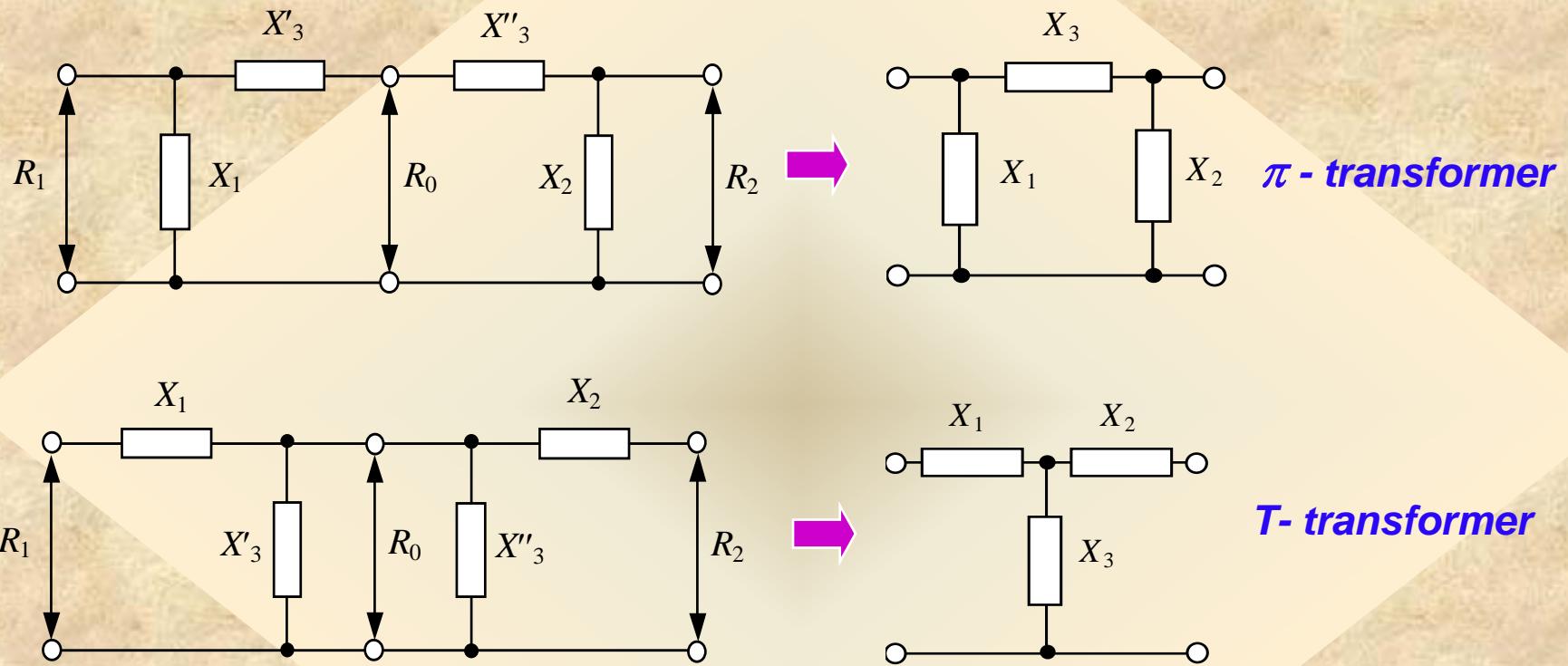

- for each L-transformer, resistances  $R_1$  and  $R_2$  are transformed to some intermediate resistance  $R_0$  with value of  $R_0 < (R_1, R_2)$
- for same resistances  $R_1$  and  $R_2$ , T- and π-transformers have better filtering properties, but narrower bandwidth compared with single L-transformer

## 2.3. Matching with lumped elements

### $\pi$ -type matching circuits

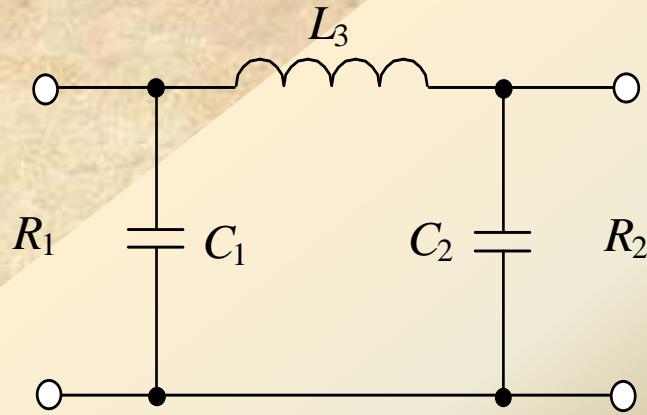

$$\omega C_1 = Q_1 / R_1 \quad \omega C_2 = Q_2 / R_2$$


$$\omega L_3 = R_1(Q_1 + Q_2)/(1 + Q_1^2)$$

$$Q_2 = \sqrt{\frac{R_2}{R_1}(1 + Q_1^2) - 1} \quad Q_1^2 > \frac{R_1}{R_2} - 1$$

- widely used as output matching circuit to provide Class B operation with sinusoidal collector voltage
- useful for interstage matching when active device input and output capacitances can be easily incorporated inside matching circuit
- provides significant level of harmonic suppression
  - with additional series LC-filter, can be directly applied to realize Class E mode with shunt capacitance

## 2.3. Matching with lumped elements


### $\pi$ -type matching circuits

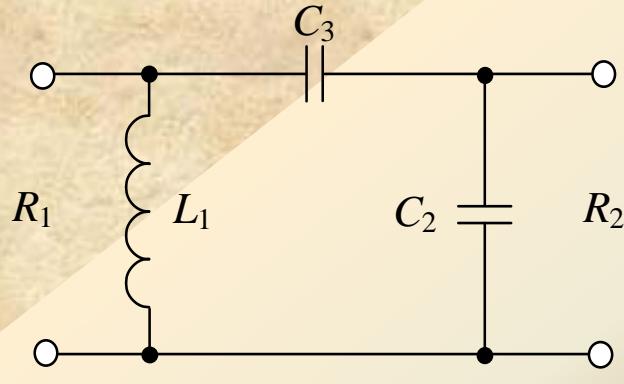

$$\omega L_1 = R_1 / Q_1 \quad \omega C_2 = Q_2 / R_2$$

$$\omega C_3 = (1 + Q_2^2) / [R_2(Q_1 - Q_2)]$$
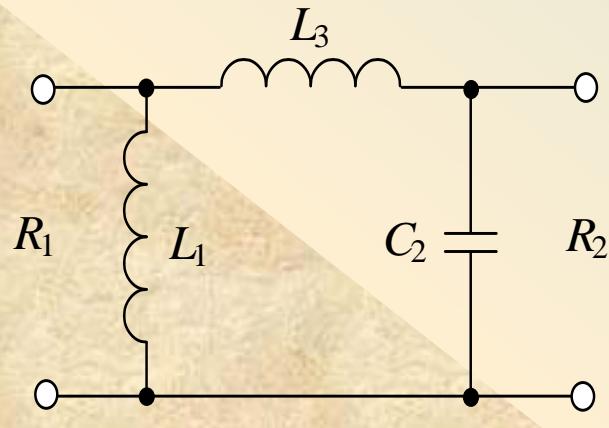
$$Q_2 = \sqrt{\frac{R_2}{R_1}(1 + Q_1^2) - 1} \quad Q_1^2 > \frac{R_1}{R_2} - 1$$




$$\omega L_1 = R_1 / Q_1 \quad \omega C_2 = Q_2 / R_2$$

$$\omega L_3 = R_2(Q_2 - Q_1) / (1 + Q_2^2),$$

$$Q_1 = \sqrt{\frac{R_1}{R_2}(1 + Q_2^2) - 1} \quad Q_2^2 > \frac{R_2}{R_1} - 1$$

## 2.3. Matching with lumped elements

### T-type matching circuits

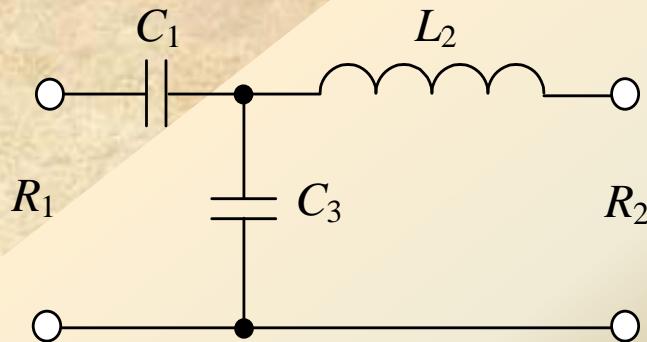

$$\omega C_1 = 1/(R_1 Q_1) \quad \omega L_2 = Q_2 R_2$$


$$\omega C_3 = (Q_2 - Q_1)/[R_2(1 + Q_2^2)]$$

$$Q_1 = \sqrt{\frac{R_2}{R_1}(1 + Q_2^2)} - 1 \quad Q_2^2 > \frac{R_1}{R_2} - 1$$

- widely used as input, interstage and output matching circuits in high power amplifiers
- can incorporate active device lead and bondwire inductances within matching circuit
- provides significant level of harmonic suppression
- can be directly applied to realize Class F mode providing high impedances at harmonics

## 2.3. Matching with lumped elements


### T-type matching circuits

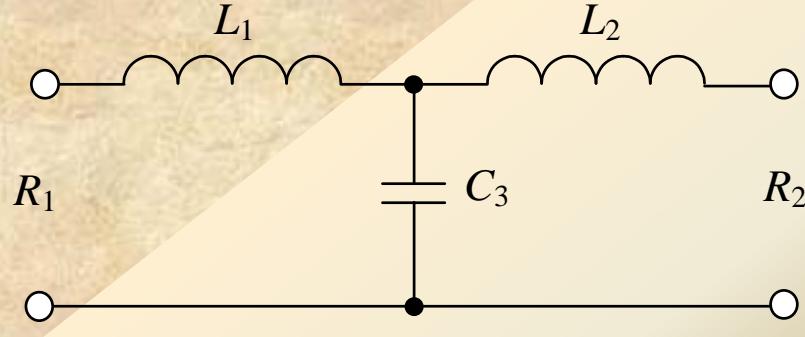

$$\omega L_1 = Q_1 R_1 \quad \omega L_2 = Q_2 R_2$$

$$\omega C_3 = (Q_1 + Q_2) / [R_2(1 + Q_2^2)]$$
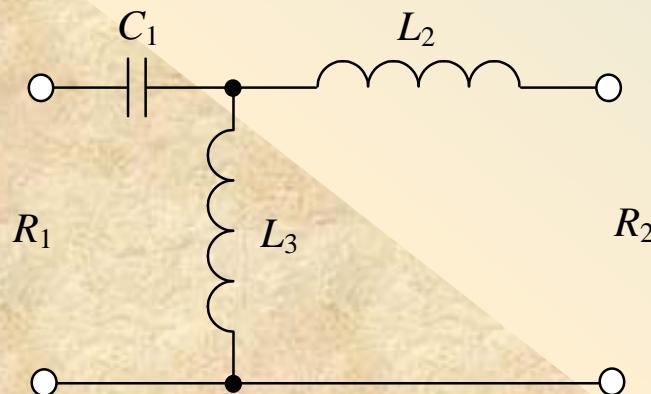
$$Q_1 = \sqrt{\frac{R_2}{R_1}(1 + Q_2^2) - 1} \quad Q_2^2 > \frac{R_1}{R_2} - 1$$




$$\omega C_1 = 1/(R_1 Q_1) \quad \omega L_2 = Q_2 R_2$$

$$\omega L_3 = R_2(1 + Q_2^2)/(Q_1 - Q_2),$$


$$Q_2 = \sqrt{\frac{R_1}{R_2}(1 + Q_1^2) - 1} \quad Q_1^2 > \frac{R_2}{R_1} - 1$$

## 2.3. Matching with lumped elements

### Matching design example

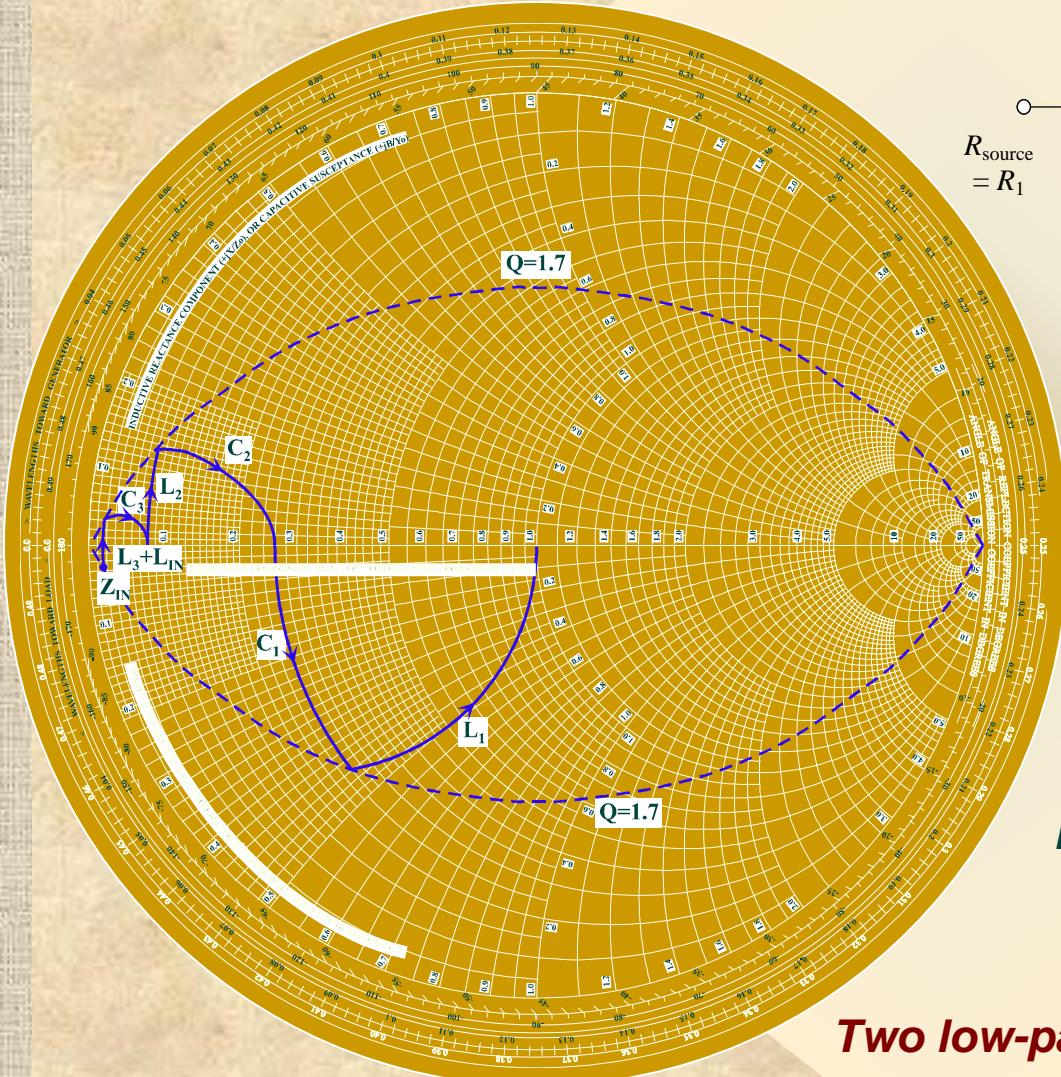

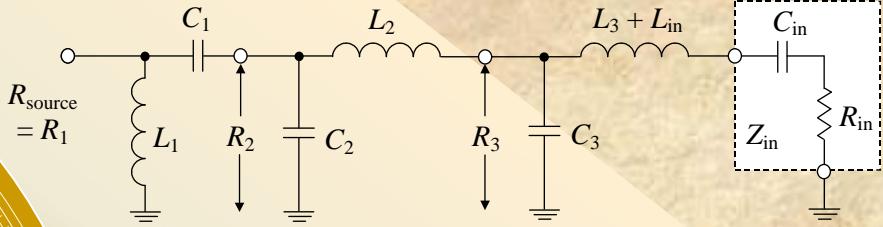**132-174 MHz 150 W MOSFET power amplifier:  
three-section input matching**



$$Z_{in} = (0.9 - j1.2) \Omega$$

$$f_c = \sqrt{132 \cdot 174} = 152 \text{ MHz}$$

$$Q = 152/(174 - 132) = 3.6$$


$$\frac{R_1}{R_2} = \frac{R_2}{R_3} = \frac{R_3}{R_{in}}$$

For  $R_{in} = 0.9 \text{ Ohm}$  and  $R_1 = 50 \text{ Ohm}$ :  
 $R_3 = 3.5 \text{ Ohm}$ ,  $R_2 = 13 \text{ Ohm}$   
 $Q = 1.7$

**Two low-pass and one high-pass L-sections**

## 2.4. Matching with transmission lines

### Transmission-line transformer

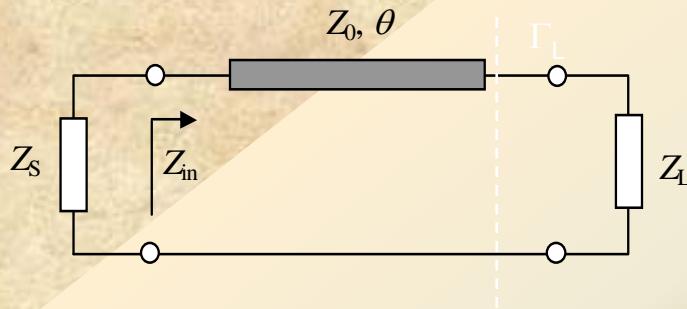

### Impedance at input of loaded transmission line:

$$\frac{Z_{in}}{Z_0} = \frac{1 + \Gamma_L \exp(-2j\theta)}{1 - \Gamma_L \exp(-2j\theta)}$$

*Input impedance for loaded transmission line with electrical length of  $\theta$ , normalized to its characteristic impedance  $Z_0$ , can be found by rotating this impedance point clockwise by  $2\theta$  around Smith chart center point with radius  $|\Gamma_L|$*

$$\frac{Z_L}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \rightarrow$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \theta}{Z_0 + jZ_L \tan \theta}$$



*For conjugate matching with reactance compensation when  $Z_S = Z_{in}^*$ :*

*For quarter-wave transmission line with  $\theta = 90^\circ$ :*

$$Z_{in} = Z_0^2 / Z_L$$

$$Z_0 = \sqrt{\frac{R_S(R_L^2 + X_L^2) - R_L(R_S^2 + X_S^2)}{R_L - R_S}}$$

$$\theta = \tan^{-1}\left(Z_0 \frac{R_S - R_L}{R_S X_L - X_S R_L}\right)$$

## 2.4. Matching with transmission lines

**For pure resistive source impedance  $Z_S = R_S$ :**

$$X_L Z_0 (1 - \tan^2 \theta) + (Z_0^2 - X_L^2 - R_L^2) \tan \theta = 0$$




**For electrical length  $\theta = 45^\circ$**

$$Z_0 = |Z_L| = \sqrt{R_L^2 + X_L^2}$$


$$R_S = R_L \frac{Z_0}{Z_0 - X_L}$$

**Any load impedance can be transformed into real source impedance using  $\lambda/8$ -transformer whose impedance is equal to magnitude of load impedance**

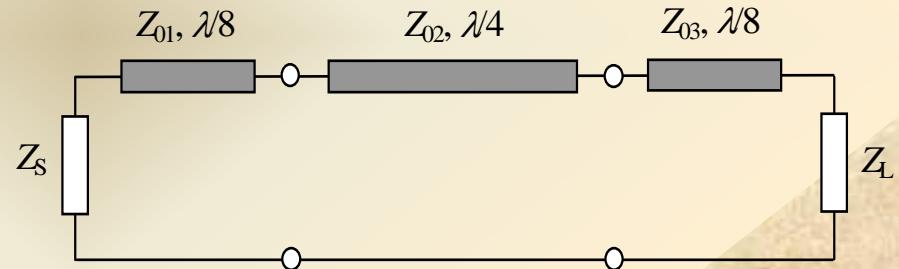**To match any source impedance  $Z_S$  and load impedance  $Z_L$ , matching circuit can be designed with two  $\lambda/8$ -transformers and one  $\lambda/4$ -transformer**





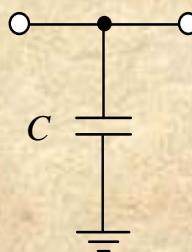**Lumped and transmission line single-frequency equivalence**




$\Leftrightarrow$

$$C = \frac{\tan \theta}{\omega Z_0}$$

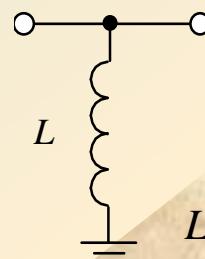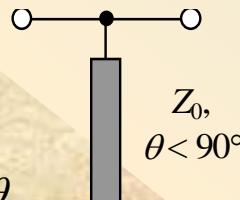


$\Leftrightarrow$

$$L = \frac{Z_0 \tan \theta}{\omega}$$

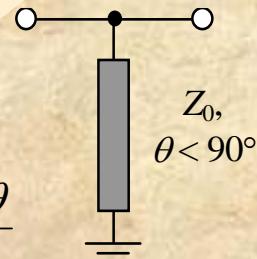

## 2.4. Matching with transmission lines

### L-type transformer

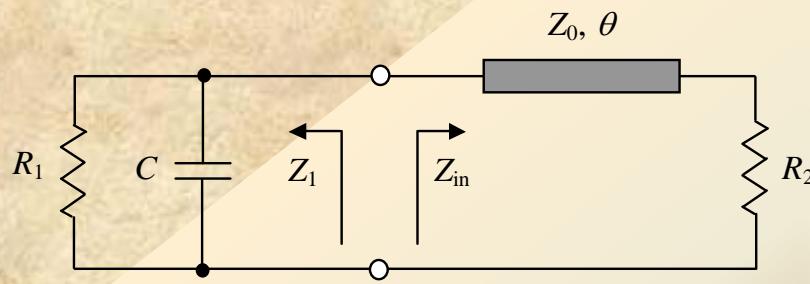

**Real and imaginary parts of**

$$Z_{\text{in}} = Z_0 \frac{R_2 + jZ_0 \tan \theta}{Z_0 + jR_2 \tan \theta}$$

**Matching for  
any ratio of  
 $R_1/R_2$**

$$R_{\text{in}} = Z_0^2 R_2 \frac{1 + \tan^2 \theta}{Z_0^2 + (R_2 \tan \theta)^2}$$

$$X_{\text{in}} = Z_0 \tan \theta \frac{Z_0^2 - R_2^2}{Z_0^2 + (R_2 \tan \theta)^2}$$

**Conjugate matching:**

$$R_{\text{in}} - jX_{\text{in}} = \frac{R_1 X_1^2}{R_1^2 + X_1^2} + j \frac{R_1^2 X_1}{R_1^2 + X_1^2}$$

$$R_1 = R_{\text{in}} (1 + Q^2)$$

$$X_1 = -X_{\text{in}} (1 + Q^{-2})$$

where  $X_1 = -1/\omega C$


$$C = Q / \omega R_1$$

$$\frac{R_1}{R_2} = \frac{1 + \left( \frac{Z_0}{R_2} - \frac{R_2}{Z_0} \right)^2 \sin^2 \theta \cos^2 \theta}{\cos^2 \theta + (R_2/Z_0)^2 \sin^2 \theta}$$


**Second implicit equation :  
numerical or graphical solution**

## 2.4. Matching with transmission lines

### Matching design example

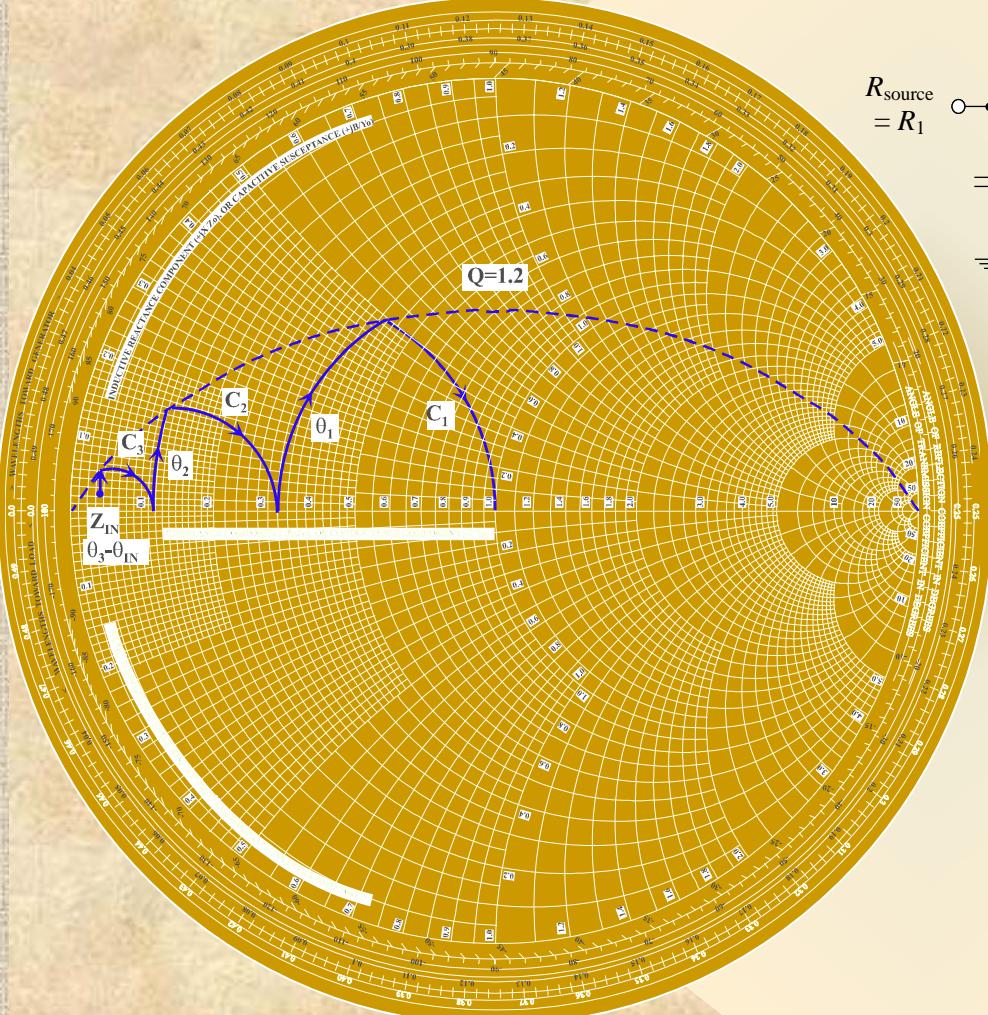

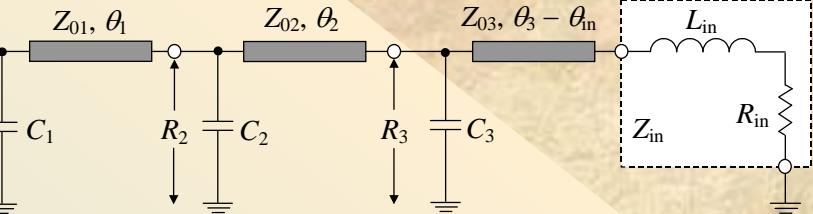**470-860 MHz 150 W LDMOSFET power amplifier:  
three-section input matching**



$$Z_{in} = (1.7 + j1.3) \Omega$$

$$f_c = \sqrt{470 \cdot 860} = 635 \text{ MHz}$$

$$Q = 635/(860 - 470) = 1.63$$

$$\frac{R_1}{R_2} = \frac{R_2}{R_3} = \frac{R_3}{R_{in}}$$

$$Q = 1.2$$

For  $R_{in} = 1.7 \text{ Ohm}$  and  $R_1 = 50 \text{ Ohm}$ :  
 $R_3 = 5.25 \text{ Ohm}$ ,  $R_2 = 16.2 \text{ Ohm}$

For  $Z_{01} = Z_{02} = Z_{03} = 50 \text{ Ohm} \Rightarrow$   
 $\theta_1 = 30^\circ$ ,  $\theta_2 = 7.5^\circ$ ,  $\theta_3 = 2.4^\circ$

For  $\theta_1 = \theta_2 = \theta_3 = 30^\circ \Rightarrow Z_{01} = 50 \text{ Ohm}$ ,  $Z_{02} = 15.7 \text{ Ohm}$ ,  $Z_{03} = 5.1 \text{ Ohm}$

## 2.5. Determination of active device impedances

### Analytical evaluation

**Output resistance in Class B :**  $R_{\text{out}}^{(\text{B})} = \frac{(V_{\text{cc}} - V_{\text{sat}})^2}{2P_{\text{out}}}$

where  $V_{\text{sat}}$  is defined from load line analysis

**Output capacitance :**

$$C_{\text{out}} = C_c \quad \text{- bipolar device}$$


$$C_{\text{out}} = C_{\text{ds}} + C_{\text{gd}} \quad \text{- FET device}$$

### Large-signal collector capacitance

$$C_c = C_{\text{co}} / \left(1 + \frac{v_c}{\varphi}\right)^\gamma \quad \text{- junction capacitance}$$

$$v_c = E_c + V_c \sin \omega t \Rightarrow i_c = C_c(v_c) \frac{dv_c}{dt}$$

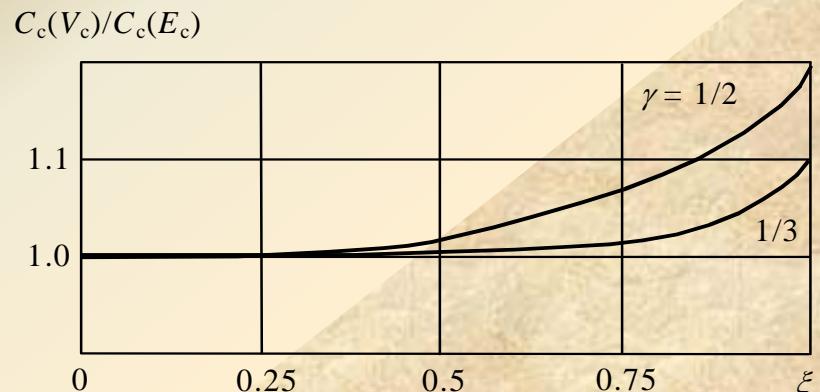
$$C_{c1} = \frac{I_{c1}}{\omega V_c} = \frac{C_c(E_c)}{\pi} \int_0^{2\pi} \frac{\cos^2 \omega t}{(1 + \xi \sin \omega t)^\gamma} d(\omega t)$$



where  $\xi = V_c / (E_c + \varphi)$

## 2.5. Determination of active device impedances

### S-parameter measurements

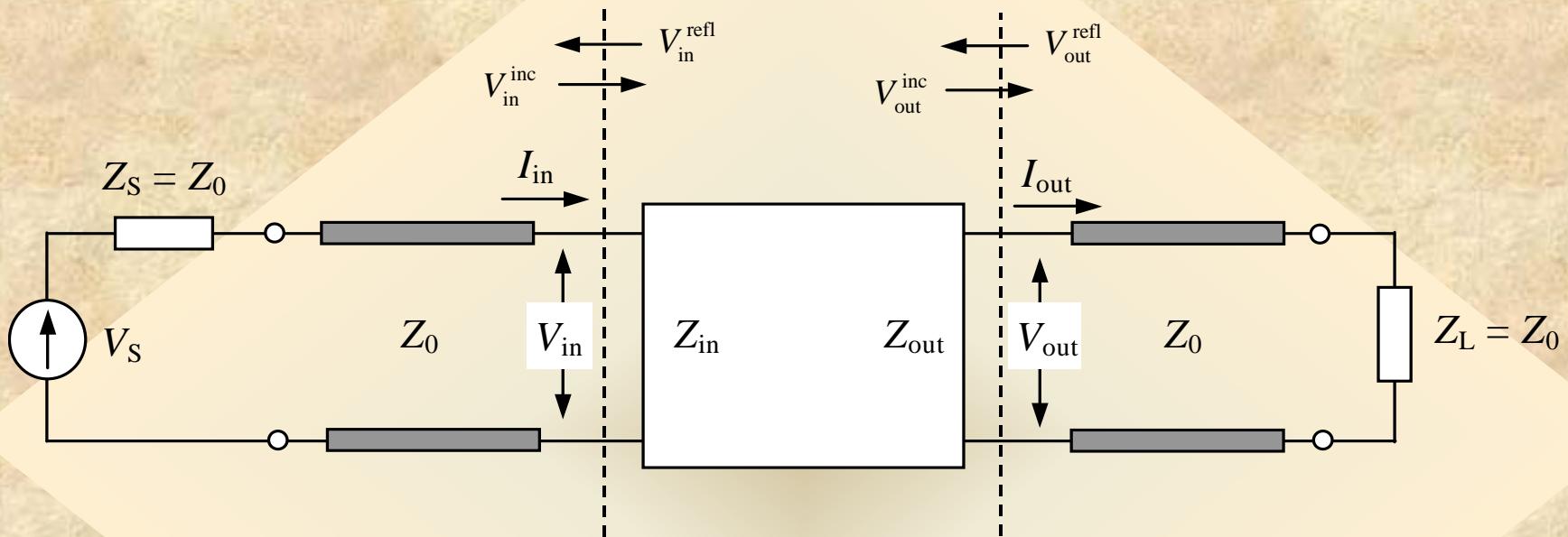

$$Z_{in} = \frac{V_{in}}{I_{in}} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}$$

where  $\Gamma_{in} = \frac{V_{in}^{refl}}{V_{in}^{inc}}$


$$Z_{out} = \frac{V_{out}}{I_{out}} = Z_0 \frac{1 + \Gamma_{out}}{1 - \Gamma_{out}}$$

where  $\Gamma_{out} = \frac{V_{out}^{refl}}{V_{out}^{inc}}$

**To define  $Z_{out}$ , source with nominal power is placed instead of load, and load becomes source**

## 2.5. Determination of active device impedances

### Power measurements

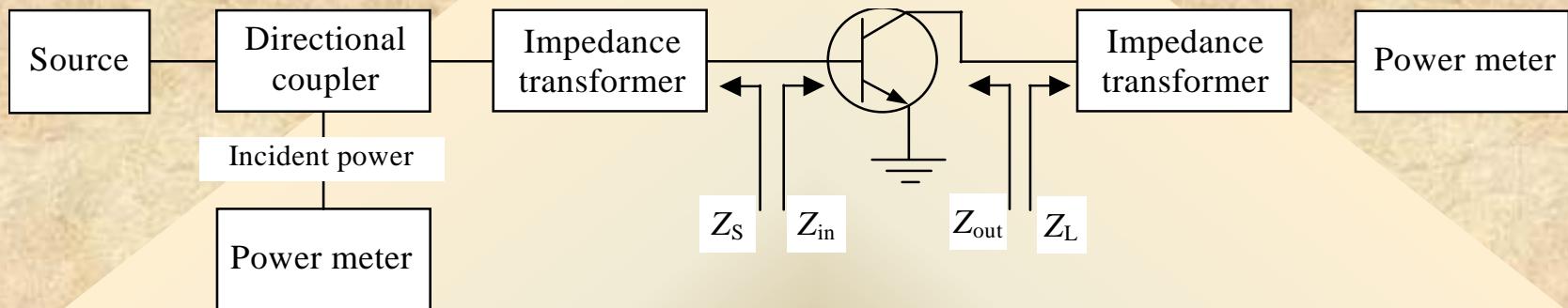


- *tune input impedance transformer to maximize incident power, i.e., power delivery from source to active device*
- *tune output impedance transformer to maximize output power delivered to load*
- *measure transformer impedances seen from the active device input and output, i.e.,  $Z_S$  and  $Z_L$*
- *calculate input and output active device impedances according to*

$$Z_{in} = Z_S^* \quad Z_{out} = Z_L^*$$

## 2.6. Types of transmission lines

### Coaxial line

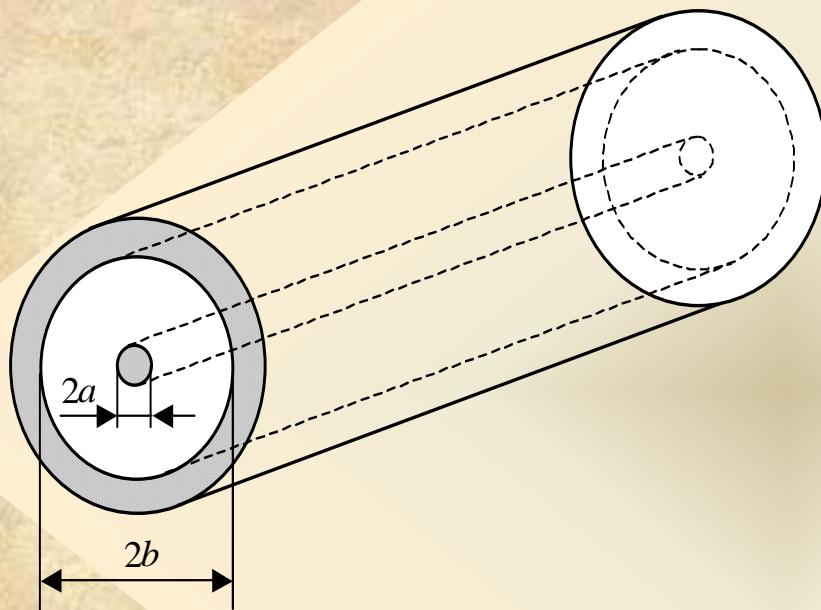

where  $\eta = \sqrt{\mu / \epsilon}$

Main wave type for coaxial line - transverse electromagnetic TEM wave

$$Z_0 = \frac{\eta}{2\pi} \ln\left(\frac{b}{a}\right)$$


- characteristic impedance

- wave impedance of lossless line equal to intrinsic medium impedance

- widely used for hybrid high power applications: combiners, dividers, transformers

## 2.6. Types of transmission lines

### Stripline

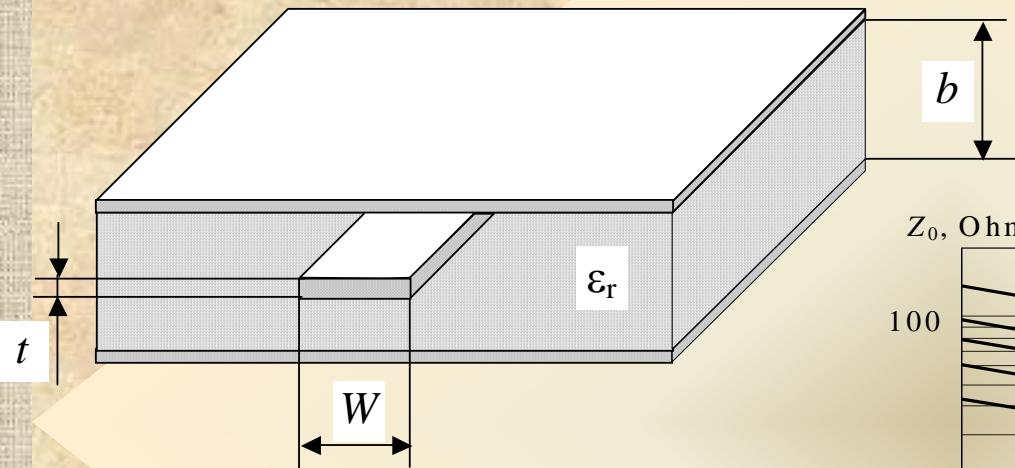


$$Z_0 = \frac{30\pi}{\sqrt{\epsilon_r}} \frac{b}{W_e + 0.441b}$$

- characteristic impedance

$$\frac{W_e}{b} = \frac{W}{b} - \begin{cases} 0 & \text{for } \frac{W}{b} > 0.35b \\ \left(0.35 - \frac{W}{b}\right)^2 & \text{for } \frac{W}{b} \leq 0.35b. \end{cases}$$

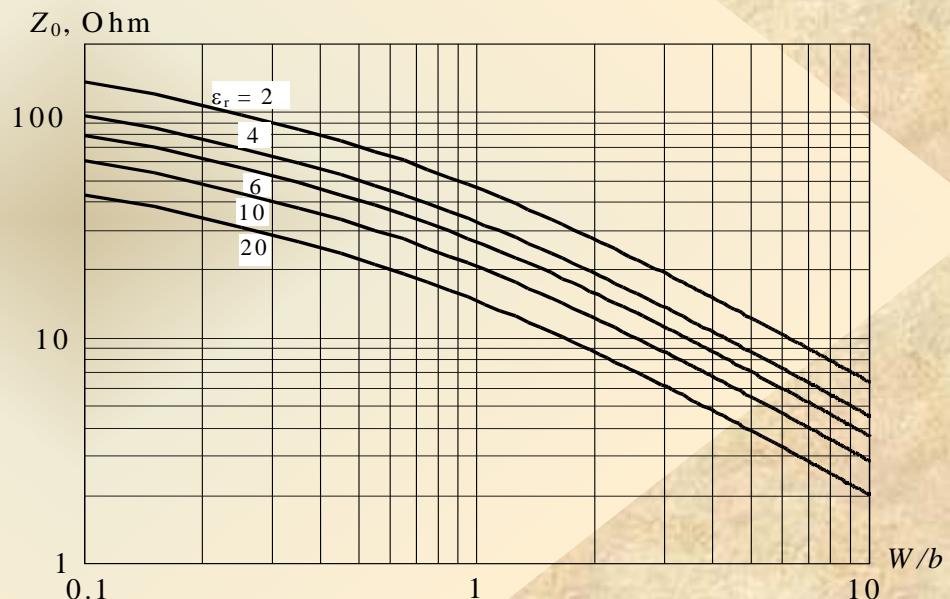
Main wave type for stripline - transverse electromagnetic TEM wave



- provides lower characteristic impedance


## 2.6. Types of transmission lines

### Microstrip line

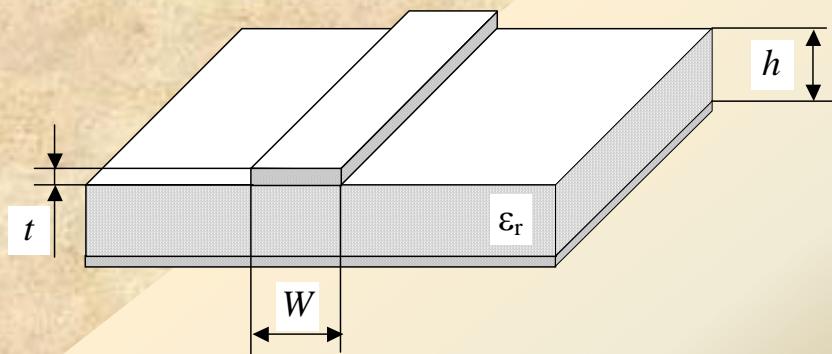


$$Z_0 = \frac{120\pi}{\sqrt{\epsilon_r}} \frac{h}{W} \frac{1}{1 + 1.735\epsilon_r^{-0.0724}(W/h)^{-0.836}}$$

- characteristic impedance

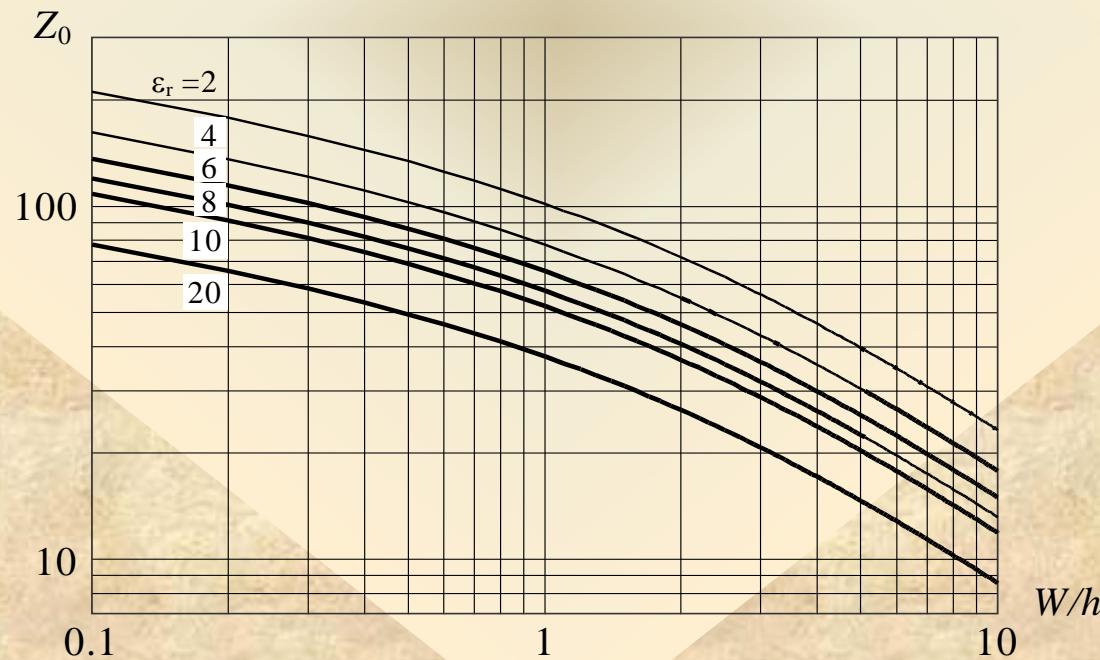


## 2.6. Types of transmission lines


**Slotline**

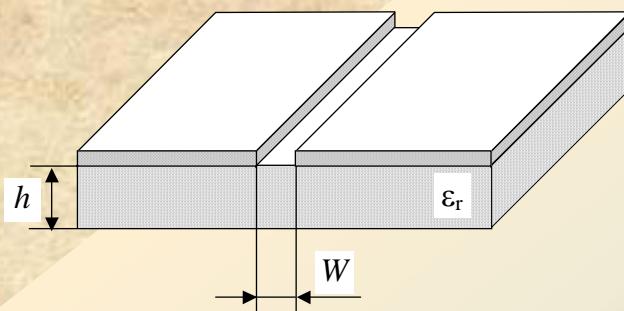

**Coplanar waveguide**

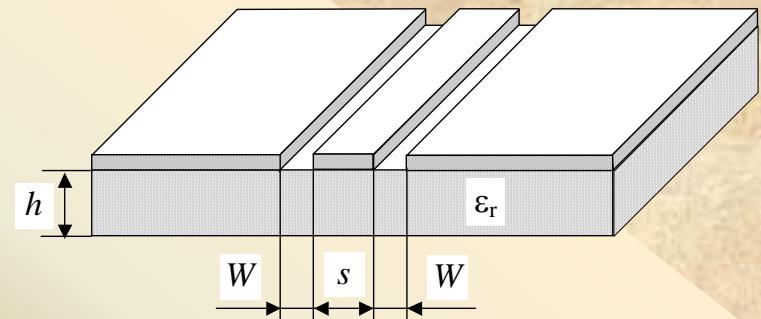

**Characteristic impedance**

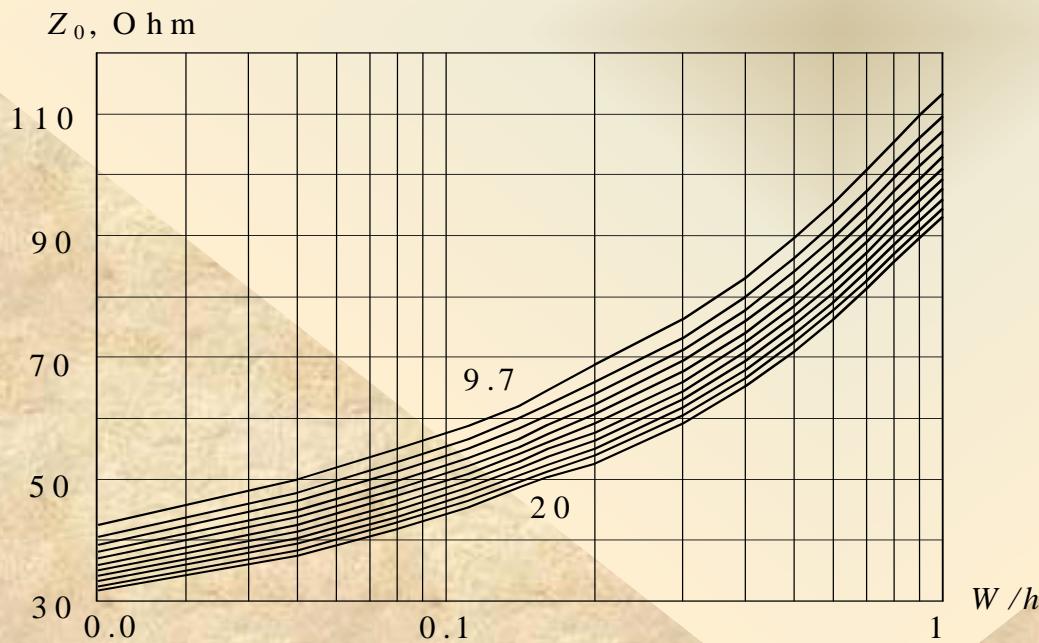

- provide higher characteristic impedance

- widely used for hybrid and monolithic integrated circuits