

## Problem Set 10 Solutions

E10.1 The key idea is to realize that both  $V_1$  and  $V_2$  can be obtained through voltage dividers:

$$\begin{aligned}\hat{V}_1 - \hat{V}_2 &= V \left[ \frac{R}{R+j\omega L} - \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right] \\ &= V \left[ \frac{R}{R+j\omega L} - \frac{1}{1+j\omega RC} \right] \\ &= V \frac{R + j\omega R^2 C - R - j\omega L}{(R + j\omega L)(1 + j\omega RC)}\end{aligned}$$

$$\hat{V}_1 - \hat{V}_2 = 0 \Rightarrow j\omega R^2 C - j\omega L = 0$$

$$j\omega R^2 C = j\omega L$$

$L = R^2 C$

E10.2 At low frequency:



At high frequency:



(a) LPF: For low freq.,  $V_o = V_i$ . For high freq.,  $V_o \approx 0V$ .

(b) HPF: For low freq.,  $V_o \approx 0V$ . For high freq.,  $V_o$  is divided down version of  $V_i$ .


(c) BSF: The LC network is open circuit at low and high freq. At  $\omega = \frac{1}{\sqrt{LC}}$ ,  $Z = 0$  which is a short, Hence close to  $\omega$ ,  $V_o$  is attenuated.

(d) BSF: The LC network is short circuit at low and high freq. at  $\omega = \frac{1}{\sqrt{LC}}$ ,  $Z = \infty$  which is an open. Hence,  $V_o$  is again attenuated close to  $\omega$ .

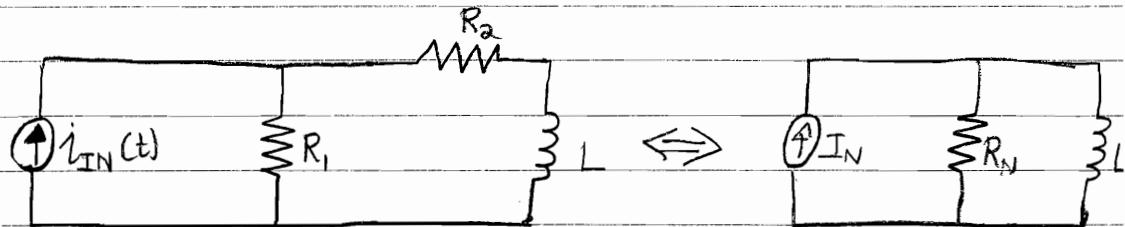Problem Set 10 Solutions

P10.1 (A)  $V_{out}(t) = i_L(t) R_2$

The current through  $L$  is the same as that through  $R_2$ . Therefore, to find  $i_L$  re-draw the circuit as follows:



$$I_N = \frac{R_1}{R_1 + R_2} i_{in}(t) \quad R_N = R_1 + R_2$$

$$I_N = \frac{V_L(t)}{R_N} + i_L(t)$$

$$I_N = \frac{L}{R_N} \frac{d i_L(t)}{dt} + i_L(t)$$

$$I_N R_2 = \frac{L}{R_N} \cdot \frac{d V_{out}(t)}{dt} + V_{out}(t)$$

$$\frac{R_1 R_2}{R_1 + R_2} i_{in}(t) = \frac{L}{R_1 + R_2} \frac{d V_{out}(t)}{dt} + V_{out}(t)$$

$$(B) \quad \frac{R_1 R_2}{R_1 + R_2} I_{in} e^{j\omega t} = \frac{L}{R_1 + R_2} \frac{d(\hat{V}_{out} e^{j\omega t})}{dt} + \hat{V}_{out} e^{j\omega t}$$

$$\frac{R_1 R_2}{R_1 + R_2} I_{in} e^{j\omega t} = \frac{L}{R_1 + R_2} e^{j\omega t} (j\omega \hat{V}_{out}) + \hat{V}_{out} e^{j\omega t}$$

$$\hat{V}_{out} \left( 1 + j\omega \frac{L}{R_1 + R_2} \right) = \frac{R_1 R_2}{R_1 + R_2} I_{in}$$

$$\hat{V}_{out} = \frac{\frac{R_1 R_2}{R_1 + R_2} I_{in}}{1 + j\omega \frac{L}{R_1 + R_2}}$$

$$\hat{V}_{out} = \frac{R_1 R_2}{R_1 + R_2 + j\omega L} I_{in}$$

Problem Set 10 Solutions

P.10.1 (C)

$$\hat{V}_{\text{out}} = \frac{R_1 R_2 (R_1 + R_2 - j\omega L)}{(R_1 + R_2)^2 + \omega^2 L^2} I_{\text{in}}$$

$$= \frac{R_1 R_2}{(R_1 + R_2)^2 + \omega^2 L^2} \sqrt{(R_1 + R_2)^2 + \omega^2 L^2} e^{-j \tan^{-1} \left[ \frac{\omega L}{R_1 + R_2} \right]} \cdot I_{\text{in}}$$

$$V_{\text{out}}(t) = \text{Re} \{ \hat{V}_{\text{out}} e^{j\omega t} \} = \text{Re} \{ | \hat{V}_{\text{out}} | e^{j \angle \hat{V}_{\text{out}}} e^{j\omega t} \}$$

$$= \text{Re} \{ | \hat{V}_{\text{out}} | e^{j(\omega t + \angle \hat{V}_{\text{out}})} \}$$

$$| \hat{V}_{\text{out}} | = \frac{R_1 R_2}{\sqrt{(R_1 + R_2)^2 + \omega^2 L^2}} I_{\text{in}} \quad \angle \hat{V}_{\text{out}} = -\tan^{-1} \left( \frac{\omega L}{R_1 + R_2} \right)$$

$$\text{Therefore, } V_{\text{out}}(t) = | \hat{V}_{\text{out}} | \cos(\omega t + \angle \hat{V}_{\text{out}})$$

$$V_{\text{out}} = | \hat{V}_{\text{out}} | = \frac{R_1 R_2}{\sqrt{(R_1 + R_2)^2 + \omega^2 L^2}} I_{\text{in}}$$

$$\phi = \angle \hat{V}_{\text{out}} = -\tan^{-1} \left( \frac{\omega L}{R_1 + R_2} \right)$$

(1)

$$\frac{V_{\text{out}}}{I_{\text{in}}} = \frac{R_1 R_2}{\sqrt{(R_1 + R_2)^2 + \omega^2 L^2}}$$

$$= \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{\sqrt{1 + \left( \frac{\omega}{\omega_c} \right)^2}}$$

$$\omega_c = \frac{R_1 + R_2}{L}$$

$$\phi = -\tan^{-1} \left( \frac{\omega L}{R_1 + R_2} \right) = -\tan^{-1} \left( \frac{\omega}{\omega_c} \right)$$


$$\omega \ll \omega_c \quad \frac{V_{\text{out}}}{I_{\text{in}}} \rightarrow \frac{R_1 R_2}{R_1 + R_2} \quad \phi \rightarrow 0$$

$$\omega = \omega_c \quad \frac{V_{\text{out}}}{I_{\text{in}}} = \frac{1}{\sqrt{2}} \frac{R_1 R_2}{R_1 + R_2} \quad \phi = -\frac{\pi}{4}$$

$$\omega \gg \omega_c \quad \frac{V_{\text{out}}}{I_{\text{in}}} \rightarrow \frac{R_1 R_2}{\omega L} \quad \phi \rightarrow -\frac{\pi}{2}$$


Problem Set 10 Solutions

P.10.1 (D) Continued

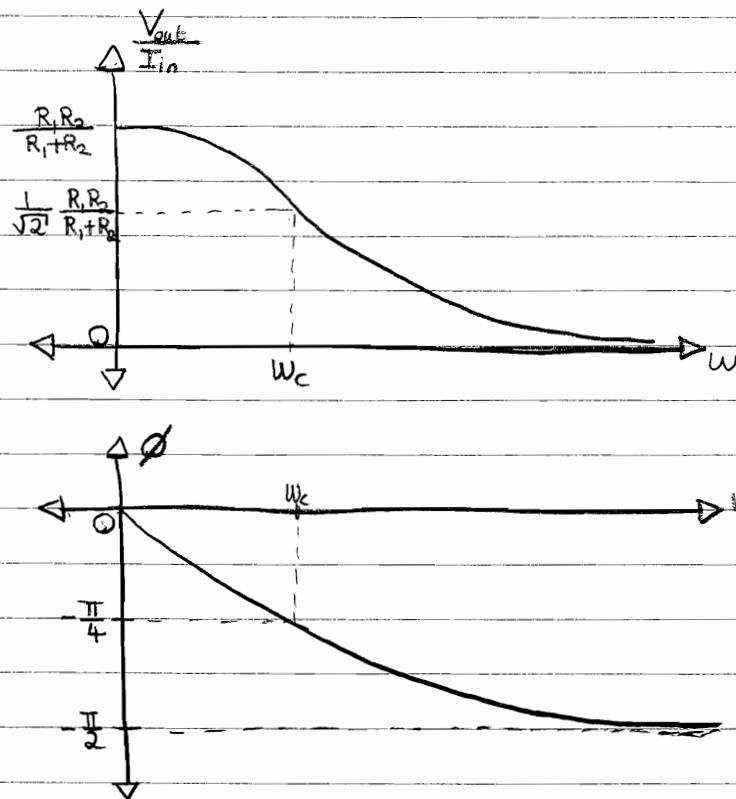

P.10.2


(A)

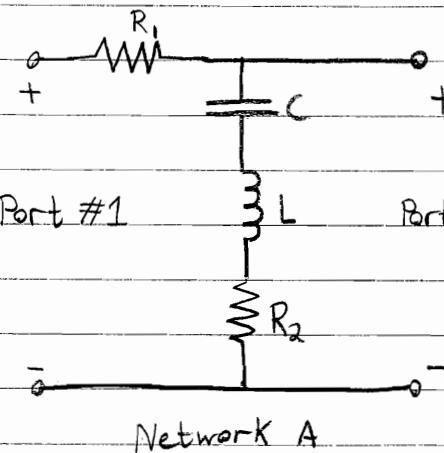

$$Z_{in,A} = R_1 + \frac{1}{j\omega C} + j\omega L + R_2$$

$$Z_{in,A} = \frac{(R_1 + R_2)j\omega C - \omega^2 L C + 1}{j\omega C}$$

Network A

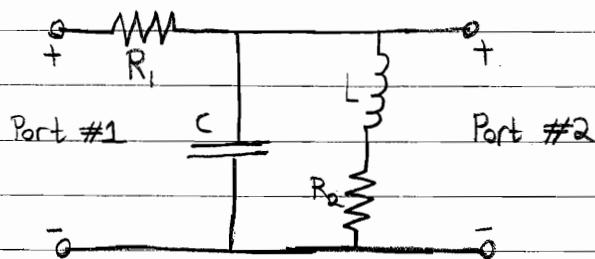

$$Z_{in,B} = R_1 + \frac{j\omega C (R_2 + j\omega L)}{R_2 + j\omega L + j\omega C}$$

$$\begin{aligned} Z_{in,B} &= R_1 + \frac{R_2 + j\omega L}{1 + (R_2 + j\omega L)j\omega C} \\ &= \frac{R_1 + R_2 - \omega^2 L R_1 C + j\omega C (R_1 R_2 C + 1)}{1 - \omega^2 L C + j\omega R_2 C} \end{aligned}$$

Problem Set 10 Solutions

P.10.2 (B)

$$\text{Port \#1} \rightarrow v_1(t) = V_1 \cos(\omega t) \Rightarrow \tilde{v}_1 = V_1 e^{j\omega t}$$

Port \#2  $\rightarrow$  Open

Network A:

$$I_{in,A} = \frac{V_1}{Z_{in,A}} = \frac{V_1 j\omega C}{(R_1 + R_2) j\omega C - \omega^2 LC + 1}$$

$$|I_{in,A}| = |I_{in,A}| e^{j\phi} \quad \text{where } \phi = \angle I_{in,A}$$

$$|I_{in,A}| = \frac{V_1 \omega C}{\sqrt{(1 - \omega^2 LC)^2 + (\omega C(R_1 + R_2))^2}}$$

$$\phi_{in,A} = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega C(R_1 + R_2)}{1 - \omega^2 LC}\right)$$

$$\text{So } i_{in,A}(t) = |I_{in,A}| \cos(\omega t + \phi_{in,A})$$

Network B:

$$I_{in,B} = \frac{V_1}{Z_{in,B}} = \frac{V_1 (1 - \omega^2 LC + j\omega R_2 C)}{R_1 + R_2 - \omega^2 L R_1 C + j\omega C (R_1 R_2 C + L)}$$

$$|I_{in,B}| = \frac{V_1 \sqrt{(1 - \omega^2 LC)^2 + (\omega R_2 C)^2}}{\sqrt{R_1 + R_2 - \omega^2 L R_1 C + \omega^2 C (R_1 R_2 C + L)}}$$

$$\phi_{in,B} = \tan^{-1}\left(\frac{\omega R_2 C}{1 - \omega^2 LC}\right) - \tan^{-1}\left(\frac{\omega (R_1 R_2 C + L)}{R_1 + R_2 - \omega^2 L R_1 C}\right)$$

$$\text{So } i_{in,B}(t) = |I_{in,B}| \cos(\omega t + \phi_{in,B})$$

(C) Voltage at Port \#2 is given by voltage divider:

Network A:

$$V_{2,A} = V_1 \frac{\frac{1}{j\omega C} + j\omega L + R_2}{R_1 + R_2 + \frac{1}{j\omega C} + j\omega L} = \frac{V_1 (1 - \omega^2 LC + j\omega R_2 C)}{1 - \omega^2 LC + j\omega C (R_1 + R_2)}$$

$$|V_{2,A}| = \frac{V_1 \sqrt{(1 - \omega^2 LC)^2 + (\omega R_2 C)^2}}{\sqrt{(1 - \omega^2 LC)^2 + (\omega (R_1 + R_2) C)^2}}$$

Problem Set 10 Solutions

P.10.2 (C) Continued

$$\phi_{2A} = \tan^{-1}\left(\frac{wR_2C}{1-w^2LC}\right) - \tan^{-1}\left(\frac{w(R_1+R_2)C}{1-w^2LC}\right)$$

$$\text{So } V_{2A}(t) = |V_{2A}| \cos(wt + \phi_{2A})$$

Network B:

$$V_{2B} = \frac{\frac{V_1}{jwC(jwL+R_2)}}{R_1 + \frac{jwC(jwL+R_2)}{jwC+R_2+jwL}} = \frac{V_1}{1 + R_1 \frac{jwC+R_2+jwL}{jwC(jwL+R_2)}}$$

$$V_{2B} = \frac{V_1}{1 + \frac{R_1(j-w^2L)+jwR_2}{jwL+R_2+R_1-w^2LC}} = \frac{V_1(jwL+R_2)}{jwL+R_2+R_1-w^2LC+jwR_2C}$$

$$|V_{2B}| = \frac{V_1 \sqrt{(wL)^2 + R_2^2}}{\sqrt{[R_2 + R_1(1-w^2LC)]^2 + w^2(L+R_1+R_2)^2}}$$

$$\phi_{2B} = \tan^{-1}\left(\frac{wL}{R_2}\right) - \tan^{-1}\left(\frac{jw(L+R_1R_2C)}{R_2 + R_1(1-w^2LC)}\right)$$

$$\text{So } V_{2B}(t) = |V_{2B}| \cos(wt + \phi_{2B})$$


(D) Run Network A in WebLab. A screen shot of WebLab is shown on the next page which includes the magnitude and phase plots. The plots show the "notch" frequency is  $f_n = 1\text{ kHz}$ . Since  $w_n = 2\pi f_n = \frac{1}{\sqrt{LC}}$  we can solve for

$$C = \frac{1}{(2\pi f_n)^2} = \frac{1}{(98 \times 10^3)(2\pi)(1 \times 10^3)^2} = 2.58 \times 10^{-7} = 258\text{nF}$$

Also, we know that for  $w = w_n = \frac{1}{\sqrt{LC}}$

$$\frac{V_2}{V_1} = \frac{wR_2C}{w(R_1+R_2)C} = \frac{R_2}{R_1+R_2} \approx 0.1981 \quad (\text{From WebLab})$$

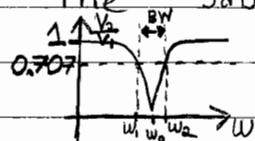The 3dB frequencies (where gain drops to  $\frac{1}{\sqrt{2}} = 0.707$ ):



$$BW = w_2 - w_1$$

From WebLab:

$$f_1 \approx 660\text{ Hz} \quad f_2 \approx 1747\text{ Hz}$$

$$w_1 = 4147\text{ rad/s}$$

$$w_2 \approx 10.977\text{ rad/s}$$

## Problem Set 10 Solutions

P10.2 (D) Therefore:

$$\frac{V_2}{V_1} = \frac{\sqrt{(1 - w_1^2 LC)^2 + (w_1 R_2 C)^2}}{\sqrt{(1 - w_1^2 LC)^2 + C w_1 (R_1 + R_2) C^2}} = \frac{1}{\sqrt{2}}$$

Let  $a = (1 - w_1^2 LC)^2 = 0.320$ ,  $b = \frac{1}{C w_1} = 5.048$   $\gamma = (w_1 C)^2$   
 $\Rightarrow \gamma = 1.145 \times 10^{-6}$

So  $\frac{a + \gamma R_2^2}{a + \gamma b^2 R_2^2} = \frac{1}{2}$

$$\Rightarrow 2a + \gamma R_2^2 = a + \gamma b^2 R_2$$

$$\gamma R_2^2 (b^2 - 1) = a$$

$$\Rightarrow R_2 = \sqrt{\frac{a}{b^2 - 1} \cdot \frac{1}{\gamma}} = 106.8 \Omega$$

Given:

$$\frac{R_2}{R_1 + R_2} = \frac{1}{b}$$

$$b R_2 = R_1 + R_2$$

$$R_1 = (b - 1) R_2$$

$$R_1 = 432.3 \Omega$$

File Measurement Results Help

Test 2: Swept Sine Experiment

Circuit Schematic

Source Level (Pk-to-Pk) (VPK) :




2.0

Start Frequency (Hz) :

1.0

Stop Frequency (Hz) :

50000.0

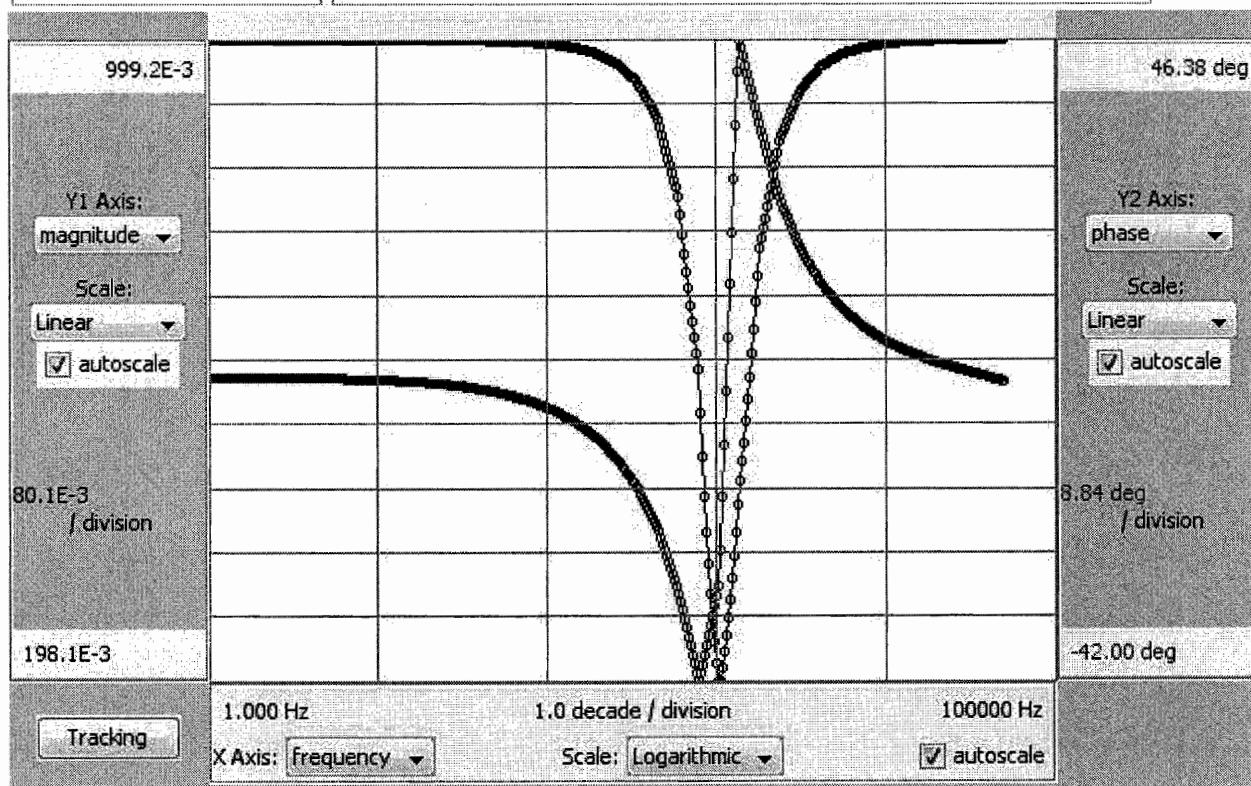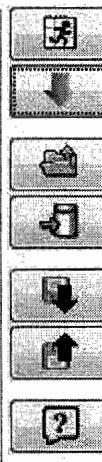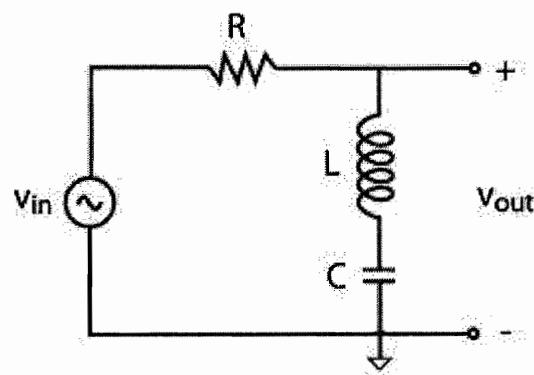

Problem Set 10 Solutions

P10.3 (A)

$$I(t) = I \cos(\omega t) = \operatorname{Re}\{I e^{j\omega t}\}$$

$$V(j\omega) = I (j\omega L // \frac{1}{j\omega C} // R) = I \left( \frac{j\omega LR}{j\omega L + R} // \frac{1}{j\omega C} \right)$$

$$= \frac{IL \frac{R}{C}}{(j\omega L + R) \left( \frac{j\omega LR}{j\omega L + R} + \frac{1}{j\omega C} \right)}$$

$$= \frac{IL \frac{R}{C}}{j\omega RL + \frac{j\omega L + R}{j\omega C}}$$

$$= \frac{I j\omega LR}{R(1 - \omega^2 LC) + j\omega L}$$

$$V(\omega) = \frac{I \omega LR}{\sqrt{R^2(1 - \omega^2 LC)^2 + (\omega L)^2}}$$

$$\phi(\omega) = \frac{\pi}{2} - \tan^{-1} \left( \frac{\omega L}{R(1 - \omega^2 LC)} \right) = \tan^{-1} \left( \frac{R(1 - \omega^2 LC)}{\omega L} \right)$$

(B)  $\max V(\omega) \Rightarrow \max Z$

$Z$  is max when  $Z_L/Z_C \rightarrow \infty$  when  $\omega = \frac{1}{\sqrt{LC}}$   
So impedance  $Z$  is just  $R$

(C)  $L = 470 \mu H$  Range of  $C$ ?

Max  $Y_L \rightarrow \max Z \rightarrow \omega = \frac{1}{\sqrt{LC}}$  from part (b)

Frequency range  $520 \text{ kHz} < f < 1610 \text{ kHz}$

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \rightarrow C = \frac{1}{(2\pi f)^2 L}$$

Minimum  $C$ :  $f = 1610 \text{ kHz}$

$$C = 20.8 \text{ pF}$$

Maximum  $C$ :  $f = 520 \text{ kHz}$

$$C = 199.3 \text{ pF}$$

Problem Set 10. Solutions

P.10.3 (D) When  $f = 1 \text{ MHz}$ ,

$$\frac{V(1 \text{ MHz} \pm 5 \text{ kHz})}{V(1 \text{ MHz})} \approx 0.25$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{so} \quad Z = R$$

$$\text{Thus } V = V_0 = IR \quad @ \quad \omega = \omega_0 = \frac{1}{\sqrt{LC}} \quad (f = 1 \text{ MHz})$$

As  $\omega$  moves away from  $\omega_0$ ,  $Z$  decreases, decreasing  $V_0$

$$\text{For } f = 1 \text{ MHz} + 5 \text{ kHz} = 1.005 \text{ MHz}, \quad \omega_1 = 1.005 \omega_0 = \frac{1.005}{\sqrt{LC}} = \frac{\gamma}{\sqrt{LC}} = \gamma \omega_0$$

$$V(\gamma \omega_0) = 0.25 IR$$

$$V(\gamma \omega_0) = \frac{IR \omega_1 L R}{\sqrt{R^2(1-\omega_1^2 LC)^2 + (\omega_1 L)^2}} = 0.25 IR$$

$$\therefore \frac{8\sqrt{\frac{L}{C}}}{\sqrt{R^2(1-\gamma^2)^2 + \gamma^2 \frac{L}{C}}} = 0.25$$

$$\frac{\gamma^2}{C R^2 (1-\gamma^2)^2 + \gamma^2} = (0.25)^2$$

$$\frac{C}{L} R^2 (1-\gamma^2)^2 + \gamma^2 = \frac{\gamma^2}{(0.25)^2}$$

$$R = \sqrt{\frac{[(\frac{\gamma}{0.25})^2 - \gamma^2]L}{(1-\gamma^2)^2 C}}$$

$$L = 470 \mu\text{H}$$

$$C = \frac{1}{2\pi f^2 L} = 53.9 \text{ pF}$$

$$R = \sqrt{\frac{15\gamma^2 L}{(1-\gamma^2)^2 C}}$$

$$\text{For } \gamma = 1.005 \quad R = 1,147 \text{ k}\Omega$$

$$\gamma = 0.995 \quad R = 1,141 \text{ k}\Omega$$

Choose larger  $R$  for better attenuation @  $1 \text{ MHz} \pm 5 \text{ kHz}$

$$R = 1,147 \text{ k}\Omega$$

(E) Find  $\frac{V(1 \text{ MHz} \pm 10 \text{ kHz})}{V(1 \text{ MHz})}$

$\therefore$  Let  $\gamma = 1.01, 0.99$

$$\frac{V(\gamma \omega_0)}{V(\omega_0)} = \frac{I \frac{\gamma}{\sqrt{LC}} LR}{\sqrt{R^2(1-\gamma^2)^2 + \gamma^2 \frac{L}{C}}} \cdot \frac{1}{IR} = \frac{\gamma}{\sqrt{\frac{C}{L} R^2 (1-\gamma^2)^2 + \gamma^2}}$$

$$\text{For } \gamma = 1.01, \quad \frac{V(1.01 \omega_0)}{V(\omega_0)} = 0.128$$

$$\text{For } \gamma = 0.99, \quad \frac{V(0.99 \omega_0)}{V(\omega_0)} = 0.127$$

Problem Set 10 Solutions

P.10.3 (E) Continued

$$f = 1 \text{ MHz}$$

$$Q = \frac{W_0}{2\alpha} = \frac{1}{\sqrt{LC}} \cdot \frac{1}{2} \cdot \frac{2RC}{1} = R\sqrt{\frac{C}{L}} = 388$$

(F) Here the transient, which decays as  $e^{-\alpha t}$ , needs to be considered, where  $\alpha = \frac{1}{2RC}$ . The "τ" of this is  $\frac{1}{\alpha} = 2RC$ , which is 124 μs. In general we can say that the transient has nearly died out after  $\sim 5\tau$  (99% decay)

$$5\tau = 620 \mu\text{s}$$