

SOLUTION OF PS 6


6.002 Fall 2007

1/11

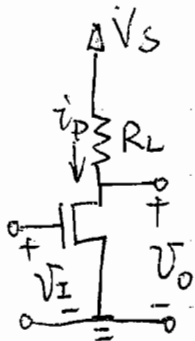Exercise 6.1: a) $\because V_T = 0 \quad \therefore i_{DS} = \frac{k}{2} (V_{GS} - V_T)^2 = \frac{k}{2} V_{GS}^2$

$$V_o = V_s - i_{DS} \cdot R_L = V_s - \frac{k}{2} V_{GS}^2 \cdot R_L = V_s - \frac{k}{2} V_I^2 \cdot R_L$$

$$\therefore V_o = f(V_I) = V_s - \frac{k R_L}{2} \cdot V_I^2$$



b) To keep the amplifier operating in saturation region, we need:

$$V_{DS} \geq V_{GS} - V_T \geq 0$$

$$\because V_T = 0$$

$$\therefore V_{DS} \geq V_{GS} \geq 0 \Rightarrow V_{DS} \geq V_I \geq 0$$

At the boundary of saturation and triode regions, we still have

$$V_{DS} = V_s - \frac{k R_L}{2} \cdot V_I^2$$

Therefore,

$$V_s - \frac{k R_L}{2} \cdot V_I^2 \geq V_I$$

$$\Rightarrow \frac{k R_L}{2} \cdot V_I^2 + V_I - V_s \leq 0$$

$$\Rightarrow V_I \leq \frac{-1 + \sqrt{1 + 2kR_L V_s}}{kR_L}$$

The negative solution is eliminated because it will put MOSFET in cutoff region.

Combining all the information we have, we obtain that

$$0 \leq V_I \leq \frac{-1 + \sqrt{1 + 2kR_L V_s}}{kR_L}$$

2/11

Because output current $i_D = i_{DS} = \frac{k}{2} V_I^2$

$$\therefore 0 \leq i_D \leq \frac{1 + KR_L V_s - \sqrt{1 + 2KR_L V_s}}{KR_L^2}$$

$$\therefore v_o = v_{DS} = V_s - i_D \cdot R_L$$

$$\therefore \frac{\sqrt{1 + 2KR_L V_s} - 1}{KR_L} \leq v_o \leq V_s$$

Note that it makes sense when it's on the boundary of saturation and triode, $v_o = v_I = \frac{\sqrt{1 + 2KR_L V_s} - 1}{KR_L}$

c) We want to set bias V_I such that v_o is half way between its valid range derived in part b), therefore,

$$v_o = \frac{-1 + KR_L V_s + \sqrt{1 + 2KR_L V_s}}{2KR_L}$$


$$\therefore i_D = \frac{V_s - v_o}{R_L}$$

$$\therefore i_D = \frac{1 + KR_L V_s - \sqrt{1 + 2KR_L V_s}}{2KR_L^2}$$

$$\therefore i_D = \frac{k}{2} V_I^2 \Rightarrow V_I = \sqrt{\frac{2i_D}{k}}$$

$$\therefore V_I = \sqrt{\frac{2i_D}{k}} = \sqrt{\frac{1 + KR_L V_s - \sqrt{1 + 2KR_L V_s}}{KR_L}}$$

Exercise 6.2:

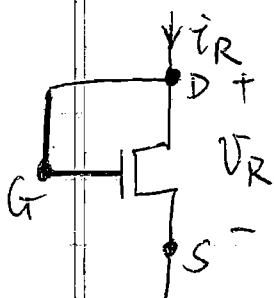

a) For a MOSFET operation in saturation region,

$$i_D = \frac{K(V_{GS} - V_T)^2}{2}$$

In this case: $V_{GS} = V_{DS} = V_D$

$$i_D = i_D$$

$$\therefore i_D = \frac{K(V_D - V_T)^2}{2}$$


b) From part a), we have $i_D = \frac{K(V_D - V_T)^2}{2}$

$$\therefore \left. \frac{di_D}{dV_D} \right|_{V_D=V_D} = \frac{2 \cdot K(V_D - V_T)}{2} \Big|_{V_D=V_D} = K(V_D - V_T)$$


i.e. When it's operating at de bias $V_D = V_D > V_T$, the small-signal model will be,

$$\frac{i_v}{v_v} = \left. \frac{di_D}{dV_D} \right|_{V_D=V_D} = K(V_D - V_T)$$

$$\Rightarrow \frac{v_v}{i_v} = \frac{1}{K(V_D - V_T)}$$

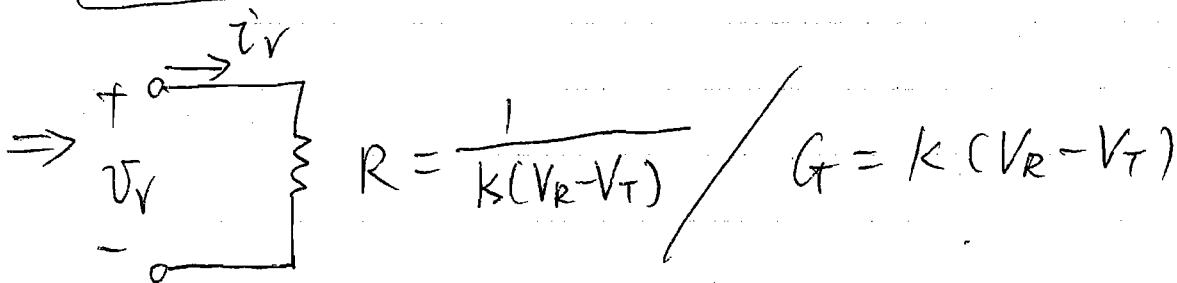

Problem 6.1:

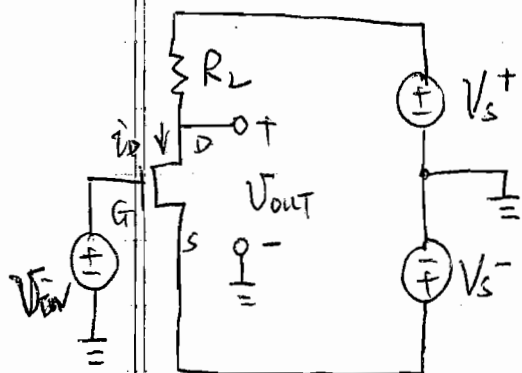a) From circuit, we know when $V_{IN} = 0V$

$$V_{GS} = V_{IN} - V_S^- = 1.5V + V_{IN} = 1.5V$$

$$V_{OUT} = -i_D \cdot R_L + V_S^+$$

$$= -\frac{K(V_{GS} - V_T)^2}{2} \cdot R_L + V_S^+ = 0V$$

$$\Rightarrow R_L = \frac{V_S^+}{\frac{K(V_{GS} - V_T)^2}{2}} = \frac{1.5}{\frac{1 \times 10^{-3} (1.5 - 0.5)^2}{2}} = 3(k\Omega)$$

b) To keep MOSFET in saturation range, we need

$$V_{DS} \geq V_{GS} - V_T$$

Take the boundary point between saturation & triode, we have:

$$V_{DS} = V_{GS} - V_T$$

~~from part a), we have~~

$$\text{from circuit, we have, } V_{DS} = V_S^+ - V_S^- - i_D R_L = V_S^+ - V_S^- - \frac{K(V_{GS} - V_T)^2}{2}$$

from part a), we have, $V_T = 0.5V$, $R_L = 3k\Omega$, $K = 1mA/V^2$, $V_S^+ = 1.5V$, $V_S^- = -1.5V$

$$\therefore 3 - \frac{3}{2}(V_{GS} - 0.5)^2 = V_{GS} - 0.5$$




$$\Rightarrow 3 - \frac{3}{2}V_{DS}^2 = V_{DS}$$

$$\Rightarrow V_{DS}^2 + \frac{2}{3}V_{DS} - 2 = 0$$

$$\Rightarrow V_{DS} = \frac{-\frac{2}{3} \pm \sqrt{(\frac{2}{3})^2 + 8}}{2} \Rightarrow V_{DS} = 1.12V \quad (\text{only positive solution applies})$$

$$\therefore V_{OUT} = V_{DS} + V_S^- = -0.38V \quad \boxed{V_{OUT, \min} = -0.38V}$$

Problem 6.2.

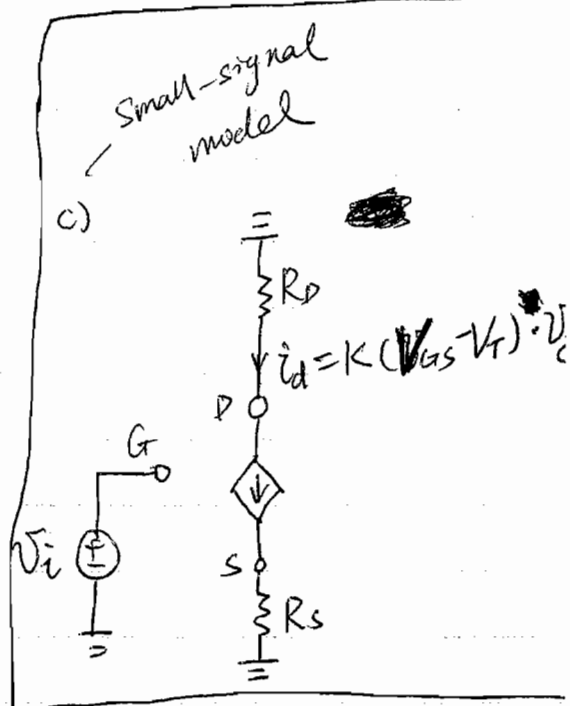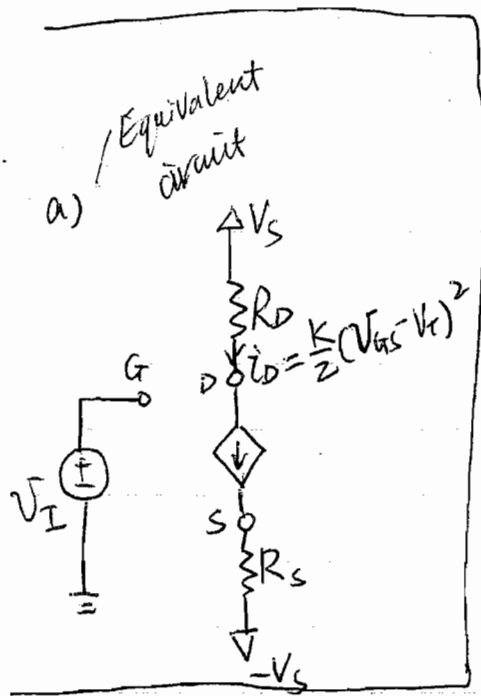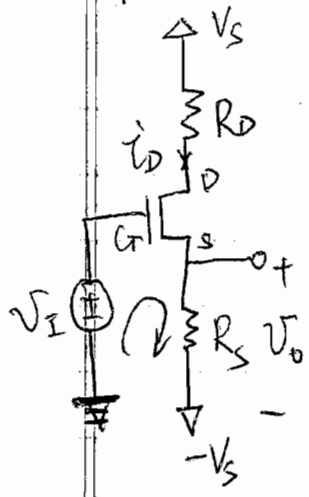

b) Write KVL loop equation around the bottom portion of the circuit and we have,

$$V_I - V_{GS} - I_D R_S = -V_S \Rightarrow V_{GS} = V_I + V_S - I_D R_S$$

So under saturation discipline, we have operating point current

$$I_D = \frac{K}{2} (V_{GS} - V_T)^2 = \frac{K}{2} (V_I + V_S - I_D R_S - V_T)^2$$

Solve the quadratic equation about I_D and notice the negative term wouldn't apply, we have,

$$I_D = \frac{1}{KR_S^2} + \frac{V_I - V_T + V_S}{R_S} - \frac{\sqrt{2KR_S(V_I - V_T + V_S) + 1}}{KR_S^2}$$


Then, $V_O = I_D R_S + (-V_S)$

$$= \frac{1}{KR_S} + V_I - V_T - \sqrt{\frac{2}{KR_S}(V_I - V_T + V_S) + \frac{1}{K^2 R_S^2}}$$

c) See up-right for small-signal model. To find small-signal gain, we take $dV_{out}/dv_i |_{v_i=V_I}$. This will give us

$$A_v = \frac{dV_{out}}{dv_i} |_{v_i=V_I} = 1 - [2KR_S(V_I - V_T + V_S) + 1]^{-1/2}$$

Problem 6.3.

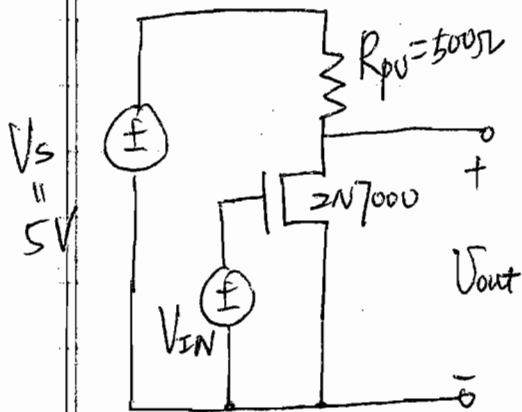

a) - Please see Page 7

b) Please see Page 8

c) Please see Page 9

d) Please see Page 10

e) Because different people could get slightly different data, so it's possible to get slightly different fitted values for K and V_T . The fitting approach should be similar, though, as following.

① From part a), b) & c), we can pick a good estimation of V_T . From my data, I pick $V_T = 2V$.

② From part b), pick a pair of (V_{GS}, V_{DS}) , which is in saturation mode. For example, I pick $(V_{GS} = 2.2V, V_{DS} = 4.5V)$, therefore, $i_D = \frac{V_S - V_{DS}}{R_{pu}} = \frac{5 - 4.5}{500} = 1mA$, which is


consistent with the measured data shown in part a) & b).

On the other hand, because it's in saturation mode, so we have, $i_D = \frac{K}{2} (V_{GS} - V_T)^2 \Rightarrow K = \frac{2i_D}{(V_{GS} - V_T)^2} = \frac{2 \times 1 \times 10^{-3}}{(2.2 - 2.0)^2} = 0.05 A/V^2$

\therefore The fitted values of V_T & K are: $V_T = 2.0 V$
Please see page 11 for graphical comparison. $K = 0.05 A/V^2$


7/11

P.6.3.a)

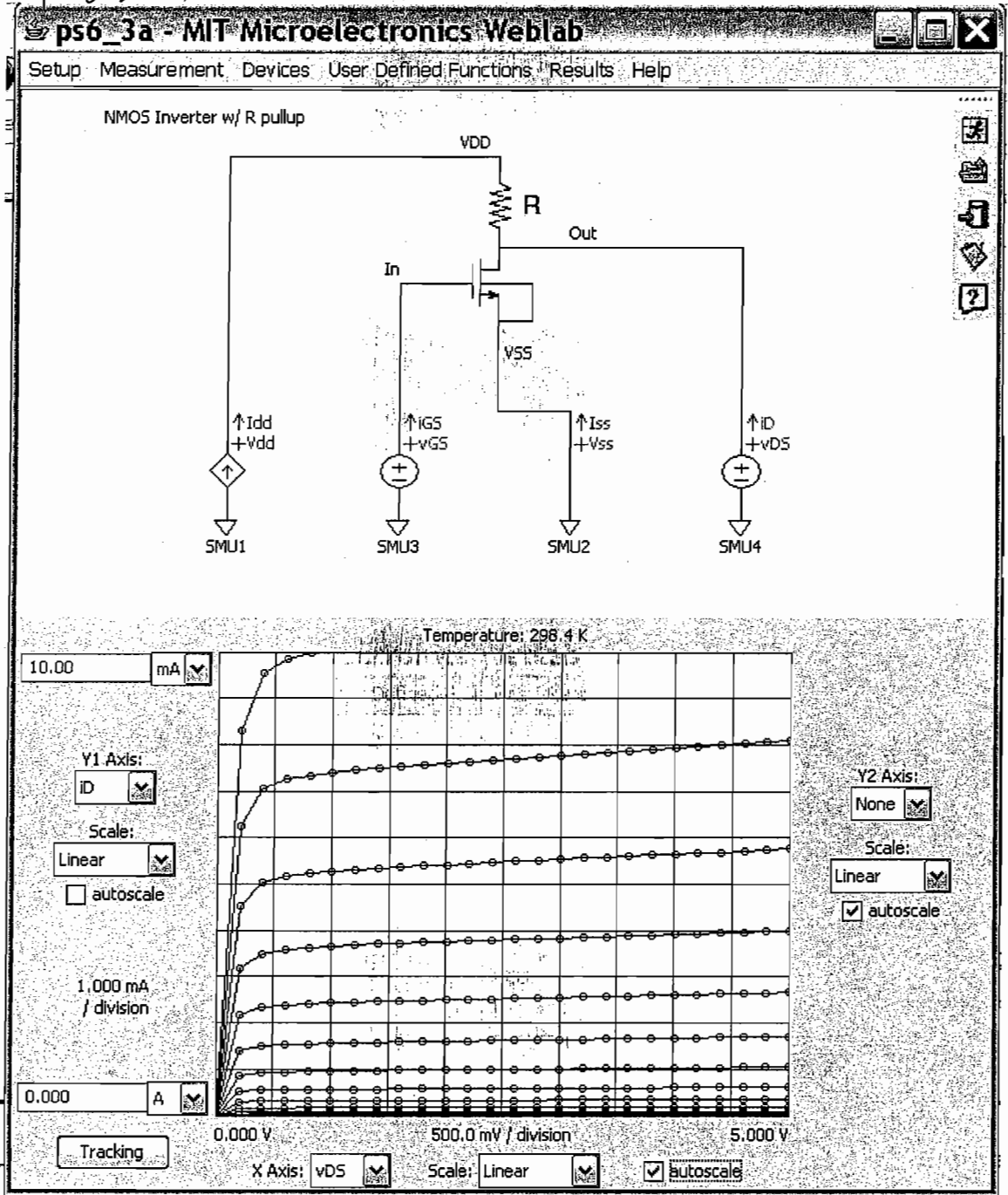


9/11

P.6.3. c)

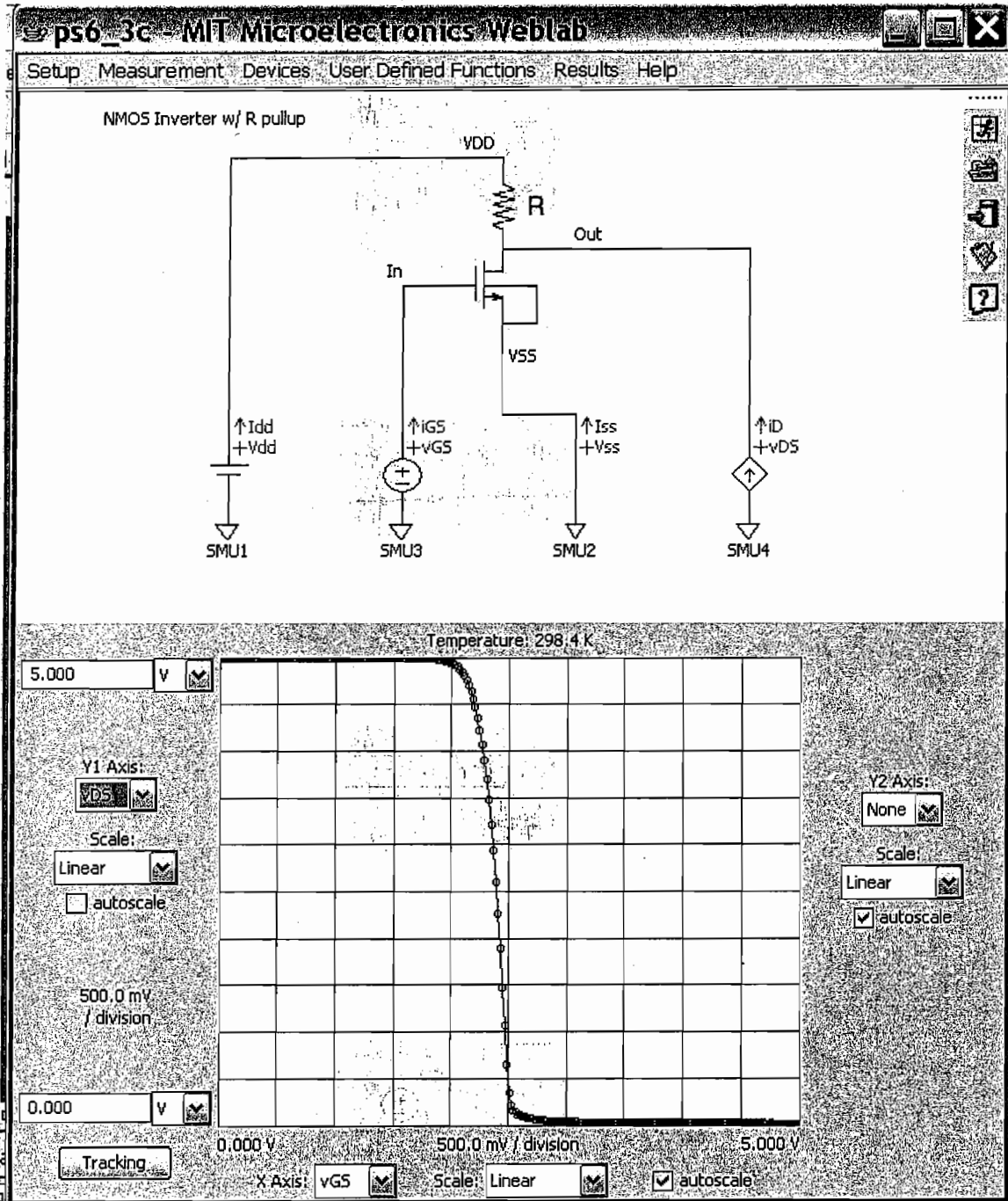


10/11

P.6.3 d)

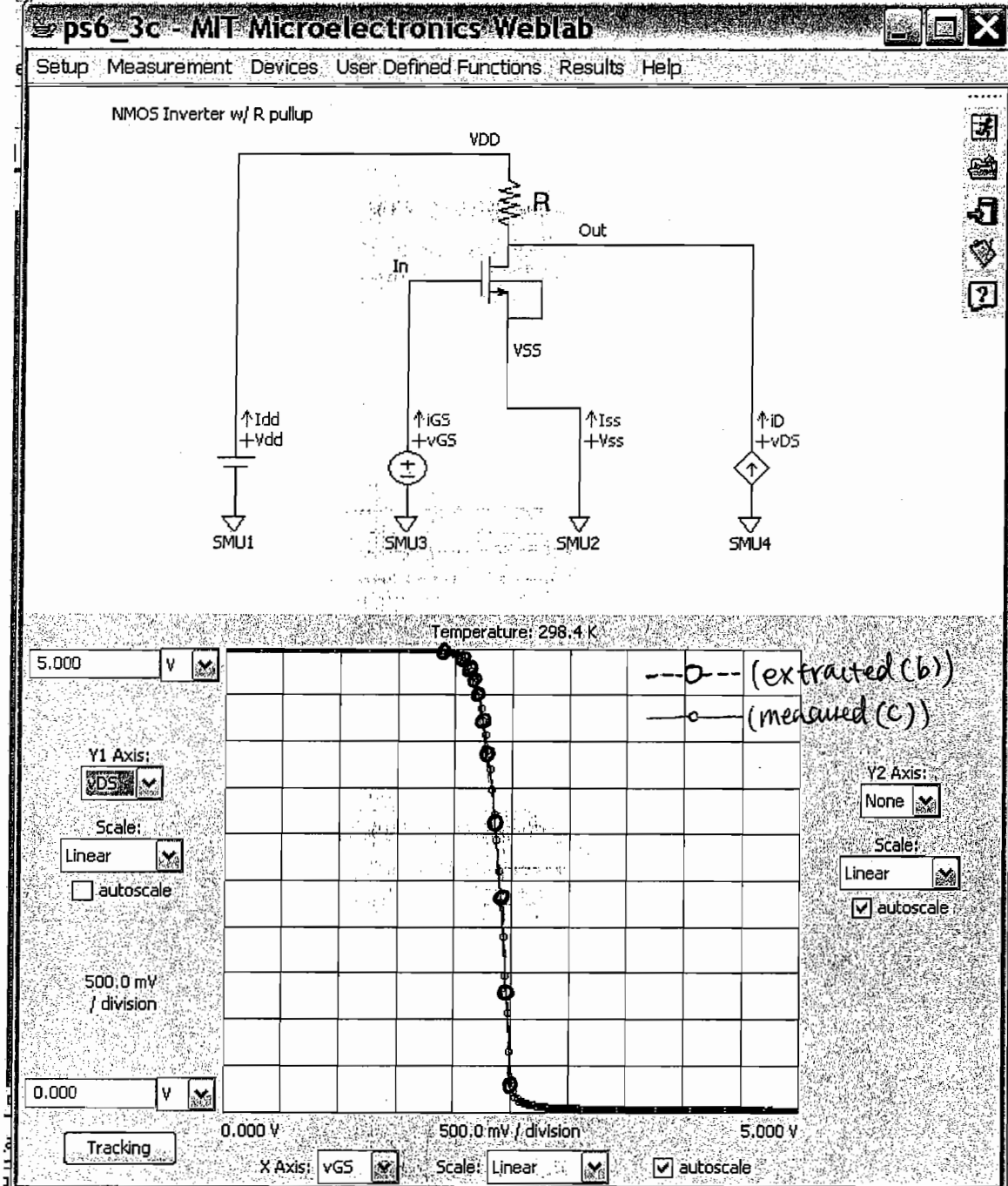

Comparison of measured and fitted data

P.6.3e)

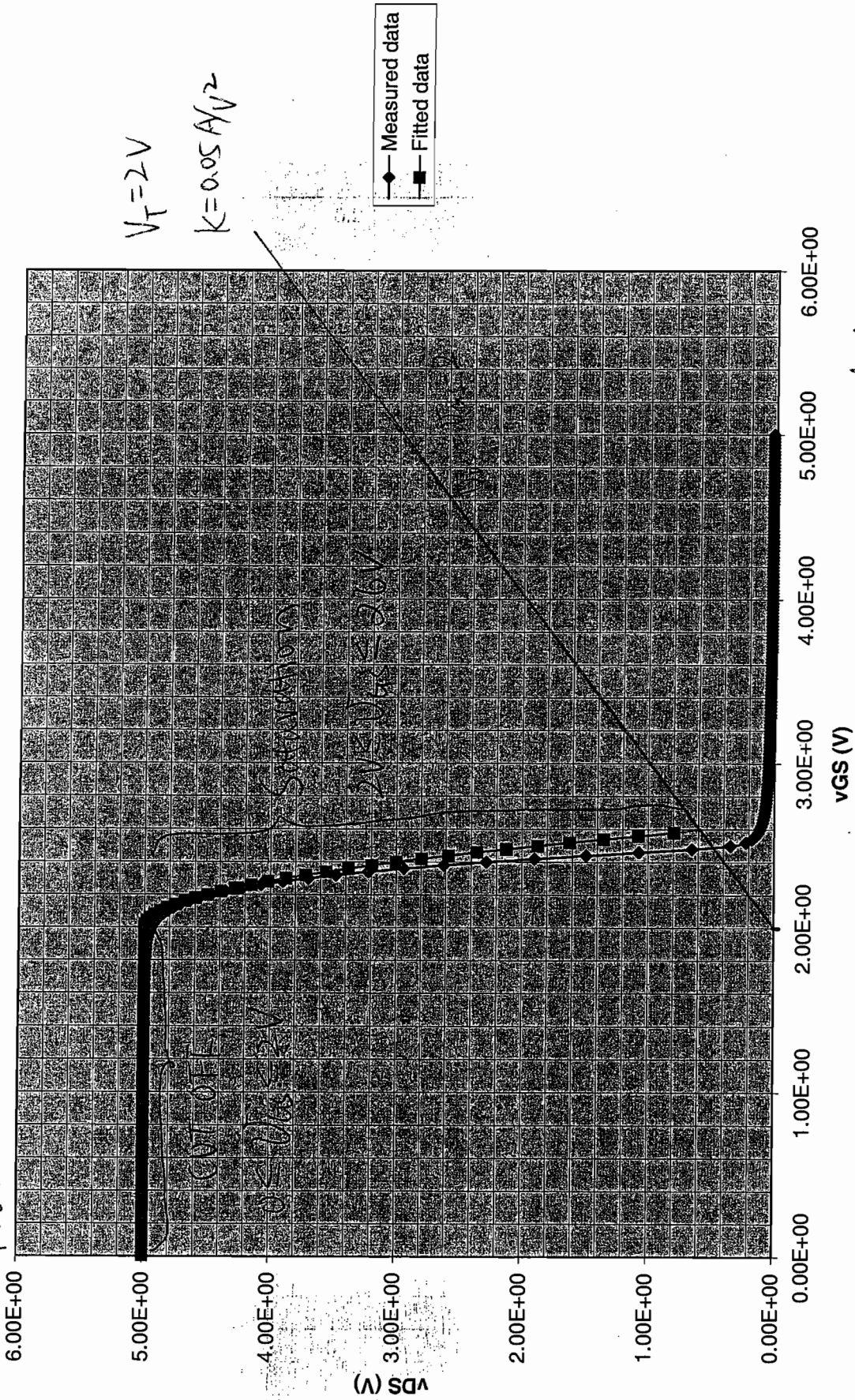

The fitted data is pretty close to the measured data.

The minor difference is due to the change/transfer from one region to another is more gradual in the measured data.