


6.002 - Spring 2008

①


Problem Set #2 Solutions

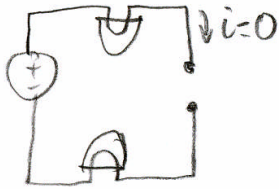Exercise 2.1: Assuming that the intensity of light is proportional to the power dissipated in the bulb:


1st Circuit) Dimmer - and go out. Opening any of the 3 bulbs in series will open the entire circuit. Current and power will be zero for all 3 bulbs.



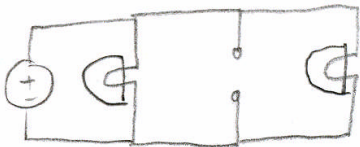2nd Circuit) No Change - with all 3 bulbs in parallel, the voltage and power, as $P = \frac{V^2}{R}$, will remain constant on the 2 remaining bulbs




3rd Circuit) Brighter - the current and power, as $P = I^2 R$, increase as the same total current is now split between the 2 remaining bulbs.

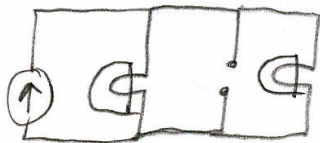

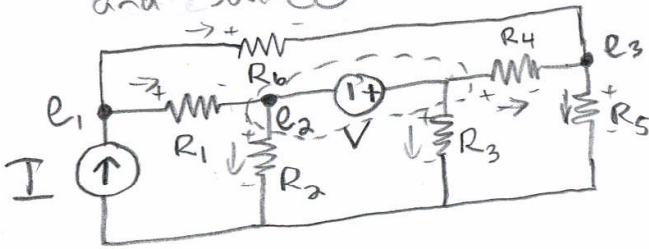Exercise 2.2

Using the node method: $G_n = \frac{1}{R_n}$, need to find the terms for the \mathbf{G} and \mathbf{S} conductance matrix and source vector.



$$\text{at } e_1: I = (e_1 - e_3)G_6 + (e_1 - e_2)G_1$$

$$\underline{I = e_1(G_1 + G_6) - e_2G_1 - e_3G_6}$$

at e_2 "supernode":

$$(e_1 - e_2)G_1 = e_2G_2 + (e_2 + V)G_3 + (e_2 + V - e_3)G_4$$

$$\underline{-V(G_3 + G_4) = -e_1G_1 + e_2(G_1 + G_2 + G_3 + G_4) - e_3G_4}$$

at e_3 :

$$(e_1 - e_3)G_6 + (e_2 + V - e_3)G_4 = e_3G_5$$

$$\underline{V \cdot G_4 = -e_1G_6 - e_2G_4 + e_3(G_4 + G_5 + G_6)}$$


and as $\mathbf{G} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \mathbf{S}$

$$\begin{bmatrix} (G_1 + G_6) & -G_1 & -G_6 \\ -G_1 & G_1 + G_2 + G_3 + G_4 & -G_4 \\ -G_6 & -G_4 & G_4 + G_5 + G_6 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} I \\ -V(G_3 + G_4) \\ V \cdot G_4 \end{bmatrix}$$


Problem 2.1

(3)

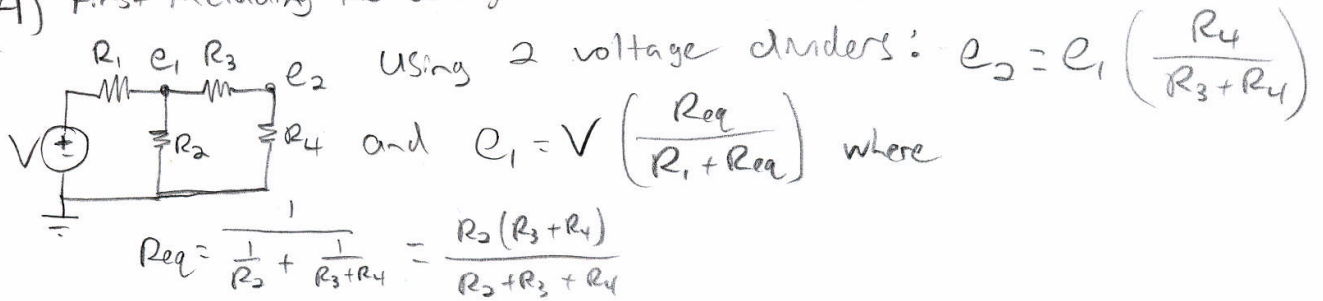(A) First including the voltage source and opening the current source:



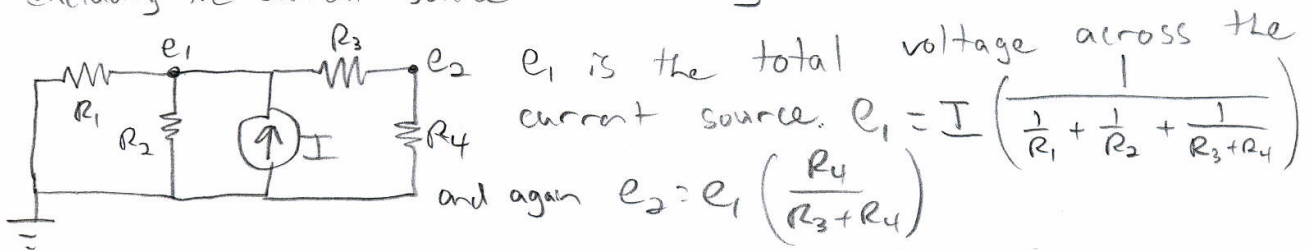Including the current source and shorting the voltage source:



Combining both parts gives:

$$e_1 = \frac{V \cdot R_2 (R_3 + R_4) + I \cdot R_1 R_2 (R_3 + R_4)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$$


$$e_2 = \frac{(V \cdot R_2 + I \cdot R_1 R_2) R_4}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$$

$$\text{and } e_2 = e_{1 \text{ tot}} \left(\frac{R_4}{R_3 + R_4} \right)$$

Problem 2.1 (continued)

(4)

(B) Using the Node Method:

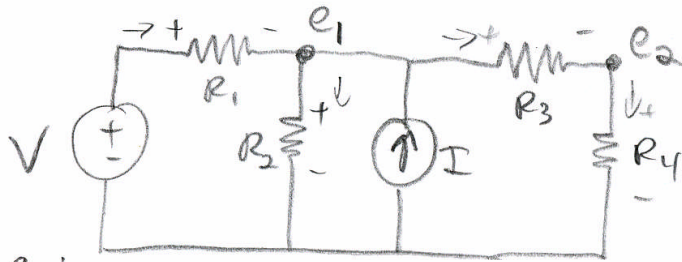

at e_1 :

$$\frac{V - e_1}{R_1} + I = \frac{e_1}{R_2} + \frac{e_1 - e_2}{R_3}$$

$$\frac{V}{R_1} + I = e_1 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} - \frac{R_4}{R_3(R_3 + R_4)} \right] = e_1 \left[\frac{(R_3 + R_4)(R_2 R_3 + R_1 R_3 + R_1 R_2) - R_4 R_1 R_2}{R_1 R_2 R_3 (R_3 + R_4)} \right]$$

$$\Rightarrow e_1 = \left(\frac{V}{R_1} + I \right) \left(\frac{R_1 R_2 R_3 (R_3 + R_4)}{R_2 R_3 R_3 + R_2 R_3 R_4 + R_1 R_3 R_3 + R_1 R_3 R_4 + R_1 R_2 R_3 + R_1 R_2 R_4 - R_1 R_2 R_4} \right)$$

$$e_1 = \frac{(V \cdot R_2 + I \cdot R_1 R_2)(R_3 + R_4)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$$

$$e_2 = \frac{R_4 (V \cdot R_2 + I \cdot R_1 R_2)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$$

at e_2 :

$$\frac{e_1 - e_2}{R_3} = \frac{e_2}{R_4}$$

$$e_1 \cdot R_4 = e_2 (R_3 + R_4)$$

$$e_2 = e_1 \cdot \left(\frac{R_4}{R_3 + R_4} \right) \text{ again}$$

(C) The solutions to parts (A) and (B) are identical.


Problem 2.1 (continued)

5

$$(D) V_{TH} = V_{oc} = e_2 = \frac{R_2 R_4 (V + IR_1)}{R_1 R_2 + (R_1 + R_2)(R_3 + R_4)}$$


from either part (A) or (B)

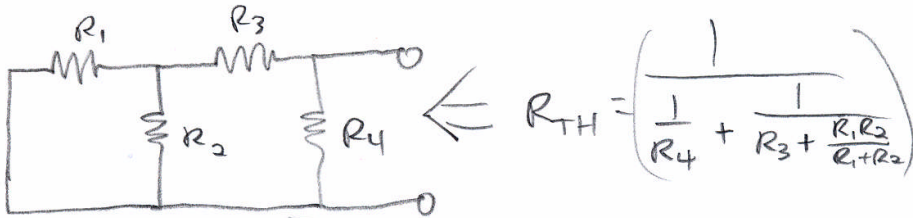The equivalent resistance, R_{TH} , looking into the terminals, with the voltage source shorted and the current source open is:




R_4 is in parallel with the series combination of R_3 with the parallel combination of R_1 and R_2 .
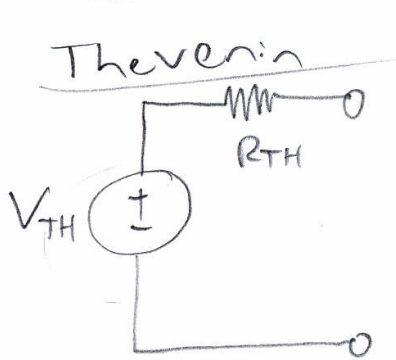
$$R_{TH} = \frac{R_4 (R_1 R_2 + R_1 R_3 + R_2 R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_1 R_4 + R_2 R_4}$$



OR

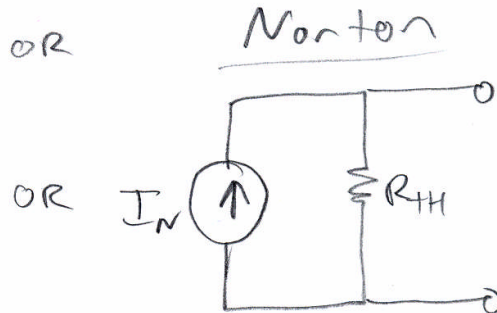

Where



$$I_N = \frac{V_{TH}}{R_{TH}}$$

the short circuit current

$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{R_2 (V + IR_1)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$



Problem 2.2

(6)

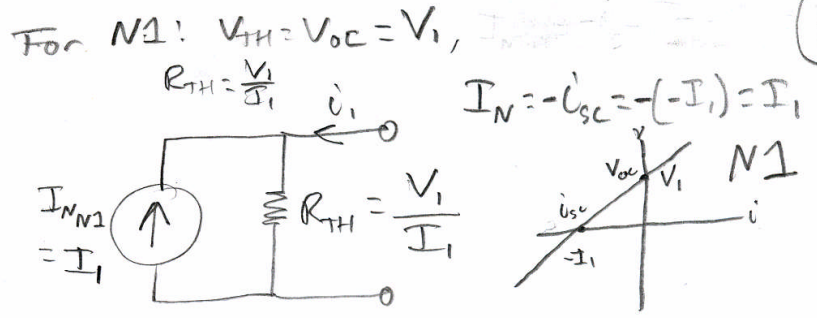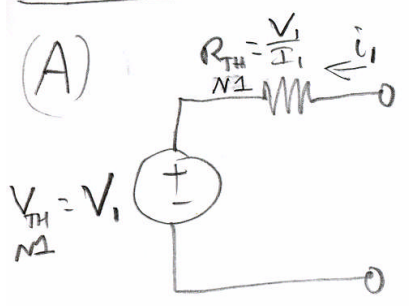


For N2:

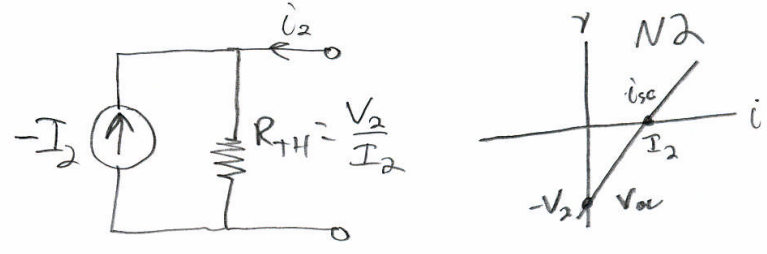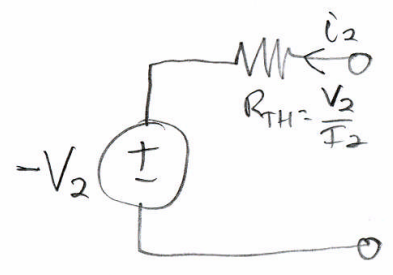$V_{TH} = V_{OC} = -V_2$; $I_N = -i_{sc} = -I_2$; $R_{TH} = \frac{V_{TH}}{I_N} = \frac{-V_2}{-I_2} = \frac{V_2}{I_2}$



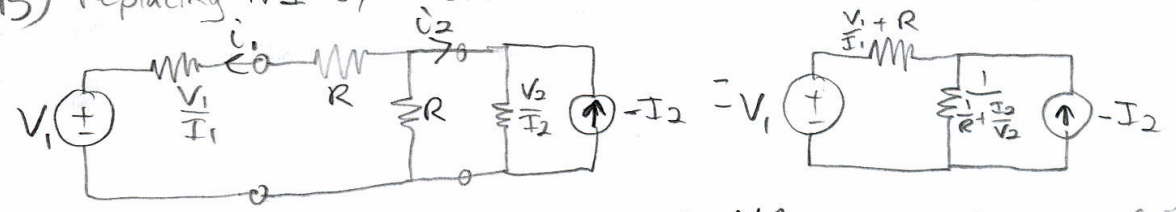(B) Replacing N1 by Thevenin and N2 by Norton equivalents:



i_1 is still the total current out of N1, using superposition and voltage and current dividers:

$$i_1 = \frac{-V_1}{\left(\frac{V_1}{I_1} + R\right) + \left(\frac{V_2 R}{V_2 + I_2 R}\right)} - I_2 \left(\frac{\frac{V_2 R}{V_2 + I_2 R}}{\left(\frac{V_1}{I_1} + R\right) + \frac{V_2 R}{V_2 + I_2 R}} \right)$$

$$i_2 = -i_{1, \text{ due to } V_1} \left(\frac{R}{R + \frac{V_2}{I_2}} \right) + I_2 \left(\frac{\frac{V_2 / I_2}{R_{eq} + \frac{V_2}{I_2}}}{R_{eq} + \frac{V_2}{I_2}} \right) \text{ where } R_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{R + \frac{V_1}{I_1}}}$$

Simplify to:


$$i_1 = \frac{-I_1 [V_1 V_2 + I_2 R (V_1 + V_2)]}{(V_1 + I_1 R)(V_2 + I_2 R) + I_1 V_2 R} ; i_2 = \frac{I_2 [V_1 V_2 + I_1 R (V_1 + 2V_2)]}{(V_1 + I_1 R)(V_2 + I_2 R) + I_1 V_2 R}$$

Problem 2.3

7

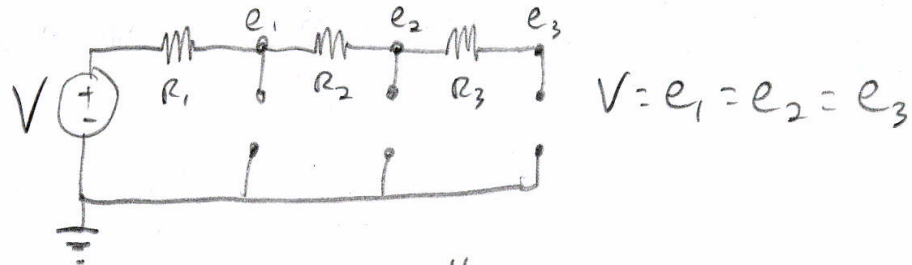(A) $\max e_2 = V$


Volts
When all loads are "off," all currents are zero, the current sources act as open circuits and there is no voltage drop across R_1 and R_2 .



$\min e_2 = V - 3IR_1 - 2IR_2$

Volts
For minimum e_2 , need maximum voltage drop and

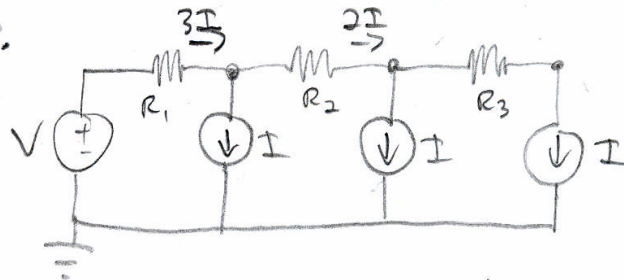current thru R_1 and R_2 . This occurs when all 3 current sources are "ON" and carry I amps. KCL at each node gives the current in each resistor.



(B) $3IV$ Watts

The maximum power will be supplied to the maximum load, when all 3 current sources, representing processor loads, are "ON." This will also give maximum current and power loss in the resistors. All 3 current sources will sink, dissipate,

power since all 3 node voltages and all 3 current sources are all positive. $I \downarrow v_n$ $P_n = i_n v_n > 0$ So the voltage source is the only power source and it must output a maximum $3IA$. The same result could be found by adding up the power dissipated in all 3 resistors and all 3 current sources.

Problem 2.3 (continued)

(8)

(C) $V_{\min} = e_{\min} + 3IR_1 + 2IR_2 + IR_3$ Volts

The lowest possible voltage, after maximum voltage drop from V across all 3 resistors, occurs at e_3 , when all 3 current sources are "ON" for maximum current in all resistors. In this case $e_3 = V - (3IR_1 + 2IR_2 + IR_3) \geq e_{\min}$

and for $V \geq e_{\min} + (3IR_1 + 2IR_2 + IR_3)$,
 $V_{\min} = e_{\min} + (3IR_1 + 2IR_2 + IR_3)$

(D) $V_{\max} = e_{\max}$ Similar to part (A) the maximum voltages occur with minimum current and voltage drop across the resistors. With all of the current sources open, at 0 A, no loads are connected, no current flows thru any of the resistors and $e_1 = e_2 = e_3 = V$.

so in this case for $e_1 = e_2 = e_3 \geq e_{\max}$

$V_{\max} = e_{\max}$

Problem 2.4

(9)

(A) $V_T \approx 2.58 \cdot 10^{-2}$ volts

using $T = 299.4$ Kelvin
in $V_T = \frac{kT}{q}$

(B) $i_D \approx -I_s$ for around $V_D \leq -0.1$ volts

Using a linear scale for current is deceptive in this case, making all of the small currents below about 0.4 V appear constant around 0 A. The log plot agrees with the theoretical expectation in that $e^{-3} \approx 0.05$, so the exponential part of the relation will have less than a 5% impact on i_D for $V_D < -3V_T$ or $V_D < -0.08$ volts

(C) With a graphical solution it is again more difficult to determine where the exponential behavior begins on the plot using a linear current scale. Using the log scale, the plot appears linear with the exponential dominating for about

$V_D > 0.1$ V

This matches theoretical expectation that for above $\frac{V_D}{V_T} \approx 3$ or 4 at $V_D \approx 0.8$ V or $V_D \approx 0.1$ V, the exponential will be contributing about 95% or 98% of i_D .



On the exponential branch of the data, I_s would be the y-intercept of the extended linear-looking plot of the exponential. From $i_D = I_s(e^{\frac{V_D}{V_T}} - 1)$ and neglecting the -1 gives $i_D \approx I_s e^{\frac{V_D}{V_T}}$ and at $V_D = 0$

Here $I_s \approx 2$ nA

$i_D \approx I_s$

This roughly agrees with $-I_s$ at the extreme negative V_D .



1N914

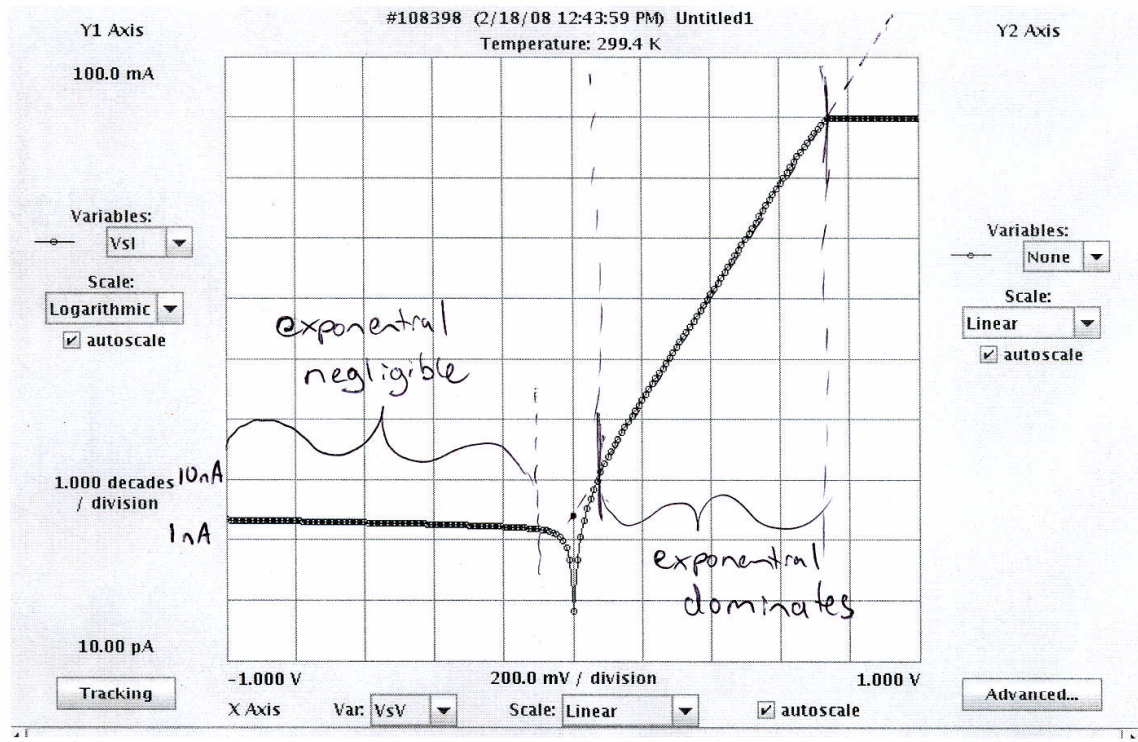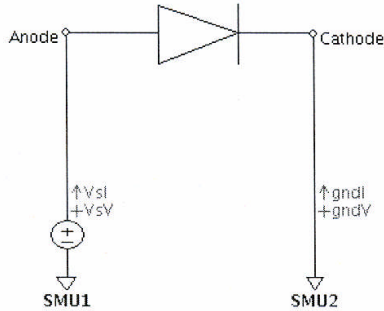


11

#108398: Untitled1

1N914

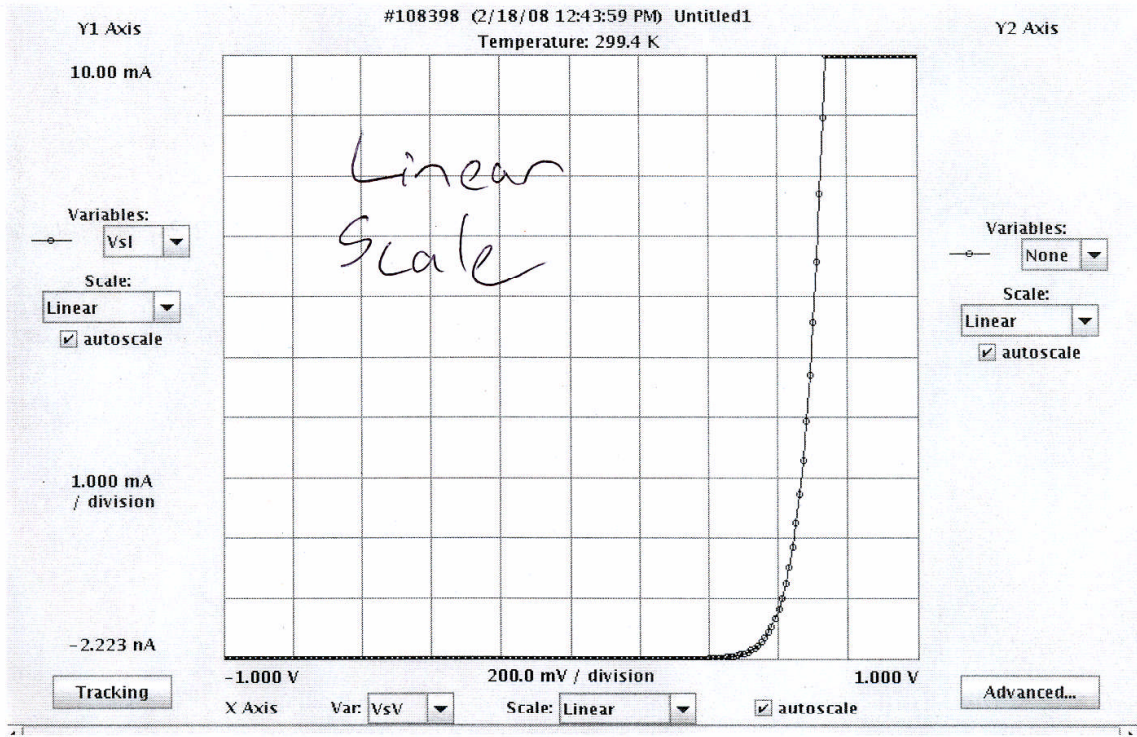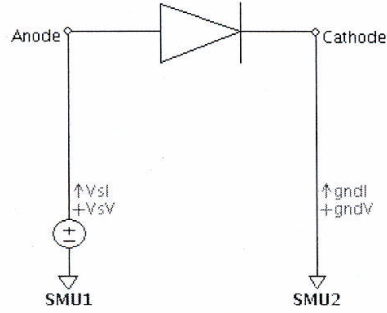

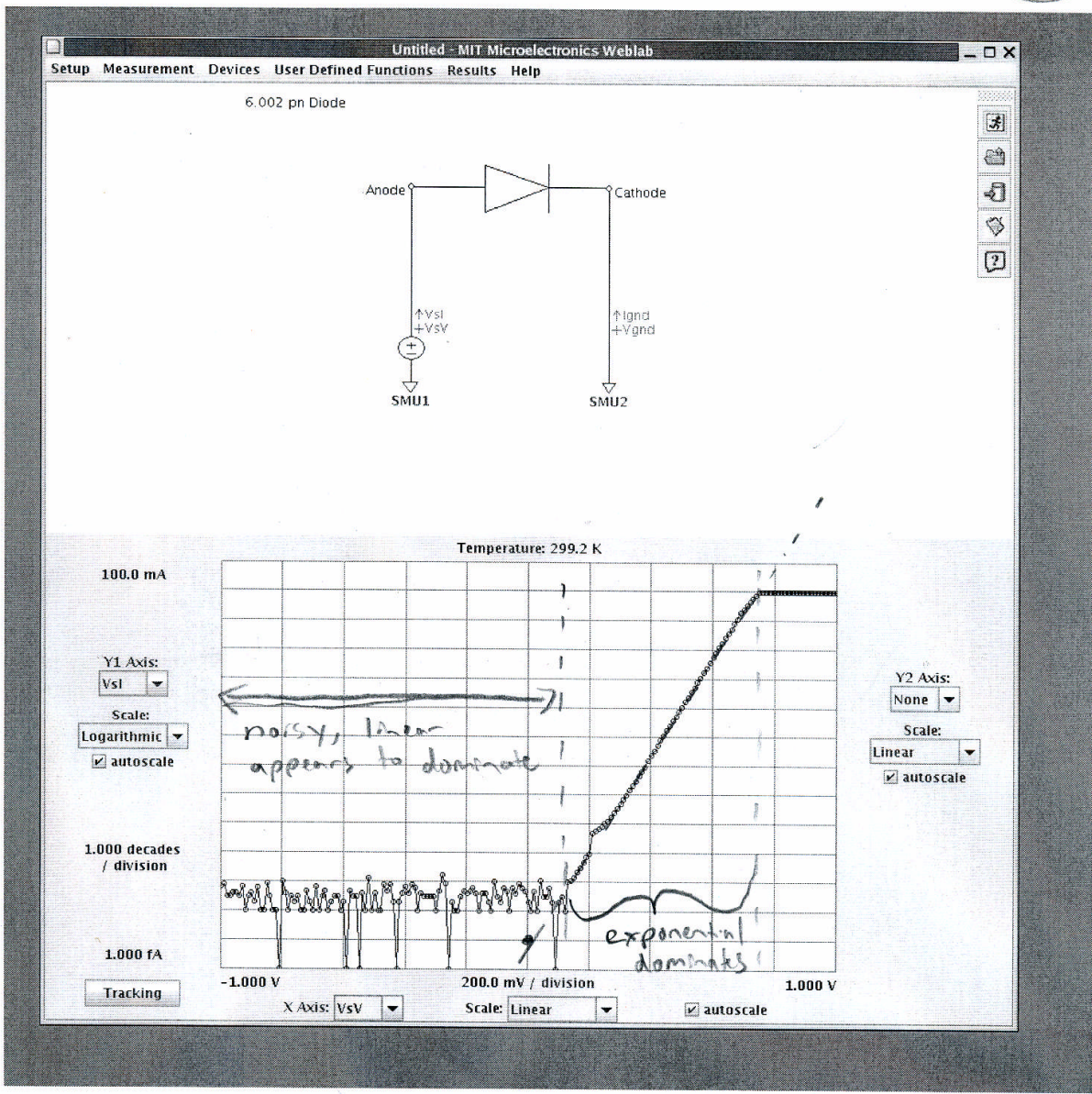

Using the 6.002 pn Diode, the exponential still dominates over about $V_D > 0.1V$, roughly agreeing with some theoretical expectations. But here the lowest current signal is noisy and it appears that the linear portion dominates for $V_D < 0.1V$, when theoretical calculations would expect around $V_D < -0.1V$. Graphically finding I_s from the exponential portion, the y-axis intercept of the extended linear-looking plot gives $I_s \approx 10fA$. This is lower than the $\approx 300fA$ average from the lowest voltage portion.