


Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits & Electronics
Spring 2008



Problem Set #6

Issued 3/12/08 – Due 3/19/08

Exercise 6.1 (1 Point): Consider the network shown below, which contains a Thevenin equivalent, a nonlinear resistor and a small-signal current source, all in parallel. The current through, and the voltage across, the nonlinear resistor are related according to $v_{NR} = (1 \text{ V/mA/mA}) \cdot i_{NR}^2$. First, assume that the small-signal current amplitude i_s is zero. Show that V_{NR} , the bias component of v_{NR} is 1 V. Second, assume that $i_s = 1 \mu\text{A}$ and use a small signal model to determine v_{nr} , the small-signal component of v_{NR} .

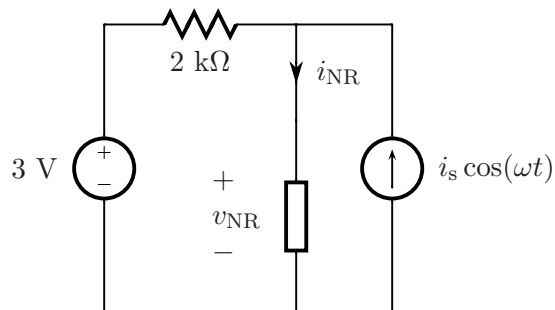


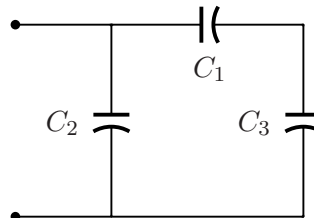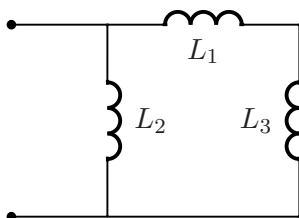Exercise 6.2 (1 Point): Find the inductance of the all-inductor network, and the capacitance of the all-capacitor network, shown below.




Problem 6.1 (2 Points): This problem studies the propagation delay of digital signals through the inverter shown below. Assume that the MOSFET in the inverter acts as a switch with on-state resistance R_{ON} . The inverter is loaded by a capacitor, having capacitance C_G , that models the combined input capacitance of the logic gates connected to its output. Assume that the inverter obeys the static discipline defined in part by V_{OL} and V_{OH} .

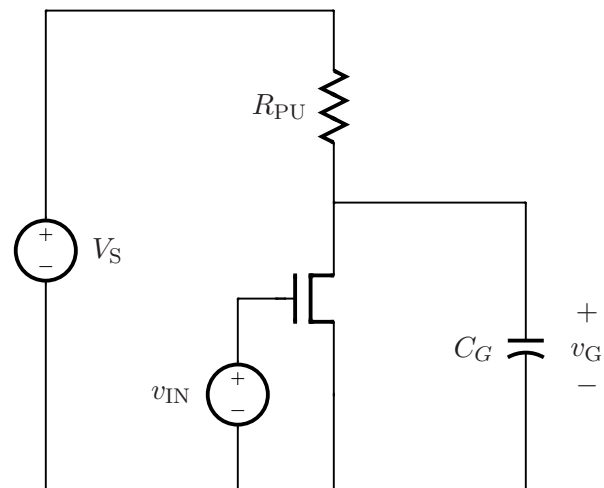
- (A) Assume that the MOSFET has been off for a very long time. At $t = 0$, v_{IN} turns the MOSFET on. Determine $v_G(t)$ for $t \geq 0$.
- (B) How long does it take $v_G(t)$ to pass by V_{OL} ? This delay is the fall time of the inverter.
- (C) Assume that the MOSFET has been on for a very long time. At $t = 0$, v_{IN} turns the MOSFET off. Determine $v_G(t)$ for $t \geq 0$.
- (D) How long does it take $v_G(t)$ to pass by V_{OH} ? This delay is the rise time of the inverter.
- (E) If more gates are connected to the output of the inverter will the delays found in Parts (B) and (D) become shorter or longer? Why?
- (F) How can the fall and rise times be shortened via the design of R_{PU} ? What limits the extent to which this design path may be followed?



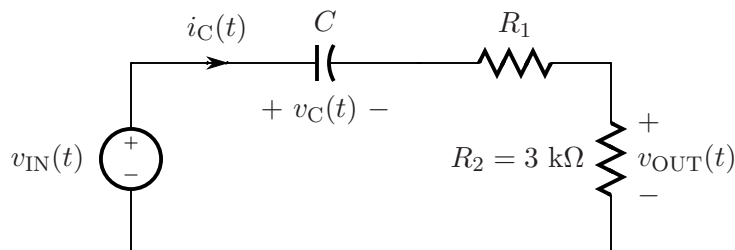Problem 6.2 (2 Points): This problem studies the response of a series RC network, both theoretically and experimentally. The experiments will be performed using the ELVIS iLab. The circuit to be studied is shown below. It comprises a capacitor, two resistors and a voltage source all in series. The voltage $v_{\text{OUT}}(t)$ across R_2 can be measured and used to determine the current through the series network.



Consider first a theoretical study of the network. Let the voltage $v_{\text{IN}}(t)$ be a periodic square wave with amplitude V and period T as shown below. The period T is much larger than the RC time constant of the network. Assume that $v_{\text{IN}}(t)$ has been applied long before $t = 0$, while any measurements start at $t = 0$. Thus, the network has reached its periodic steady state before any measurements are taken.

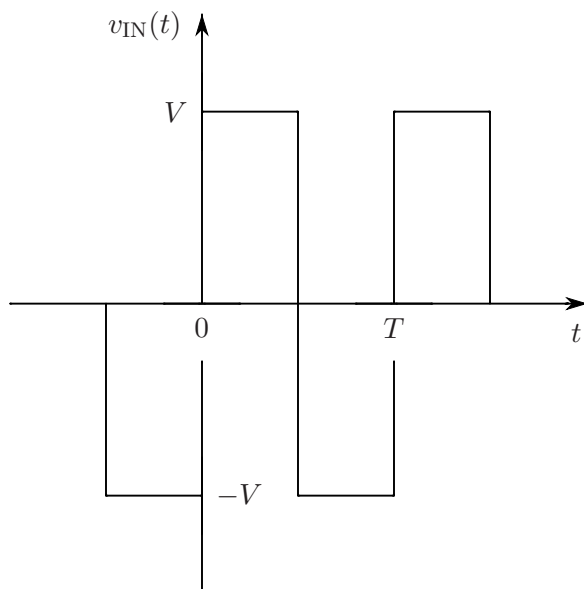

- Derive an expression for $v_C(t)$, the voltage across the capacitor. Your answer should include separate expressions for the time period over which $v_{\text{IN}}(t) = V$, and the time period over which $v_{\text{IN}}(t) = -V$. Hint: consider the consequences of T being much longer than the RC time constant of the network, and use reasonable engineering judgement.
- Derive an expression for $i_C(t)$, the current flowing through network.
- Derive an expression for $v_{\text{OUT}}(t)$, the voltage across R_2 .

Now consider an experimental study of the network. First, log in to the ELVIS iLab as in previous homeworks. After launching the iLab, you should see a network that is equivalent to the one shown


above.

First, select the voltage source, or FGEN signal generator, and set its parameters to WaveForm = SQUARE, Frequency = 200 Hz, Amplitude = 1 V, and Offset = 0 V. Second, select the SCOPE output measurement unit and program it with a suitable sampling rate that will allow you to see at least one full cycle of $v_{\text{OUT}}(t)$ with enough resolution. Note that the system will only allow you to take a maximum of 201 data samples at the output. Third, run the experiment. Finally, select $v_{\text{IN}}(t)$ for the Y1 axis and $v_{\text{OUT}}(t)$ for the Y2 axis, and use linear axes for both. When the figure resembles what you expect, capture a screen shot for subsequent analysis.

- (D) From the experimental data, extract the RC time constant of the network. You can see the actual numerical values of the data that you have obtained by looking into *View Data* under the *Results* menu. You can also download the data to Excel using the *Results* menu.
- (E) From the experimental data, extract the value of the resistor R_1 . When you do this, note that even though you selected 1 V as the amplitude, the signal generator does not impose this voltage very accurately; the actual amplitude is measured as v_{IN} .
- (F) From the experimental data, extract the value of C .

Problem 6.3 (2 Points): In the circuit shown below, a MOSFET and an external resistor having resistance R_X are used to control the current i_R in the winding of a relay. Here, the relay is modeled as a series inductor and resistor having inductance L_R and resistance R_R , respectively. The MOSFET may be modeled as an ideal switch.

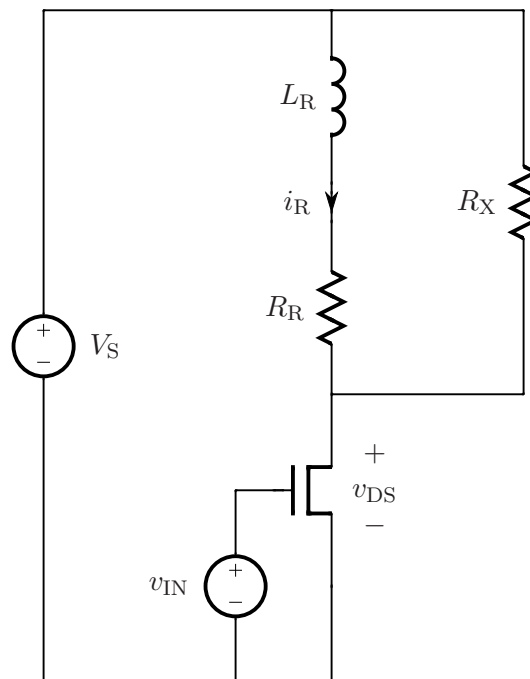- (A) At $t = 0$, v_{IN} turns the MOSFET on so that $v_{DS} = 0$. Determine $i_R(t)$ for $t \geq 0$ given that $i_R(t = 0) = 0$.
- (B) Next, at $t = T$, v_{IN} turns the MOSFET off. Determine both $i_R(t)$ and $v_{DS}(t)$ for $t \geq T$. Hint: $i_R(t)$ is continuous at $t = T$.
- (C) Sketch and clearly label graphs of both $i_R(t)$ and $v_{DS}(t)$ for $t \geq 0$ assuming that $T \approx 5L_R/R_R$ and $R_X = R_R$.
- (D) The relay control circuit would be less expensive without the external resistor, which may be “removed” from the circuit by considering the limit $R_X \rightarrow \infty$. Why might such a cost reduction be unwise?



Problem 6.4 (2 Points): At $t = 0^-$, the two networks shown below both have zero initial state. That is, the inductor current $i(t)$ and the capacitor voltage $v(t)$ are both zero at $t = 0^-$. At $t = 0$, the current source produces an impulse of area Q , and the voltage source produces an impulse of area Λ .

- (A) Derive the differential equations that relate $i(t)$ to $I(t)$ and $v(t)$ to $V(t)$. Hint: consider using Thevenin and/or Norton equivalents to simplify the work.
- (B) Find the inductor current $i(t)$ and capacitor voltage $v(t)$ at both $t = 0^+$ and $t = \infty$. One way to find the state at $t = 0^+$ is to integrate the corresponding differential equation from $t = 0^-$ to $t = 0^+$ under the assumption that the state remains finite during that time; you should justify this assumption. Then, substitute the initial condition at $t = 0^-$ into the result to determine the state at $t = 0^+$. Try to determine the states at $t = \infty$ through physical, rather than mathematical, reasoning.
- (C) Next, find the time constant by which each state goes from its initial value at $t = 0^+$ to its final value at $t = \infty$.
- (D) Using the previous results, and without necessarily solving the differential equations directly, construct $i(t)$ and $v(t)$ for $t \geq 0$.
- (E) Verify that the solutions to Part (D) are correct by substituting them into the differential equation found in Part (A).

