


1

6.002 Spring 2008

Problem Set #6 Solutions

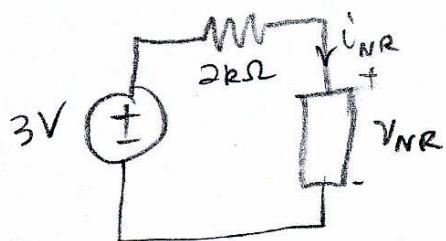Exercise 6.1

First, with $i_s = 0$: KVL: $3V - 2k\Omega i_{NR} = V_{NR}$



given $V_{NR} = \left(\frac{V}{mA/mA}\right) i_{NR}^2$

expect, assume units of i_{NR} to be mA,
to cancel out with $k\Omega$ for Volts

$$3 - 2i_{NR} = 1 i_{NR}^2 \text{ or } i_{NR}^2 + 2i_{NR} - 3 = 0$$


$$\frac{-2 \pm \sqrt{2^2 - 4(1)(-3)}}{2(1)} = \frac{-2 \pm \sqrt{16}}{2} = -1 \pm 2 \text{ mA}$$

the voltage source will drive a clockwise current, so
 i_{NR} will be positive. and can discard the negative solution

$$i_{NR} = 1 \text{ mA} \text{ and } V_{NR} = \frac{V}{mA^2} (1 \text{ mA})^2 = 1 \text{ V}$$

Small Signal Model:

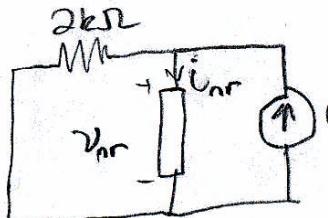Linearizing the behavior of NR
at the bias point:



$$V_{NR} = \left(\frac{dV_{NR}}{di_{NR}} \right) \cdot i_{NR} = 2 \left(\frac{V}{mA} \right)^2 \cdot i_{NR}$$


$i_{NR} = 1 \text{ mA}$

linear slope of nonlinear small
v-i characteristic deviation
at bias point from bias
point

2

Exercise 6.1 (continued)

Small signal model:

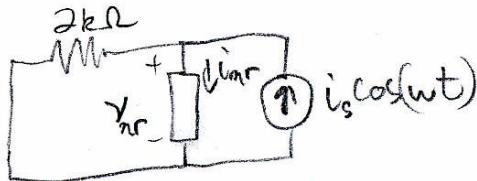

Small signal device:

$$V_{nr} = 2 \frac{V}{mA} i_{nr} = (2 \cdot 10^3) i_{nr}$$

KCL: $i_s \cos(\omega t) = \frac{V_{nr}}{2k\Omega} + i_{nr}$ solve for V_{nr}

$$i_s \cos(\omega t) = \frac{V_{nr}}{2k\Omega} + \frac{V_{nr}}{2k\Omega} = \frac{V_{nr}}{1k\Omega}, i_s = 1\mu A$$


$$V_{nr} = (1 \times 10^{-6} A)(1 \times 10^3 \Omega) \cos(\omega t) \Rightarrow V_{nr} = \cos(\omega t) mV$$

As a sanity check, with $V_{nr} = 2 \frac{V}{mA} i_{nr} = (2 \cdot 10^3) i_{nr}$, the nonlinear device acts as a $2k\Omega$ resistor to small signal responses around this bias point, so with two $2k\Omega$ resistors in parallel, i_{nr} should be half of the source current. $i_{nr} = \frac{V_{nr}}{2 \cdot 10^3 \Omega} = \frac{1 \cdot 10^{-3} \cos(\omega t) V}{2 \cdot 10^3 \Omega}$

$$i_{nr} = 0.5 \times 10^{-6} \cos(\omega t) A$$

$$|i_{nr}| = 0.5 \mu A = 0.5 \text{ mA}$$

✓

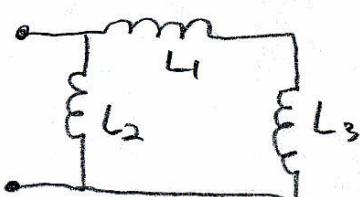Exercise 6.2

Capacitors combine like conductances

$$C_{tot} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_3}} + C_2$$

$$C_{tot} = \frac{C_1 C_3}{C_1 + C_3} + C_2$$


Inductor combine same as resistors:

$$L_{tot} = L_2 // (L_1 + L_3) = \frac{1}{\frac{1}{L_2} + \frac{1}{L_1 + L_3}} = \frac{L_2(L_1 + L_3)}{L_1 + L_2 + L_3}$$

3


Problem 6.1

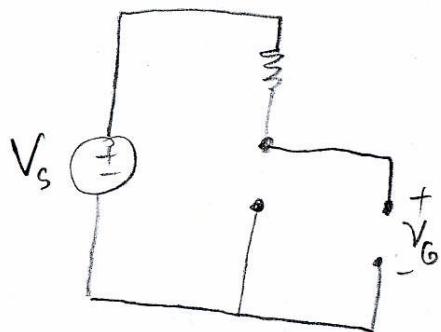(A) Since the MOSFET was off for a long time before $t=0$, the circuit had reached a steady state equilibrium: with $\frac{dV_G}{dt} = 0$ and $i_{C_G} = C_G \frac{dV_G}{dt} = 0$ and C_G modeled as an open circuit:



$$V_G(t=0) = V_s$$

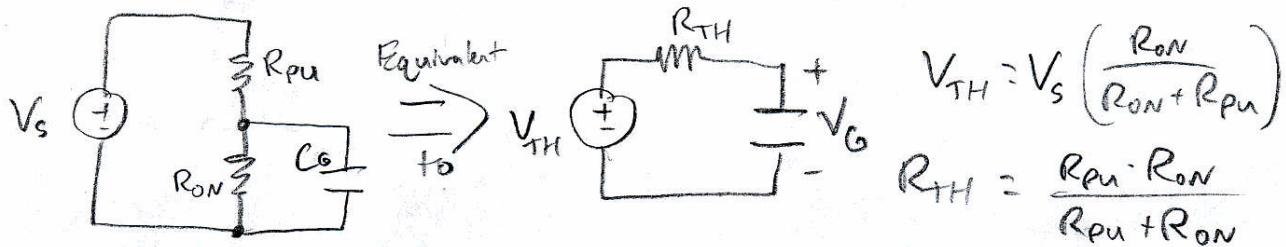After the MOSFET turns on:
Expect V_G to exponentially drop to $V_s \left(\frac{R_{ON}}{R_{ON} + R_{pu}} \right)$



$$\text{KCL: } \frac{V_{TH} - V_G}{R_{TH}} = i_G = C_G \frac{dV_G}{dt}, \quad \frac{dV_G}{dt} + \frac{V_G}{R_{TH} C_G} = \frac{V_{TH}}{R_{TH} C_G}$$

$$V_G(t) = V_G(t_0) + V_G(t)$$

total particular homogeneous

$$\underline{V_{G_{part}} = V_{TH}}$$

$$\frac{dV_{G_{homogeneous}}}{dt} + \frac{V_{G_{homogeneous}}}{R_{TH} C_G} = 0$$

Problem 6.1 (continued)

4

(A) Solving for homogeneous part: $\frac{dV_{Gn}}{dt} = \frac{-V_{Gn}}{R_{TH}C_G}$

$$\int \frac{dV_{Gn}}{V_{Gn}} = \int \frac{-dt}{R_{TH}C_G}$$

$$\ln V_{Gn} = \frac{-t}{R_{TH}C_G} + \text{Const} \quad \text{or} \quad V_{Gn} = e^{\frac{-t}{R_{TH}C_G}} \cdot \text{Const}$$

$$V_{Gn} = A e^{\frac{-t}{R_{TH}C_G}} \quad \text{combining } V_{G_{\text{tot}}} = V_{G_{\text{part}}} + V_{G_{\text{homogeneous}}}$$

$$V_G(t) = V_{TH} + A e^{\frac{-t}{R_{TH}C_G}} \quad \text{apply Initial Condition to solve for } A$$

$$V_G(t=0) = V_s = V_{TH} + A(1) \quad A = V_s - V_{TH}$$

$$V_G(t) = V_{TH} + (V_s - V_{TH}) e^{\frac{-t}{R_{TH}C_G}}$$

where $V_{TH} = V_s \left(\frac{R_{on}}{R_{on} + R_{pu}} \right)$ and $R_{TH} = \frac{R_{on} \cdot R_{pu}}{R_{on} + R_{pu}}$

(B) Solving $V_G(t) = V_{OL}$ for t_{fall} $\rightarrow V_{OL} = V_{TH} + (V_s - V_{TH}) e^{\frac{-t_{\text{fall}}}{R_{TH}C_G}}$

$$\frac{V_{OL} - V_{TH}}{V_s - V_{TH}} = e^{\frac{-t_{\text{fall}}}{R_{TH}C_G}} \quad \text{and} \quad -t_{\text{fall}} = R_{TH}C_G \ln \left(\frac{V_{OL} - V_{TH}}{V_s - V_{TH}} \right)$$

$$t_{\text{fall}} = R_{TH}C_G \ln \left(\frac{V_s - V_{TH}}{V_{OL} - V_{TH}} \right)$$


Again with

$$V_{TH} = V_s \left(\frac{R_{on}}{R_{on} + R_{pu}} \right) \quad \text{and} \quad R_{TH} = \frac{R_{on} \cdot R_{pu}}{R_{on} + R_{pu}}$$

More Problem 6.1

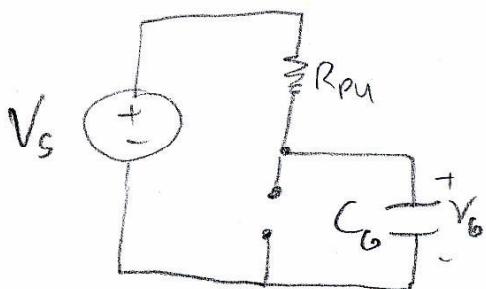(C) ON for long time $\Rightarrow V_G(t=0) = V_{TH} = V_s \left(\frac{R_{ON}}{R_{ON} + R_{pu}} \right)$ 5

After opens, will eventually rise back to $V_G = V_s$



Similar to (A) but with V_s and R_{pu}

$$KCL: \frac{V_s - V_G}{R_{pu}} = I_G = C_G \frac{dV_G}{dt}$$

$$\frac{dV_G}{dt} + \frac{V_G}{R_{pu} C_G} = \frac{V_s}{R_{pu} C_G}$$

$$V_G(t) = V_{G_p}(t) + V_{G_n}(t)$$

New Particular Solution $V_{G_p}(t) = V_s$

$$\text{Same } V_{G_n}(t) = A_c e^{-t/R_{pu}C_G} \text{ with new } R \text{ and } A_c$$

$$V_G(t=0) = V_{TH} = V_s + A_c \text{ and } A_c = V_{TH} - V_s$$

$$V_G(t) = V_s + (V_{TH} - V_s) e^{-t/R_{pu}C_G} \quad \text{for } t \geq 0$$

$$V_{TH} = V_s \left(\frac{R_{ON}}{R_{ON} + R_{pu}} \right) \text{ still}$$

(D) Solving new $V_G(t_{rise}) = V_{OH}$ for $t_{rise} \Rightarrow V_{OH} = V_{TH} + (V_{TH} - V_s) e^{\frac{-t_{rise}}{R_{pu}C_G}}$

$$\frac{V_{OH} - V_{TH}}{V_{TH} - V_s} = e^{\frac{-t_{rise}}{R_{pu}C_G}} \text{ and } -t_{rise} = R_{pu}C_G \ln \left(\frac{V_{OH} - V_{TH}}{V_{TH} - V_s} \right)$$


$$t_{rise} = R_{pu}C_G \ln \left(\frac{V_{TH} - V_s}{V_{OH} - V_{TH}} \right)$$

$$V_{TH} = V_s \left(\frac{R_{ON}}{R_{ON} + R_{pu}} \right)$$

Last of Problem 6.1

6

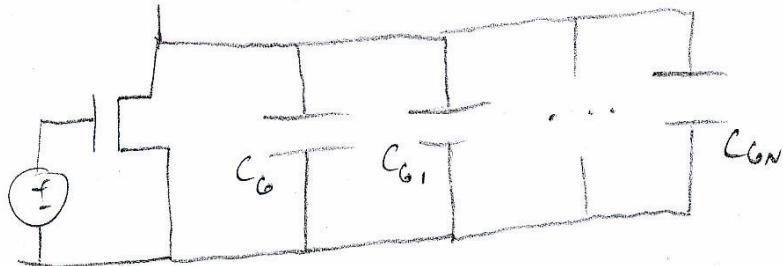(E) Connecting more gates to the inverter output will add additional gate capacitors across the output, in parallel with C_G :




And since parallel capacitors add directly, the total equivalent capacitance will be $C_{tot} = C_G + C_1 + \dots + C_N$. This increased total capacitance will increase the RC time constants and increase the rise and fall times from parts (B) and (D).

(F) Similarly, decreasing R_{pn} will decrease the rise and fall times. However, the lowest possible output of the inverter is $V_{TH} = V_S \left(\frac{R_{on}}{R_{on} + R_{pn}} \right)$, so to obey the static discipline, this minimum must be below V_{OL} , and changing R_{pn} will impact delays thru both the time constant and the final values.

7

Problem 6.2

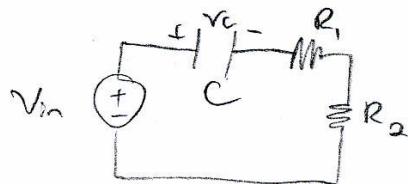(A) With $T \gg RC$, the circuit will reach steady state before switching. In the steady state the capacitor can be modeled by an open circuit, so the steady state voltages will be the source voltage, $\pm V$. And the initial condition will be the steady state from the previous interval, $\mp V$.



$$\text{KVL: } V_m - V_c - i_c(R_1 + R_2) = 0 \quad i_c = C \frac{dV_c}{dt}$$

$$\frac{dV_c}{dt} + \frac{V_c}{C(R_1 + R_2)} = V_m$$

$V_c(t) = V_p(t) + V_h(t)$ total solution is sum of particular and homogeneous solutions

$$V_{ph}(t) = V_m C(R_1 + R_2)$$

Solving $\int \frac{dV_{ch}}{V_{ch}} = \int \frac{-dt}{C(R_1 + R_2)}$ $\Rightarrow \ln V_{ch} = -\frac{t}{C(R_1 + R_2)} + \text{constant}$

$$V_{ch}(t) = Ae^{-t/C(R_1 + R_2)} \text{ and } V_c(t) = V_m + Ae^{-t/C(R_1 + R_2)}$$

Have 2 cases with different initial conditions

after each transition $\pm V = V_m + A$

$$\text{And } A_1 = -V - V_m \text{ when } V_m(t) = V \Rightarrow A_1 = -2V$$

$$A_2 = V - V_m \text{ when } V_m(t) = -V \Rightarrow A_2 = 2V$$

$$V_c(t) = \begin{cases} V(1 - 2e^{-t/C(R_1 + R_2)}) & \text{for } V_m(t) = V \\ V(-1 + 2e^{-t/C(R_1 + R_2)}) & \text{for } V_m(t) = -V \end{cases}$$

(where t is time since last transition)

More Problem 6.2

(B) $i_c(t) = C \frac{dV_L(t)}{dt}$ using $V_L(t) = \begin{cases} V(1 - 2e^{-t/\tau}), & v_m(t) = V \\ V(-1 + 2e^{-t/\tau}), & v_m(t) = -V \end{cases}$

$$i_c(t) = \begin{cases} \frac{2CV}{\tau} e^{-t/\tau} & \text{for } v_m(t) = V \\ -\frac{2CV}{\tau} e^{-t/\tau} & \text{for } v_m(t) = -V \end{cases}$$

(where t is time since last transition)

$\tau = C(R_1 + R_2)$

(C) $v_{out}(t) = i_c(t) \cdot R_2$

$$v_{out}(t) = \begin{cases} \frac{2R_2 CV}{\tau} e^{-t/\tau}, & \text{for } v_m(t) = V \\ -\frac{2R_2 CV}{\tau} e^{-t/\tau}, & \text{for } v_m(t) = -V \end{cases}$$

(where t is time since last transition and)

$\tau = C(R_1 + R_2)$

(D) Multiple ways to do this - reaches steady state

$5\tau \approx 1ms \Rightarrow \tau \approx 250 \mu sec.$

This agreed with value from extending initial slope to 0 crossing and finding $\tau = 5t$

(E) from (C) $v_{out, max} = \frac{2R_2 CV}{\tau(R_1 + R_2)} = \frac{R_2(2V)}{R_1 + R_2} = \frac{R_2(V_{high} + V_{low})}{R_1 + R_2}$ (since V_m is not very accurate)

$R_2 = 3k\Omega$



$$\left(\frac{-288.9 mV}{(-1,265 - 1,072) mV} \right) (R_1) = 3k\Omega \left[1 - \left(\frac{288.9}{1265 + 1072} \right) \right] \Rightarrow R_1 \approx 21 k\Omega$$

(F) $\tau = C(R_1 + R_2) \Rightarrow C = \frac{\tau}{R_1 + R_2} = \frac{250 \times 10^{-6} \text{ sec.}}{24 \times 10^3 \Omega} \Rightarrow C = 12 nF$

Q

Configuration Measurement Setups Results Help


RC Circuit

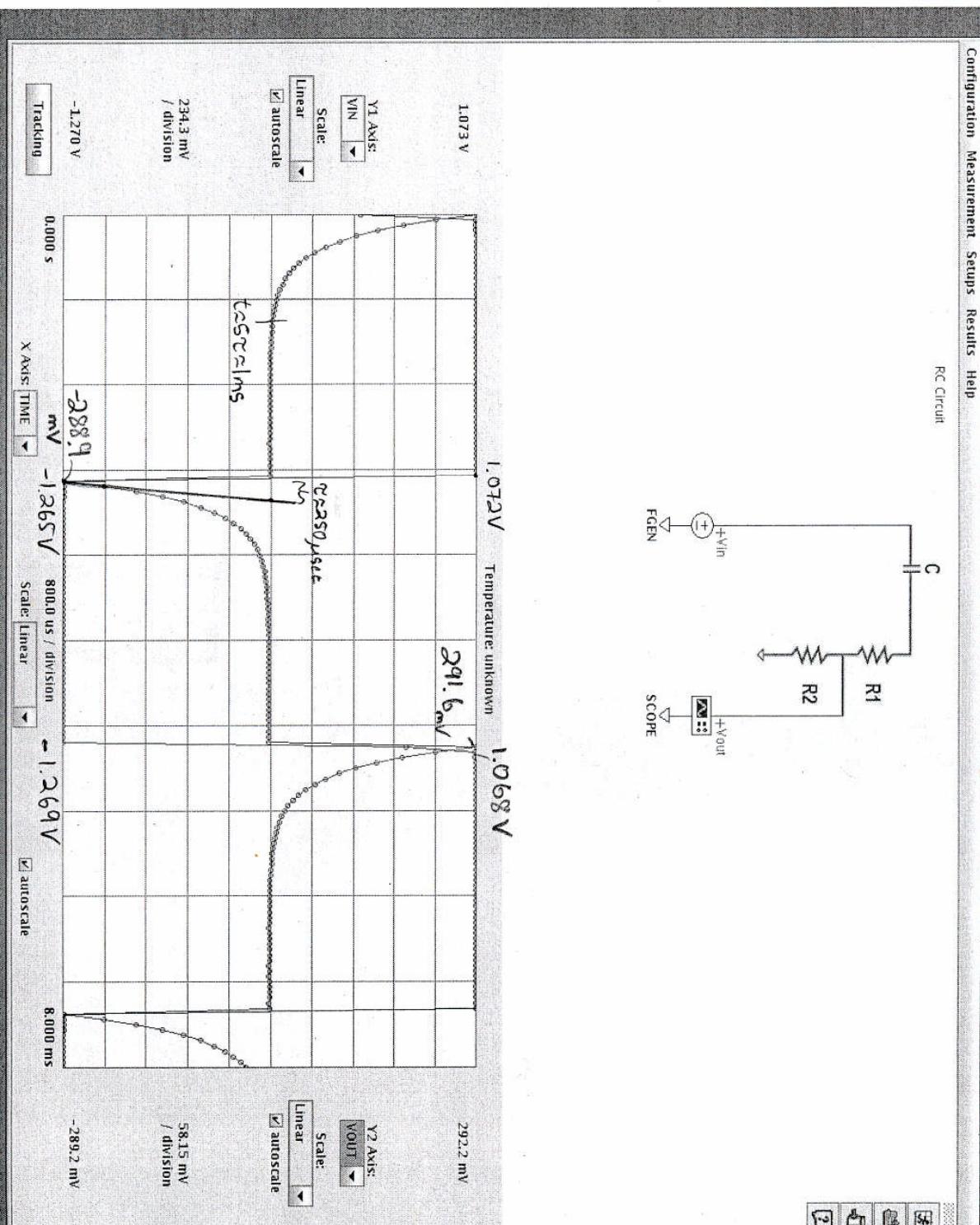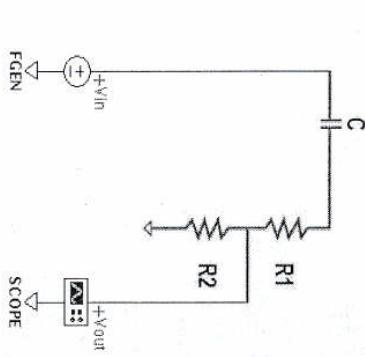

Problem 6.3

10

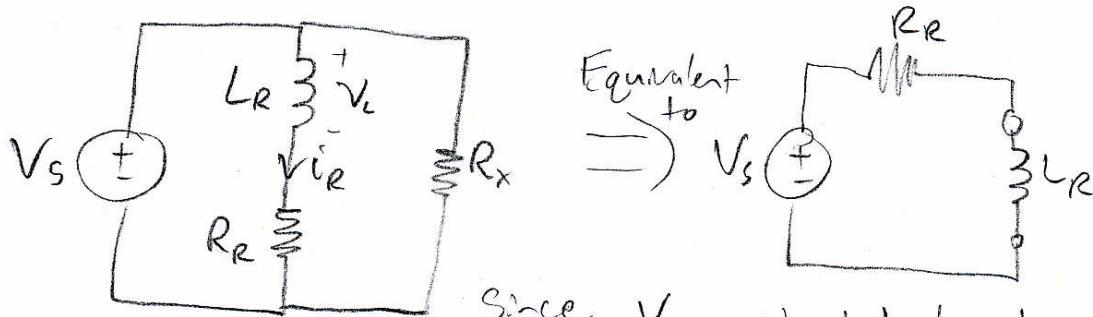(A) given $i_R(t=0)=0$, find $i_R(t)$ with MOSFET on:



Since V_{TH} at inductor terminals = V_s ,
 $R_{TH} = R_R$, and $I_{SC} = \frac{V_s}{R_R}$.

In this case,

R_x has no impact on the voltage across or current thru L_R .

$$KVL: V_s - V_L - i_R R_R = 0 \quad \text{and} \quad V_L = L_R \frac{di_R}{dt}$$

$$V_s - L_R \frac{di_R}{dt} - i_R R_R = 0 \quad \text{or} \quad \frac{di_R}{dt} + i_R \frac{R_R}{L_R} = \frac{V_s}{L_R}$$

And the total solution is the combination of a particular and a homogeneous solution:

$$i_R(t) = i_{R_p}(t) + i_{R_H}(t)$$

the particular solution is a constant where

$$i_{R_p} - \frac{R_R}{L_R} i_{R_p} = \frac{V_s}{L_R} \Rightarrow i_{R_p}(t) = \frac{V_s}{R_R}$$

Problem 6.3 (continued)

(A) Homogeneous Part: $\frac{di_{RH}(t)}{dt} + i_{RH}(t) \frac{R_E}{L_R} = 0$

$$\int \frac{di_{RH}}{i_{RH}} = -\int \frac{R_E}{L_R} dt \Rightarrow \ln i_{RH} = -t \cdot \frac{R_E}{L_R} + \text{constant}$$

$$i_{RH} = e^{-t/R_E} e^{\text{const}} = A e^{-t/R_E} \text{ where } \tau = \frac{L_R}{R_E}$$

Total solution $i_E(t) = \frac{V_S}{R_E} + A e^{-t/R_E}$ use initial condition to find A:

$$i_E(t=0) = 0 = \frac{V_S}{R_E} + A \Rightarrow A = -\frac{V_S}{R_E}$$

$$\boxed{i_E(t) = \frac{V_S}{R_E} \left(1 - e^{-t \cdot \frac{R_E}{L_R}} \right)} \quad A \text{ for } t \geq 0$$


(B) New "initial" condition at $t=T$: $i_E(t=T) = i_E(t=0)$ from (A)

Since $i_E(t)$ must be continuous

$$i_E(t=T) = \frac{V_S}{R_E} \left(1 - e^{-T/R_E} \right) = i_0 \text{ where } T_1 = \frac{L_R}{R_E}$$

With MOSFET OPEN: L_R will supply a current thru

the 2 resistors that decays to zero

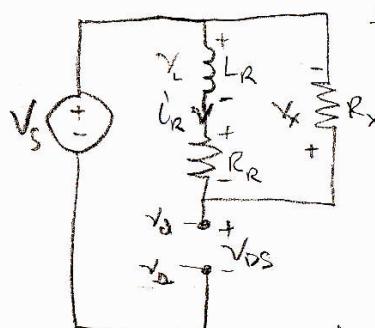

$$\text{KVL: } V_L + i_E(R_E + R_X) = 0$$

$$\underline{\frac{di_E}{dt} + i_E(R_E + R_X) = 0}$$

and for V_{DS} : $V_A - V_X - V_S = V_{DS}$ with $V_{DS} = V_A - V_Z$

$$\underline{V_{DS} = V_X + V_S}$$

More Problem 6.3

12

$$(B) \text{ Solving } \frac{di_R}{dt} = \frac{-(R_R + R_x)dt}{L_R}$$

there are no source terms,
so it's just the homogeneous part,
 $i_{R_p}(t) = 0$

$$\ln i_R = -t \frac{(R_R + R_x)}{L_R} + \text{constant} \quad \text{and} \quad i_R = A e^{-t/\tau_2}, \quad \tau_2 = \frac{L_R}{R_R + R_x}$$

Apply initial condition to solve for A, but now
the "initial" condition and switching occur at

$t = T$, not $t = 0$, so solution for i_R must be
shifted $t \rightarrow (t - T)$

$$i_R(t=T) = i_0 = A e^{-(T-T)/\tau_2} = A, \quad A = i_0$$

$$i_R(t) = i_0 e^{-(t-T)/\tau_2}, \quad i_0 = \frac{V_0}{R_R} \left(1 - e^{-T \frac{R_R}{L_R}}\right)$$

$$i_R(t) = \frac{V_0}{R_R} \left(1 - e^{-T \frac{R_R}{L_R}}\right) e^{-\frac{(t-T)(R_R + R_x)}{L_R}} \quad A \text{ for } t \geq T$$


$$V_{DS}(t) = V_S - V_{Rx} = V_S - i_R(t) \cdot R_x$$

$$V_{DS}(t) = V_S - \frac{V_S R_x}{R_R} \left(1 - e^{-T \frac{R_R}{L_R}}\right) e^{-\frac{(t-T)(R_R + R_x)}{L_R}} \quad V \text{ for } t \geq T$$


More Problem 6.3

13

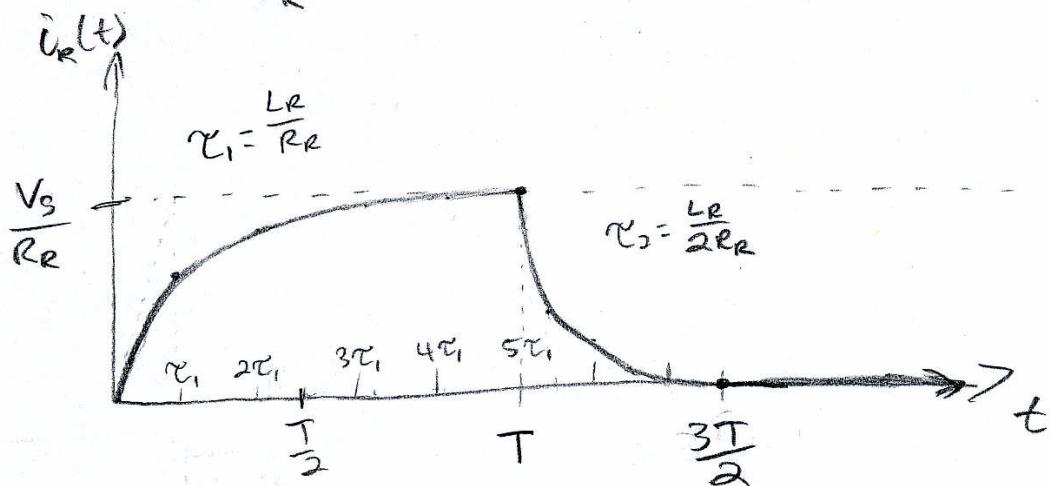- (C) i_R starts at zero, rises towards $\frac{V_s}{R_R}$ until $T = 5\tau_1 = 5\tau_i$ at 5 the constants $i_R \approx \frac{V_s}{R_R}$, then decays to zero with a time constant $\tau_2 = \frac{L_R}{2R_R}$, half as large, so twice as fast



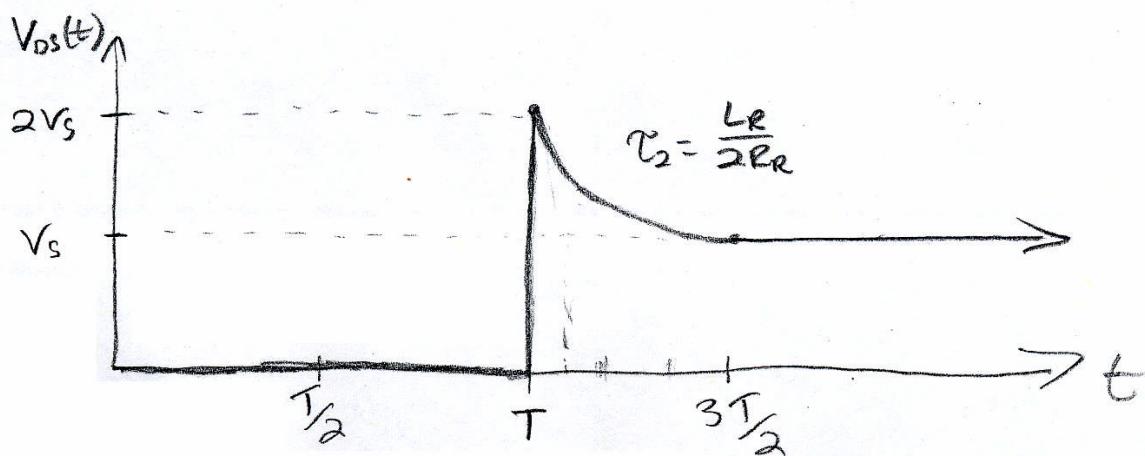If the MOSFET is an ideal switch, $V_{ds} = 0$ for $t < T$, then switches up to $V_{ds} = V_s + i_R \cdot R_L = V_s + \frac{V_s}{R_R} \cdot R_L = 2V_s$ then decays down to V_s with the same time constant and curve as $i_R(t)$:



End of Problem 6.3

14

- (D) A complete circuit loop is needed to provide a current path after the MOSFET opens.

The current in the inductor must be continuous so if R_x were removed, as soon as the MOSFET tried to open and instantly switch

the inductor current to zero, the inductor voltage would approach infinity according to

$$V_L = L \frac{di}{dt}$$

as the finite i turned off over a very small dt . The rising V_{DS} from the inductor could increase above the rated breakdown voltage of the MOSFET and force it to conduct, destroying the switch.

Problem 6.4

- (A) For the inductor circuit, $R_{TH_L} = R_1 + R_2$ and $I_{SC_L} = I(t) \cdot \frac{R_1}{R_1 + R_2}$

For the capacitor circuit: $R_{TH_C} = \frac{R_1 \cdot R_2}{R_1 + R_2}$ and $V_{TH_C} = V(t) \cdot \frac{R_2}{R_1 + R_2}$

But know $V_L = L \frac{di_L}{dt}$ and $i_C = C \frac{dv_C}{dt}$ so simpler

to use a series circuit for the inductor and a parallel circuit for the capacitor


$$\text{and } V_{TH_L} = I_{SC_L} \cdot R_{TH_L} = R_1 \cdot I(t)$$

$$\text{and } I_{NC} = \frac{V_{TH_C}}{R_{TH_C}} = \frac{V(t)}{R_1}$$

Problem 6.4 (continued)

15

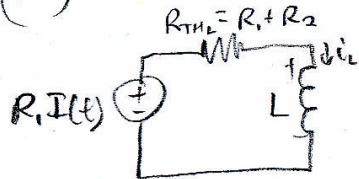
(A) For Inductor: $KVL: R_1 I(t) - i_L (R_1 + R_2) = V_L = L \frac{di_L}{dt}$



$$\frac{di_L}{dt} + i_L \frac{(R_1 + R_2)}{L} = \frac{R_1 I(t)}{L}$$

For Capacitor:
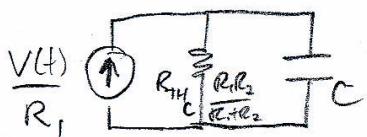
$$KCL: \frac{V(t)}{R_1} = \frac{V_c}{R_{Th_C}} + i_C \Rightarrow \frac{V(t)}{R_1} = \frac{V_c (R_1 + R_2)}{R_1 R_2} + C \frac{dV_c}{dt}$$



$$\frac{dV_c}{dt} + V_c \frac{(R_1 + R_2)}{R_1 R_2 C} = -\frac{V(t)}{R_1 C}$$

(B) At $t = \infty$, both circuits will be in steady state, with $\frac{di_L}{dt} = 0$ and $\frac{dV_c}{dt} = 0$, nothing changing, the inductor acting as a short circuit and the capacitor open:

$$i_C(t=\infty) = 0 \text{ and } V_L(t=\infty) = 0$$

and the initial charge and flux delivered by the impulse sources has bled out through the resistors

Problem 6.4 (continued)

16

(B) (continued) to find $i_L(t=0^+)$ and $V_C(t=0^+)$, integrate the differential equation from $t=0^-$ to $t=0^+$.

$$\int_{0^-}^{0^+} di + \int_{0^-}^{0^+} i_L(t) \frac{(R_1+R_2)}{L} dt = \int_{0^-}^{0^+} \frac{R_1 Q}{L} \delta(t) dt$$

$$\int_{0^-}^{0^+} dV + \int_{0^-}^{0^+} V_C(t) \frac{(R_1+R_2)}{R_1 R_2 C} dt = \int_{0^-}^{0^+} \frac{1}{R_1 C} \delta(t) dt$$

If $i_L(t)$ and $V_C(t)$ remain finite, then the integrals of these finite values over zero time go to zero. Even though the $I(t)$ and $V(t)$ from the impulse sources may be infinite values, forcing the inductor voltage and capacitor current to infinite values, we know that the sources still deliver only a finite amount of charge, A in this case, and flux, Q here, to the inductor and capacitor. With finite charge and flux, the capacitor voltage, $V_C(t)$, and inductor current, $i_L(t)$ must remain finite. So the second terms above $\rightarrow 0$ and left with:

$$i_L(t=0^+) - i_L(t=0^-) + 0 = \frac{R_1}{L} Q \quad \text{with } i_L(t=0^-) = 0$$

$$V_C(t=0^+) - V_C(t=0^-) + 0 = \frac{1}{R_1 C} \quad \text{with } V_C(t=0^-) = 0$$

$i_L(t=0^+) = \frac{R_1}{L} Q$ and $V_C(t=0^+) = \frac{1}{R_1 C}$

Problem 6.4

17

(C) From the Thvenin and Norton equivalents,

$$\tau_L = \frac{L}{R_{TH_L}} \quad \text{and}$$

$$\tau_C = R_{TH_C} C$$

$$\boxed{\tau_L = \frac{L}{R_1 + R_2}}$$

$$\boxed{\tau_C = \frac{R_1 R_2}{R_1 + R_2} C}$$

(D) Know initial and final values and time constants for exponential decay: Using values at $t=0^+$, after sources act, for initial values:

$$V_c(t) = V_c(t=0^+) e^{-t/\tau_C} \quad \text{and} \quad i_L(t) = i_L(t=0^+) e^{-t/\tau_L}$$

$$\boxed{V_c(t) = \frac{1}{R_1 C} e^{-t/(R_1 R_2 / (R_1 + R_2))} C}$$

$$\boxed{i_L(t) = \frac{R_1 Q}{L} e^{-t/(R_1 R_2 / (R_1 + R_2))}} \quad t \geq 0$$

(E) Plugging back into differential equation: first for inductor:

$$\frac{i_L(t=0^+)}{-\tau_L} e^{-t/\tau_L} + \frac{i_L(t=0^+) e^{-t/\tau_L}}{\tau_L} = \frac{R_1 Q \delta(t)}{L} = 0 \quad \text{for all } t > 0$$

and for capacitor:

$$-\frac{V_c(t=0^+)}{\tau_C} e^{-t/\tau_C} + \frac{V_c(t=0^+) e^{-t/\tau_C}}{\tau_C} = \frac{A \delta(t)}{R_1 C} = 0 \quad \text{for all } t > 0$$

The first 2 terms cancel out in both, to be true for all t , $V_c(t)$ and $i_L(t)$ should both include a step function $u(t)$