

# Problem Set #6

1. Since  $V_{BS} = -1$  first we need to find the new threshold voltage ( $V_{Tn}$ )

$$V_{Tn} = V_{Ton} + \gamma_n (\sqrt{-2\phi_p - V_{BS}} - \sqrt{-2\phi_p}) \\ = 1\text{v} + 0.6 (\sqrt{0.84+1} - \sqrt{0.84}) = 1.26\text{v}$$

Since  $V_{GS} = 3\text{v}$  is bigger than  $V_{Tn} = 1.26\text{v}$  and  $V_{DS} = 5\text{v}$  is bigger than  $V_{GS} - V_{Tn} = 1.74\text{v}$ , the nMOS is in saturation, as expected.

Note that channel length modulation is ignored to make the calculations simpler

$$I_D = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_{Tn})^2 = \frac{22}{2 \times 1.8} 50 \frac{\mu\text{A}}{\text{v}^2} (3\text{v} - 1.26\text{v})^2 = 925 \mu\text{A}$$

note that  $L = L_{gate} - 2L_D = 2.0\text{ }\mu\text{m} - 0.2\text{ }\mu\text{m} = 1.8\text{ }\mu\text{m}$

a)

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D} = \sqrt{2 \frac{22}{1.8} 50 \times 10^{-6} \times 925 \times 10^{-6}} = 1063 \mu\text{s}$$

$$g_{mb} = \frac{\gamma_n g_m}{2\sqrt{-2\phi_p - V_{BS}}} = \frac{0.6 \times 1063 \times 10^{-6}}{2\sqrt{0.84 + 1}} = 235 \mu\text{s}$$

$$g_o = \frac{1}{r_o} = \lambda_n I_D = \frac{0.1}{1.8} \times 925 \times 10^{-6} = 51 \mu\text{s} \Rightarrow r_o = 19.5 \text{ k}\Omega$$


b)  $C_{gs} = \frac{2}{3} WL C_{ox} + WC_{ov} \approx \frac{2}{3} WL C_{ox} + WL_D C_{ox} = \left(\frac{2}{3}L + L_D\right) WC_{ox}$   
 $= \left(\frac{2}{3} 1.8\text{ }\mu\text{m} + 0.1\text{ }\mu\text{m}\right) 22\text{ }\mu\text{m} \times 1.42 \text{ FF}/\mu\text{m}^2 = 40.6 \text{ FF}$

$$C_{gd} = WC_{ov} \approx WL_D C_{ox} = 22\text{ }\mu\text{m} \times 0.1\text{ }\mu\text{m} \times 1.42 \text{ FF}/\mu\text{m}^2 = 3.1 \text{ FF}$$




$$C_{sb} = WL_{diff} \sqrt{\frac{q\epsilon_s Na}{2(\phi_B - V_{BS})}} = 22\text{ }\mu\text{m} \times 6\text{ }\mu\text{m} \sqrt{\frac{1.6 \times 10^{-19} \times 11.7 \times 8.85 \times 10^{-14} \times 10^{17}}{2(0.97 + 1)}} \\ = 85.6 \text{ FF}$$

$$C_{db} = WL_{diff} \sqrt{\frac{q\epsilon_s Na}{2(\phi_B - V_{BD})}} = 22\text{ }\mu\text{m} \times 6\text{ }\mu\text{m} \sqrt{\frac{1.6 \times 10^{-19} \times 11.7 \times 8.85 \times 10^{-14} \times 10^{17}}{2(0.97 + 6)}} \\ = 45.5 \text{ FF}$$

2.

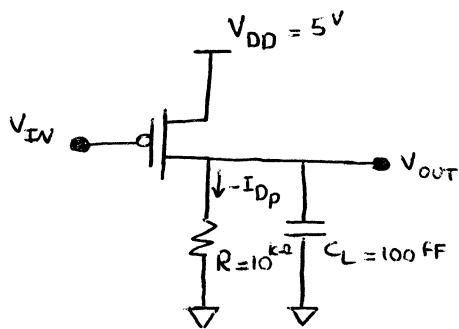


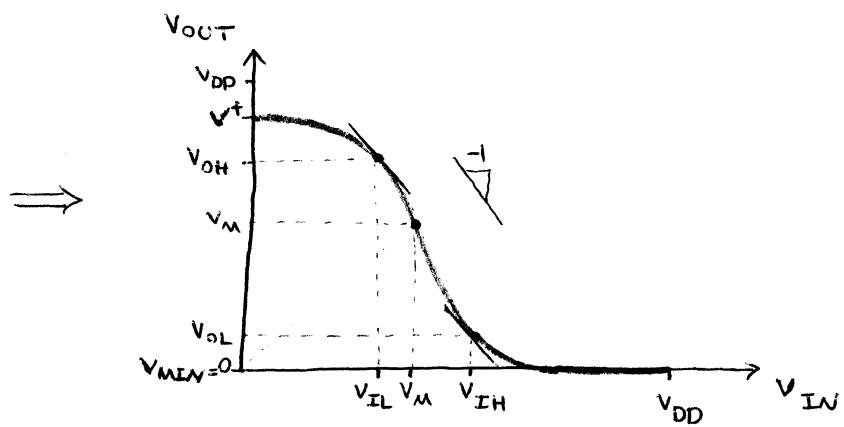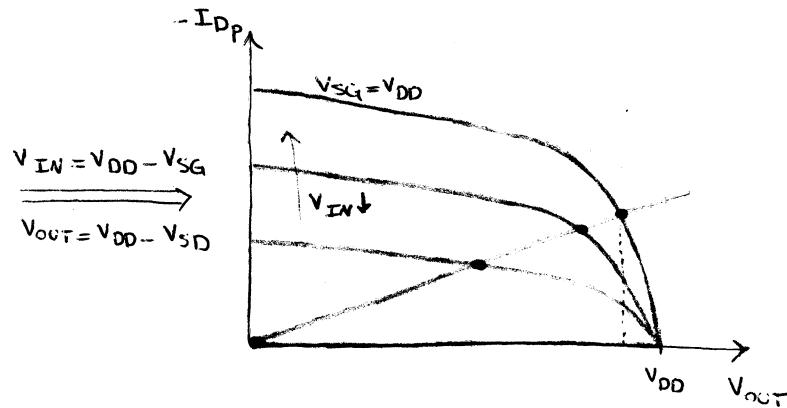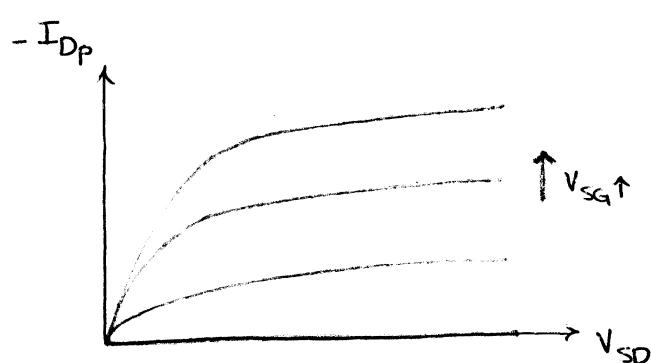a) The voltage transfer characteristic can be calculated from drain characteristics of the pMOS:



notice  $V^+ < V_{DD}$  and  $V_{MIN} = 0V$

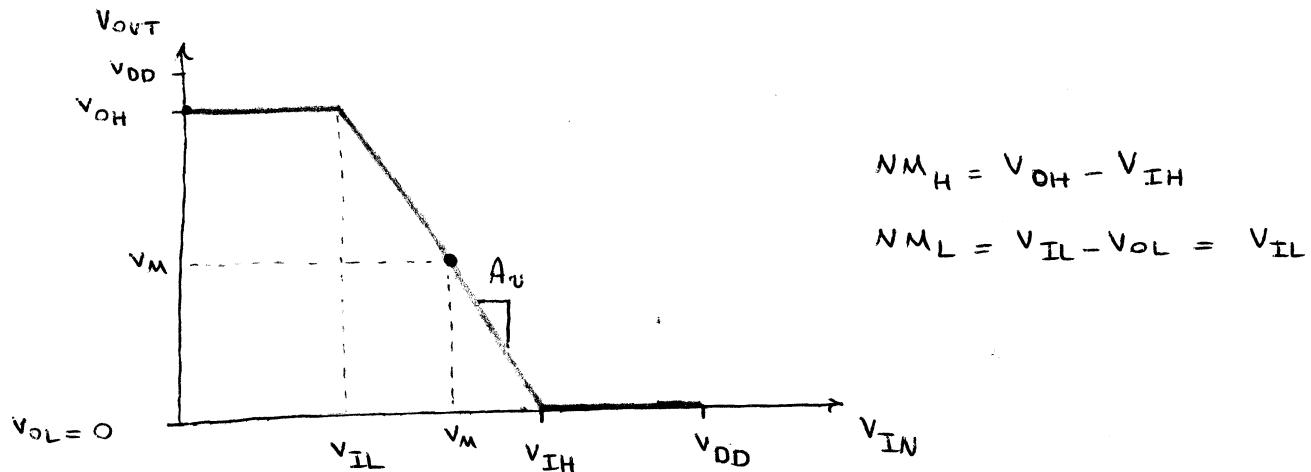b) In the simplified model the transfer characteristics is approximated by a piecewise linear function:



at  $V_{IN} = V_M$ , where  $V_{OUT} = V_M$ , the pMOS is in saturation, there :

$$-I_{Dp} = \frac{W}{2L} \mu_p C_{ox} (V_{SG} + V_{Tp})^2 = I_R = \frac{V_{OUT}}{R}$$

$$\Rightarrow \frac{W}{2L} \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2 = \frac{V_M}{R}$$

$$\Rightarrow \frac{20}{2 \times 1} 25 \times 10^{-6} (5 - V_M - 1)^2 = \frac{V_M}{10^4} \Rightarrow V_M^2 - 8.4 V_M + 16 = 0 \\ \Rightarrow V_M = 2.9 \text{ V}$$

Also  $-I_{Dp} = I_R = \frac{V_M}{R} = \frac{2.9 \text{ v}}{10 \text{ k}\Omega} = 290 \mu\text{A}$

therefore  $g_m = \sqrt{2 \frac{W}{L} \mu_p C_{ox} (-I_D)} = \sqrt{2 \frac{20}{1} 25 \times 10^{-6} \times 290 \times 10^{-6}}$   
 $= 539 \mu\text{s}$

so  $A_v = -g_m (r_o \parallel R) \approx -g_m R = -5.39$

By knowing  $V_M$  and  $A_v$  we can calculate  $V_{IH}$ :

$$V_{IH} = V_M - \frac{V_M}{A_v} = 2.9^V + \frac{2.9^V}{5.39} = \underline{\underline{3.4^V}}$$

To figure out  $V_{OH}$  we need to write down the equation for drain current at  $V_{IN}=0$  ( $V_{OUT}=V_{OH}$ ). since the pMOS is in triode regime at this point:

$$\frac{W}{L} \mu_p C_{ox} (V_{SG} + V_{Tp} - \frac{V_{SD}}{2}) V_{SD} = \frac{V_{OUT}}{R}$$

$$\Rightarrow \frac{W}{L} \mu_p C_{ox} (V_{DD} + V_{Tp} - \frac{V_{DD} - V_{OH}}{2}) (V_{DD} - V_{OH}) = \frac{V_{OH}}{R}$$

$$\Rightarrow \frac{W}{2L} \mu_p C_{ox} (V_{DD} + 2V_{Tp} + V_{OH}) (V_{DD} - V_{OH}) = \frac{V_{OH}}{R}$$

$$\Rightarrow \frac{20}{2 \times 1} 25 \times 10^{-6} (5 - 2 + V_{OH}) (5 - V_{OH}) = \frac{V_{OH}}{10^4}$$

$$\Rightarrow V_{OH}^2 - 1.6 V_{OH} - 15 = 0 \Rightarrow \underline{\underline{V_{OH} = 4.8^V}}$$

therefore

$$V_{IL} = \frac{1-A_v}{-A_v} V_M - \frac{V_{OH}}{-A_v} = \frac{1+5.39}{5.39} 2.9 - \frac{4.8}{5.39} = \underline{\underline{2.5^V}}$$

Finally

$$NM_H = V_{OH} - V_{IH} = 4.8 - 3.4 = 1.4^V$$

$$NM_L = V_{IL} - V_{OL} = 2.5 - 0 = \underline{\underline{2.5^V}}$$

c)

$$\begin{aligned}
 C_{DB} &= WL_{diff} C_{jp} + (W + 2L_{diff}) C_{JSSWp} \\
 &= 22 \mu\text{m} \times 6 \mu\text{m} \times 0.3 \frac{\text{FF}}{\mu\text{m}^2} + (22 \mu\text{m} + 12 \mu\text{m}) \times 0.35 \frac{\text{FF}}{\mu\text{m}} \\
 &= 51.5 \text{ FF}
 \end{aligned}$$

$$C_{Total} = (C_L \parallel C_{DB}) = C_L + C_{DB} = 100 + 51 = 151 \text{ FF}$$

$$t_{PLH} = RC_{Total} \ln(2) = 10^4 \times 151 \times 10^{-15} \ln(2) = 1.05 \text{ nsec}$$

$$t_{PHL} = RC_{Total} \ln \left( \frac{-2I_D R}{-2I_D R - V_{DD}} \right) \quad \text{where } -I_D = 290 \mu\text{A}$$


(From part (b))

$$\Rightarrow t_{PHL} = 10^4 \times 151 \times 10^{-15} \ln \left( \frac{2 \times 290 \times 10^{-6} \times 10^4}{2 \times 290 \times 10^{-6} \times 10^4 - 5} \right) = 2.99 \text{ nsec}$$

- d) Static power dissipation is due to the power consumed by the pull down resistor when  $V_{out}$  is high ( $V_{OH}$ )

$$P_{diss} = \frac{V_{OH}^2}{R} = \frac{(4.8)^2}{10^4} = 2.3 \times 10^{-3} \text{ J/S}$$

3.

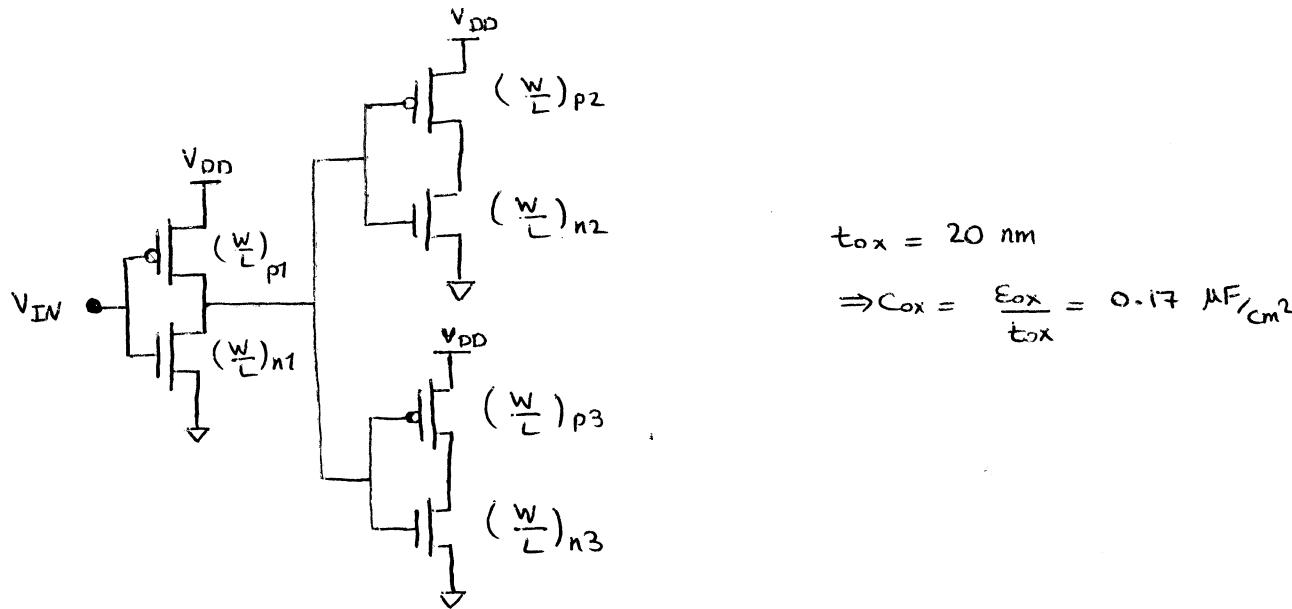

$$t_{ox} = 20 \text{ nm}$$

$$\Rightarrow C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 0.17 \text{ } \mu\text{F/cm}^2$$

a)

$$V_M = \frac{V_{Tn} + \sqrt{\frac{k_p}{k_n} (V_{DD} + V_{Tp})}}{1 + \sqrt{\frac{k_p}{k_n}}}$$

$$\Rightarrow \frac{k_p}{k_n} = \left( \frac{V_M - V_{Tn}}{V_{DD} + V_{Tp} - V_M} \right)^2 = \left( \frac{2.5 - 0.7}{5 - 0.9 - 2.5} \right)^2 = 1.26$$

$$\frac{w_n}{w_p} = \frac{\mu_p}{\mu_n} \frac{k_n}{k_p} = \frac{200}{500} \frac{1}{1.26} = 0.32$$

b)

$$I_{Dn} = \left( \frac{W}{2L} \right)_n \mu_n C_{ox} (V_M - V_{Tn})^2 \Rightarrow$$

$$1 \text{ mA} = \frac{w_n}{2 \times 2 \mu\text{m}} 500 \times 0.17 \times 10^{-6} (2.5 - 0.7)^2 \Rightarrow w_n = 14.5 \mu\text{m}$$

$$-I_{Dp} = \left( \frac{W}{2L} \right)_p \mu_p C_{ox} (V_{DD} - V_M + V_{Tp})^2 \Rightarrow$$

$$1 \text{ mA} = \frac{w_p}{2 \times 2 \mu\text{m}} 200 \times 0.17 \times 10^{-6} (5 - 2.5 - 0.9)^2 \Rightarrow w_p = 46.0 \mu\text{m}$$

$$\begin{aligned}
 c) \quad C_{DB} &= W_n L_{diff,n} C_{jn} + (W_n + 2L_{diff,n}) C_{JSW_n} + W_p L_{diff,p} C_{jp} + (W_p + 2L_{diff,p}) C_{JSW_p} \\
 &= 14.5 \mu\text{m} \times 6 \mu\text{m} \times 0.1 \text{ FF}/\mu\text{m}^2 + (14.5 \mu\text{m} + 12 \mu\text{m}) 0.5 \text{ FF}/\mu\text{m} \\
 &\quad + 46.0 \mu\text{m} \times 6 \mu\text{m} \times 0.3 \text{ FF}/\mu\text{m}^2 + (46.0 \mu\text{m} + 12 \mu\text{m}) 0.35 \text{ FF}/\mu\text{m} \\
 &= \underline{125 \text{ FF}}
 \end{aligned}$$

d) Since the source acting as ground for the four nMOS and pMOS in the second stage:

$$\begin{aligned}
 C_L &= 2C_{gS,n} + 2C_{gS,p} \approx 2 \left( \frac{2}{3} W_n L C_{ox} + \frac{2}{3} W_p L C_{ox} \right) \\
 &= 2 \left( \frac{2}{3} \times 14.5 \mu\text{m} \times 2 \mu\text{m} \times 0.17 \frac{\text{MF}}{\text{cm}^2} + \frac{2}{3} \times 46.0 \mu\text{m} \times 2 \mu\text{m} \times 0.17 \frac{\text{MF}}{\text{cm}^2} \right) \\
 &= \underline{274 \text{ FF}}
 \end{aligned}$$

$$\begin{aligned}
 e) \quad t_{PLH} &\approx \frac{C_{total} V_{DD}}{\frac{W_p}{L_p} \mu_p C_{ox} (V_{DD} + V_{T_p})^2} = \frac{(125 \text{ FF} + 274 \text{ FF}) 5 \text{ V}}{\frac{46}{2} 200 \times 0.17 \times 10^{-6} (5 - 0.9)^2} \\
 &= \underline{152 \text{ p sec}}
 \end{aligned}$$

$$\begin{aligned}
 t_{PHL} &\approx \frac{C_{total} V_{DD}}{\frac{W_n}{L_n} \mu_n C_{ox} (V_{DD} - V_{T_n})^2} = \frac{(125 \text{ FF} + 274 \text{ FF}) 5 \text{ V}}{\frac{14.5}{2} 500 \times 0.17 \times 10^{-6} (5 - 0.7)^2} \\
 &= \underline{175 \text{ psec}}
 \end{aligned}$$

4.

a) The graph for transistor output characteristics is on next page.

b) For small  $V_{DS}$  and  $V_{BS} = 0$ :

$$I_D = \frac{W}{L} \mu_n C_{ox} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \approx \frac{W}{L} K_P \left( V_{GS} - V_{T_{on}} \right) V_{DS}$$

Therefore  $K_P$  can be calculated from the slope of the graph in part (a) for the small  $V_{DS}$  region.

For high  $V_{DS}$  and  $V_{BS} = 0$ :

$$I_D = \frac{W}{2L} \mu_n C_{ox} \left( V_{GS} - V_T \right)^2 (1 + \lambda V_{DS})$$

$$= \left[ \frac{W}{2L} K_P \left( V_{GS} - V_{T_0} \right)^2 \right] + \left[ \frac{W}{2L} K_P \left( V_{GS} - V_{T_0} \right)^2 \lambda \right] V_{DS}$$

Therefore LAMBDA can be calculated from the slope of the graph in part (a) for high  $V_{DS}$  region.


Summary of results:


From pset #5

$$K_P = 33.5 \frac{\mu A}{V^2}, \quad \text{LAMBDA} = 0.058 V^{-1}$$

$$V_{TO} = 0.85 V, \quad \text{GAMMA} = 1.6 V^{1/2}, \quad \text{PHI} = 0.8 V$$

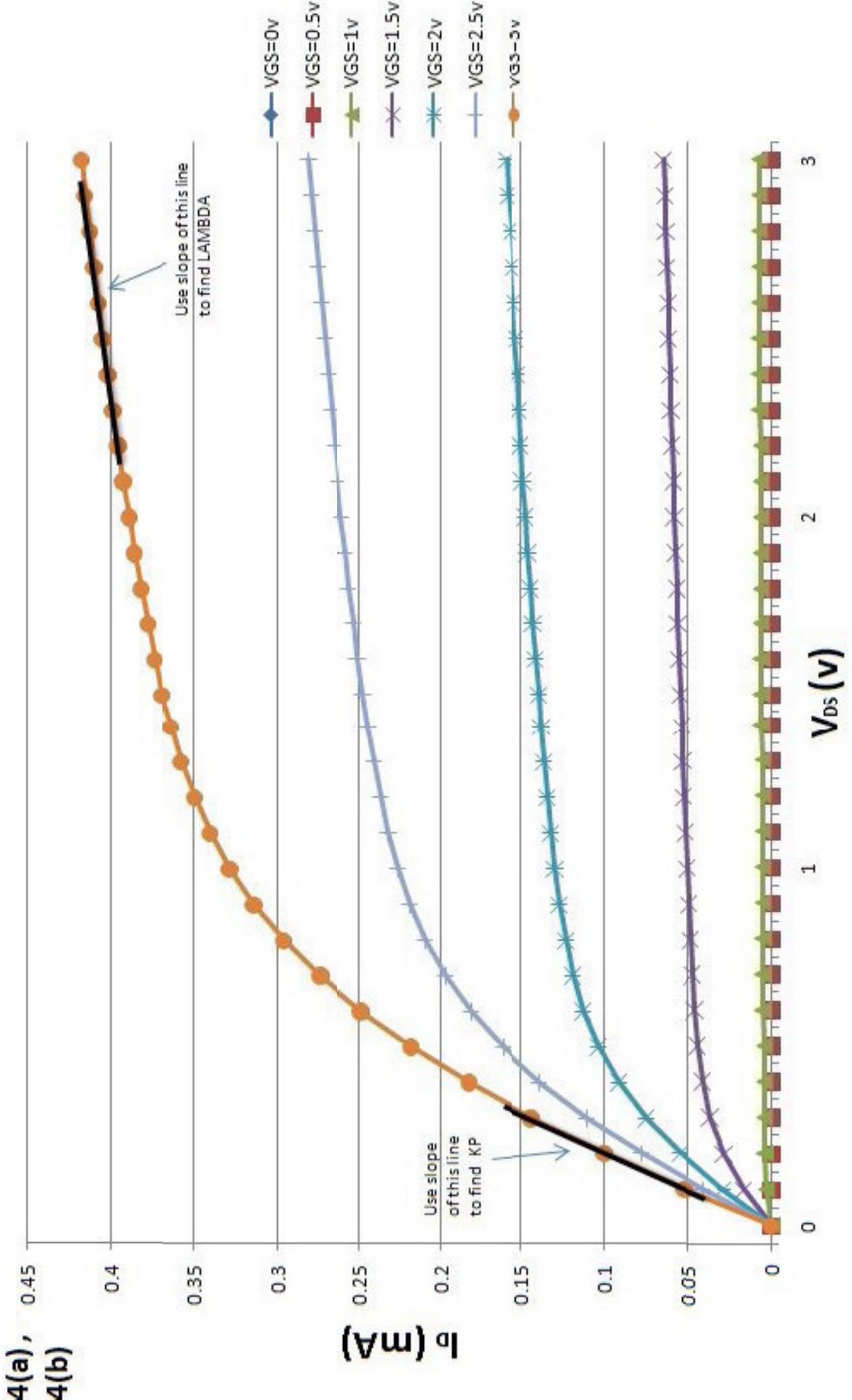c) Output characteristics ( $I_D$  vs  $V_{DS}$ ) and transfer characteristics ( $I_D$  vs  $V_{GS}$ ) is on next pages.



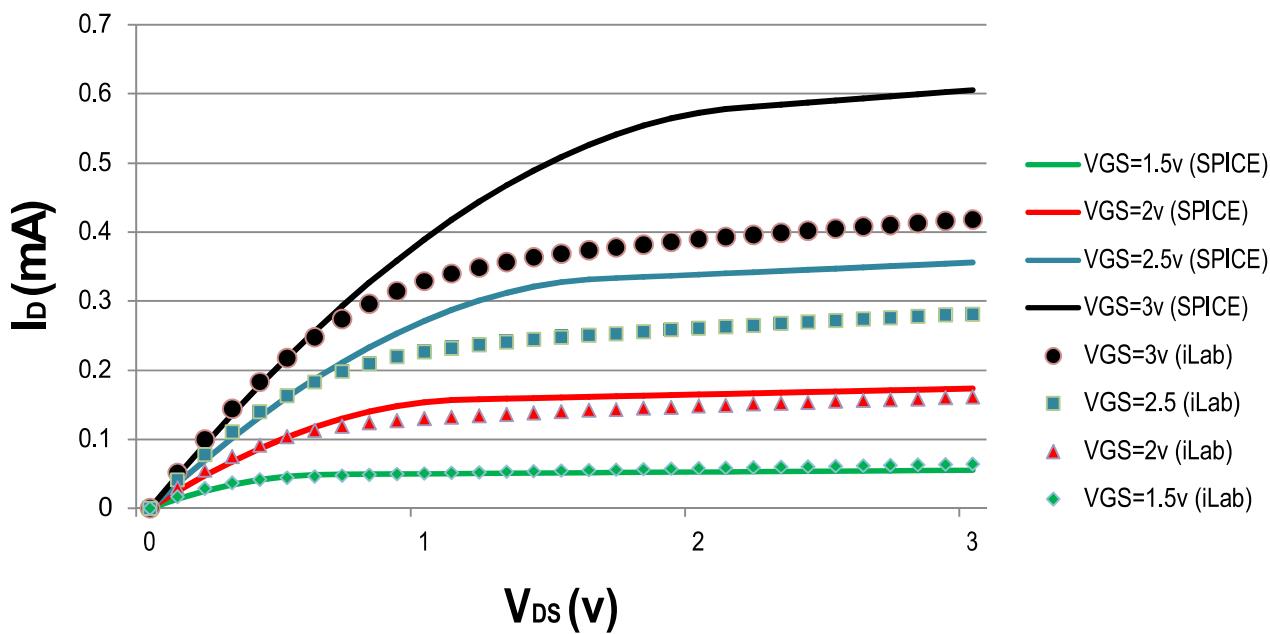**4(c)****4(c)**