
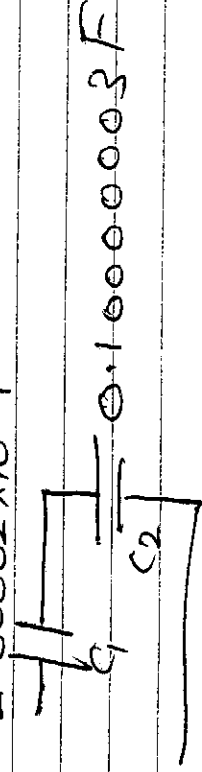


$$2.00002 \times 10^{-5} \text{ F}$$

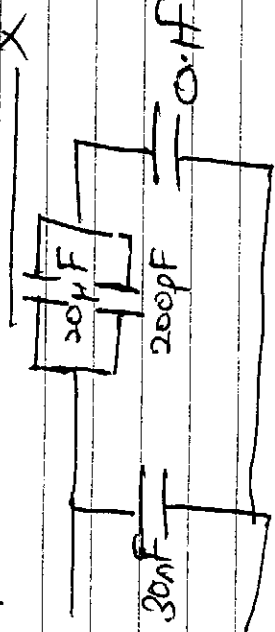


$$C_T = C_1 + C_2$$

$$C_T = 1.99962 \times 10^{-5} \text{ F}$$




$$2.00002 \times 10^{-5} \text{ F}$$

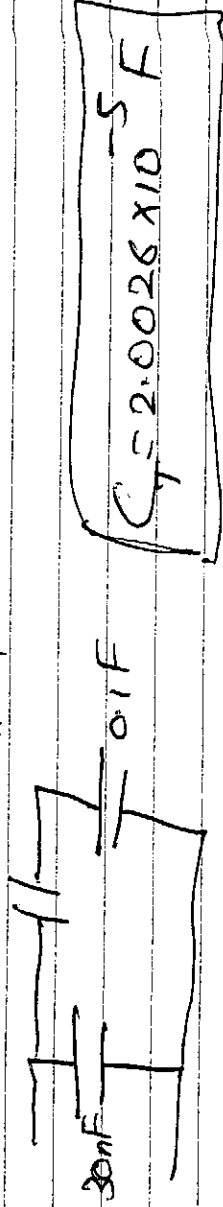

b)

2.

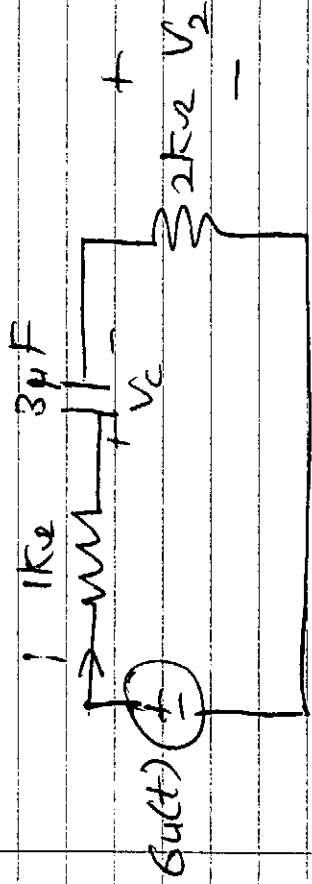

$$t < 0 \quad V_C = 0 \quad V_2 = 0$$

$$t > 0 \quad V_C = 6(1 - e^{-t/\tau}) \quad \tau = 3k\Omega \times 3\mu H = 9 \times 10^{-3} s$$

$$i = \frac{6}{3k} e^{-t/\tau}$$


$$-6 + 1k i + V_C + V_2 = 0$$

$$V_2 = 6 - V_C = 1k i$$


$$V_2 = 6 - 6(1 - e^{-t/\tau}) = 2e^{-t/\tau}$$

$$V_2 = 4e^{-t/\tau} \quad \tau = 9 \times 10^{-3} s$$

→ →

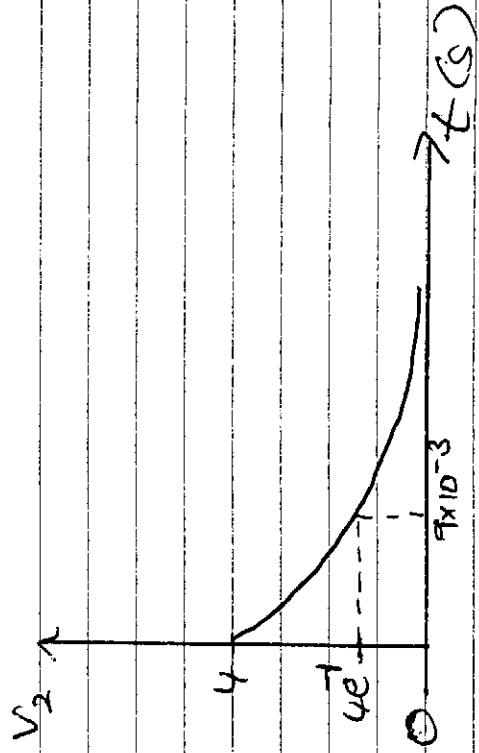

3a  $t < 0$  (switch closed)

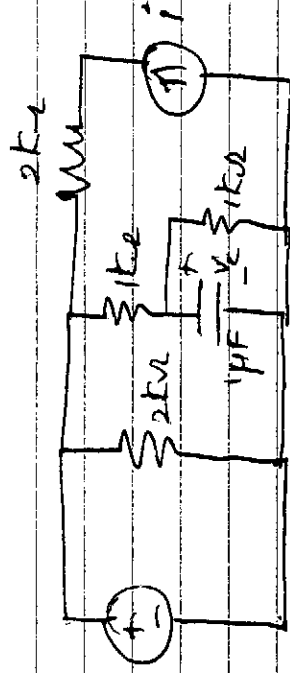

$$V_c = 2V$$

Thevenin resistance looking from capacitor



$$R = 0.5k\Omega$$


$$C = 1\mu F$$

$$\tau_2 = RC = 0.5ms$$


$$= 0.5 \times 10^{-3}s$$

$$V_1 = 2V$$

$t > 0$  (switch open)

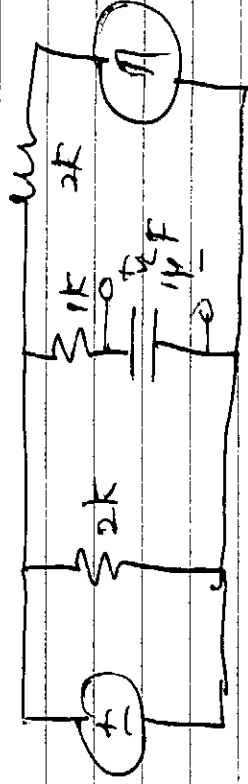

$R_{th}$

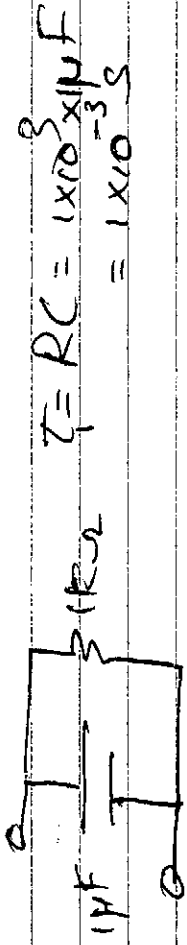


$$\tau = RC = 1 \times 10^{-3} \times 10^3 \mu F = 1 \times 10^{-3} s$$

$$\tau_1 = 1 \times 10^{-3} s$$

— X —

4. a)

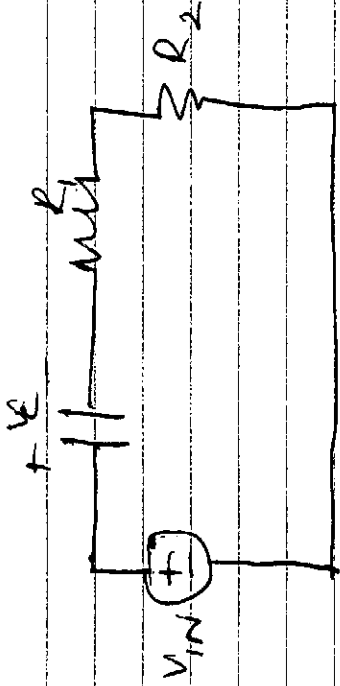

$$V_C(t) = V_{\text{initial}} e^{-t/\tau} + V_{\text{Final}} (1 - e^{-t/\tau})$$

if  $V_{IN}(t) = V$

$V_{\text{initial}} = -V$  since  $\tau > RC$   
 so capacitor has settled  
 to final voltage

$$V_C(t) = -V e^{-t/\tau} + V(1 - e^{-t/\tau})$$

$$V_C(t) = V(1 - 2e^{-t/\tau}) \quad \text{if } V_{IN}(t) = V$$

if  $V_{IN}(t) = -V$

$$V_C(t) = V e^{-t/\tau} - V(1 - e^{-t/\tau})$$

$$V_C(t) = -V(1 - 2e^{-t/\tau}) \quad \text{if } V_{IN}(t) = -V$$

$$\tau = (R_1 + R_2)C$$

b) if  $v_N(t) = V$

$$v_C(t) = V(1 - 2e^{-t/\tau})$$
$$\tau = (R_1 + R_2)C$$

$$i_C = C \frac{dv_C}{dt}$$

$$i_C = CV \frac{2}{\tau} e^{-t/\tau}$$

$$i_C = \frac{2V}{R_1 + R_2} e^{-t/\tau}$$

$$\tau = (R_1 + R_2)C$$

$$v_N = V$$

if  $v_N(t) = -V$

$$v_C(t) = -V(1 - 2e^{-t/\tau})$$

$$i_C = C \frac{dv_C}{dt}$$

$$= -CV \frac{2}{\tau} e^{-t/\tau}$$

$$i_C = \frac{-2V}{R_1 + R_2} e^{-t/\tau}$$

$$\tau = (R_1 + R_2)C$$

$$v_N = -V$$

— x —

c)  $V_{out} = i_c R_2$

if  $V_{in} = V$   $V_{out} = \frac{2VR_2}{R_1 + R_2} e^{-t/\tau}$   $\tau = (R_1 + R_2)C$

if  $V_{in} = -V$   $V_{out} = -\frac{2VR_2}{R_1 + R_2} e^{-t/\tau}$   $\tau = (R_1 + R_2)C$

— X —

d) from plot

$t = 0$   $V_{out} = 203.92 \times 10^{-3} V$

$t = 850 \times 10^{-6}$   $V_{out} = 16.98 \times 10^{-3} V$

$16.98 m = 203.92 m e^{-\frac{850 \times 10^{-6}}{\tau}}$

$\tau = 340 \mu s$

e)

$V_{out} = 174.59 mV$

$V_{in} = 1.069 V$

$t = 50 \times 10^{-6}$

$-\frac{50 \times 10^{-6}}{340 \times 10^{-6}}$

$174.59 m = 2 (1.069) 3k e^{-\frac{50 \times 10^{-6}}{340 \times 10^{-6}}}$


$R_1 + 3k$

$R_1 = 28.7 k\Omega$

f)

$\tau = 340 \mu s = (28.7 + 3) k C$


$\therefore C = 10.7 nF$

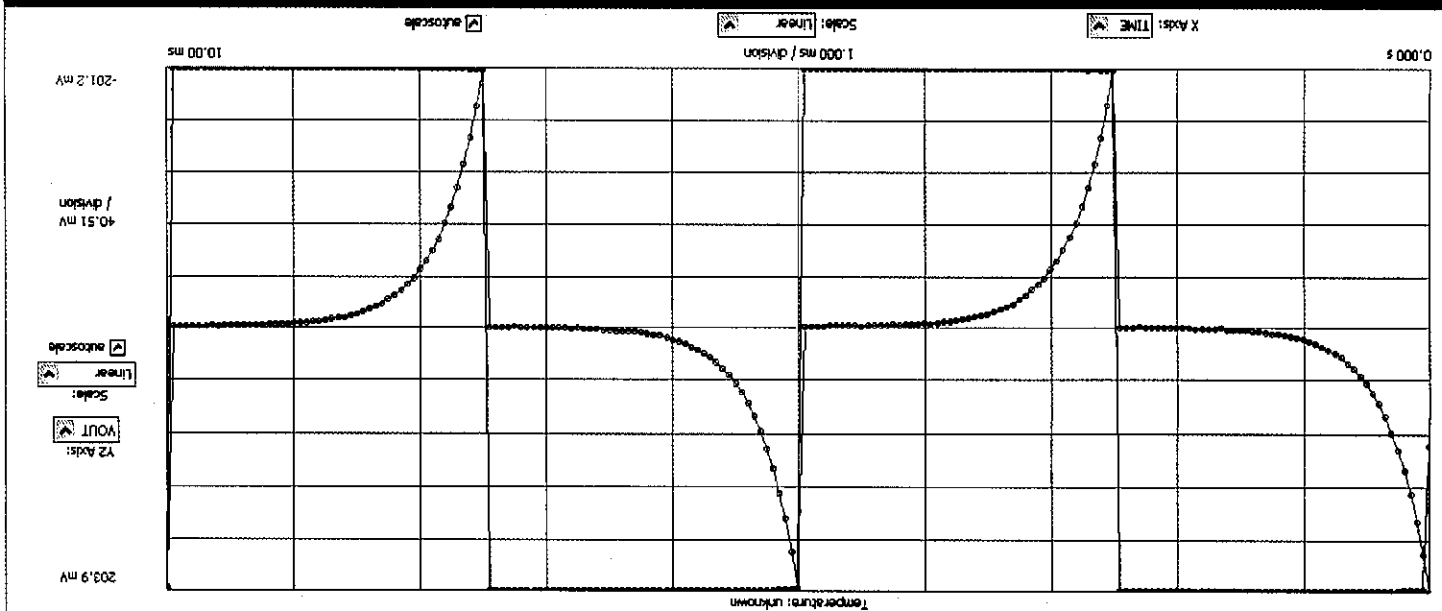

View Data

TIME	VIN	VOUT
0	429.861911067516e-3	203.920269122476e-3
50e-6	1.06933163912526	174.599873794812e-3
100e-6	1.069659395265079	149.7717631212229e-3
150e-6	1.06933163912526	127.85447114861e-3
200e-6	1.069659395265079	110.449563194468e-3
250e-6	1.07062089322839	94.9785341795734e-3
300e-6	1.07126552028096	81.7636971013801e-3
350e-6	1.07126552028096	69.8381125823728e-3
400e-6	1.070943320675459	60.1687198408115e-3
450e-6	1.070943320675459	52.4332057192167e-3
500e-6	1.0715878338075	45.3423178301394e-3
550e-6	1.07126552028096	39.2183692413987e-3
600e-6	1.0719101473342	33.4167373726925e-3
650e-6	1.07223246086108	29.2266637339346e-3
700e-6	1.0719101473342	25.0365937135614e-3
750e-6	1.0719101473342	22.135776017898e-3
800e-6	1.0719101473342	18.91264525523444e-3
850e-6	1.07255477438812	16.978766802831e-3

Close

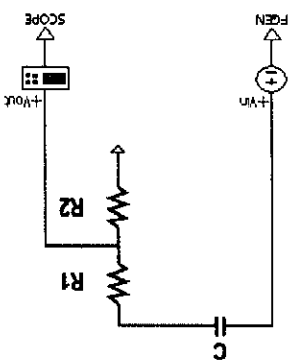




## Homework #6 – March 18, 2009


Due: April 1, 2009 at recitation

*No late homework accepted*

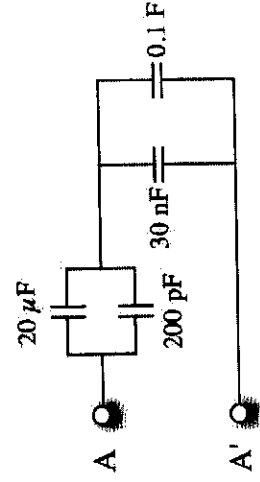1. [20 points] Find the equivalent capacitance of the following two networks, (a) and (b):



(a)

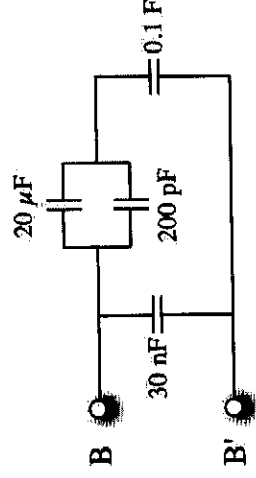

(b)

2. [20 points] Exercise 10.16, p572 of Agarwal and Lang. (Note ‘Exercise’ not ‘Problem’)
3. [20 points] Exercise 10.20, p572 of Agarwal and Lang.
4. [40 points] This problem studies the response of a series RC network, both theoretically and experimentally. The experiments will be performed using the ELVIS iLab. The circuit to be studied is shown below. It comprises a capacitor, two resistors and a voltage source all in series, Figure 4.1. The voltage  $v_{\text{out}}(t)$  across  $R_2$  can be measured and used to determine the current through the series network.

b) Derive an expression for  $i_c(t)$ , the current flowing through network.

c) Derive an expression for  $v_{out}(t)$ , the voltage across  $R_2$ .

Now consider an experimental study of the network. First, log in to the ELVIS iLab as in previous homeworks. After launching the iLab, you should see a network that is equivalent to the one shown above.

First, select the voltage source, or FGEN signal generator, and set its parameters to WaveForm = SQUARE, Frequency = 200 Hz, Amplitude = 1 V, and  $O_{set} = 0$  V. Second, select the SCOPE output measurement unit and program it with enough sampling rate that will allow you to see at least one full cycle of  $v_{out}(t)$  with enough resolution. Note that the system will only allow you to take a maximum of 201 data samples at the output. Third, run the experiment. Finally, select  $v_{in}(t)$  for the Y1 axis and  $v_{out}(t)$  for the Y2 axis, and use linear axes for both. When the figure resembles what you expect, capture a screen shot for subsequent analysis.

d) From the experimental data, extract the  $RC$  time constant of the network. You can see the actual numerical values of the data that you have obtained by looking into *View*

*Data* under the *Results* menu. You can also download the data to Excel using the *Results* menu

e) From the experimental data, extract the value of the resistor  $R_1$ . When you do this, note that even though you selected 1 V as the amplitude, the signal generator does not impose this voltage very accurately; the actual amplitude is measured as  $v_{in}$ .

f) From the experimental data, extract the value of  $C$ .