 


**Homework # 5 - March 11, 2009**

Due: March 18, 2009 at recitation

*No late homework accepted*

1. [20 Points]: For part (a) to (c), all MOSFETs have the same  $V_T = 2\text{V}$  and  $K = 0.1\text{mA/V}^2$ . The input voltages  $V_1$  and  $V_2$  represent logic values: 0 ( $V_1$  or  $V_2 < 1\text{V}$ ) and 1 ( $V_1$  or  $V_2 > 3\text{V}$ ). The power supply is  $V_{dd} = 5\text{V}$ .



(a) [4 Points] What should be the value of  $R_1$  so that the noise margin at node A is  $0.5\text{V}$ ?

Noise margin ( $NM_0$ ) is defined as the largest amount of noise that can be added to any valid output ( $V_O$ ) before it becomes invalid as the input ( $V_I$ ) for the next stage.

I.e.  $NM_0 = \text{Min}(|V_{IL} - V_{OL}|, |V_{OH} - V_{IH}|)$

(b) [4 Points] Assume now for simplicity that when “ON” these MOSFETs can be represented by a resistance  $R_{ON} = 5\text{k}\Omega$ . What should be the value of  $R_2$  so that the noise margin at node B is  $0.5\text{V}$ ?

(c) [4 Points] What logic function is implemented?

(d) [8 Points] Consider now that this gate is to be implemented with MOSFETs having  $0.5\text{V} < V_T < 3\text{V}$  and  $10^3\Omega < R_{ON} < 10^5\Omega$ , and pull-up resistors having  $10^3\Omega < R_{PU} < 10^5\Omega$ . (The inequalities express a permissible design space as opposed to a range of manufacturing uncertainty.) The MOSFETs and pull-up resistors need not have identical parameters.

Complete the design of the logic gate by choosing values of  $V_T$  and  $R_{ON}$  for each transistor, and  $R_{PU1}$  and  $R_{PU2}$  so that:  $V_{OL} = 0.5V$ ;  $V_{IL} = 1.5V$ ;  $V_{IH} = 2V$ ;  $V_{OH} = 3V$ ; and the power dissipated by the gate is minimized. If any parameter does not have a unique design value, then give the permissible range for that parameter. Assume  $V_{dd} = 5V$ .

2. [20 Points]: For all parts below, assume the input is a step signal:


$$v_i(t) = \begin{cases} 0 & t < 0 \\ V & t > 0 \end{cases}$$

In addition, assume the capacitor voltage at  $t=0$  is zero:


$$v_C(t=0) = 0.$$

Calculate the time constant(s); sketch and label carefully  $v_O(t)$ .


(a) [5 Points]

 


(b) [5 Points] Assume  $G < 1/R$ .

 

 (c) [5 Points] Assume the diodes are ideal.



 
(d) [5 Points] Assume the diodes are ideal, and  $V_1 = V_X$ ,  $V_2 = 2V_X$ . ( $V_2 < V$ )



3. [20 Points]: Agarwal and Lang, Problem 10.22 (Assume zero initial state,  $v_C(t=0) = 0$ )

4. [20 Points]: Agarwal and Lang, Problem 10.23

 5. [20 Points]: This problem makes use of the ELVIS iLab to study the small-signal characteristics of a common-source MOSFET-resistor amplifier. The amplifier is shown below. The transistor is the 2N7000 MOSFET that you have characterized in previous homework. Suitable parameters for this transistor are  $K = 0.14 \text{ A/V}^2$  and  $V_T = 1.9 \text{ V}$ . The resistor has a nominal value of  $500\Omega$ . Notice that in this amplifier, the top power supply is set to  $+2.5\text{V}$ , and the bottom power supply is set to  $-2.5\text{V}$ , both with respect to ground. This is to allow an optimum bias point at the output that is right around  $0 \text{ V}$  with respect to ground. In this problem, you will measure the transfer characteristics of the amplifier and the small-signal voltage gain, and compare the voltage gain to a prediction based on the models developed in class.



(A) [5 Points] The transfer characteristics of this amplifier can be obtained by sweeping the input voltage between  $-2.5\text{V}$  and  $2.5\text{V}$ . To do so, apply a sine wave at the input with a frequency of  $100\text{Hz}$ , an amplitude of  $2.5\text{V}$  and an offset of  $0\text{V}$ . At the output, appropriately configure the oscilloscope to see at least one full period of the output signal

with good resolution. To graph the transfer characteristics, graph  $v_{OUT}$  against  $v_{IN}$ . Print a screen shot of the canvas showing the transfer characteristics.

Using the Tracking feature in the bottom left corner of the client, read off the input bias voltage,  $V_{IN}$ , that results in an output bias voltage,  $V_{OUT}$ , that is close to 0 V. Give these values.

(B) [5 Points] Now, measure the small-signal gain at the bias point that you just determined. To do so, reduce the input amplitude to 100mV, and apply the offset found in Part (A) such that the output is biased close to 0V. When you do this, you will see that the instrument is not perfectly precise and that the input bias is a bit different from what you program. You will need to try different offset values until you get close enough. Once the output bias voltage is within about  $\pm 300\text{mV}$  of 0V, it is good enough. For this case, plot the waveforms of the input voltage and the output voltage versus time. Print a screen shot of this plot. Measure the amplitudes of both signals and determine the voltage gain.

(C) [5 Points] Next, obtain the input and output waveforms and extract the gain for other bias points. Bias the input 0.6V below (more negative than) the bias point you selected for Part (B). Plot the input and output waveforms, print a screen shot of this plot, measure the amplitudes of both signals, and extract the voltage gain. Do the same for an input bias 0.3V above (more positive than) the bias point you selected for Part (B). Plot and measure the same parameters. Comment on the change in voltage gain and the distortion that you observe in the output waveforms. Explain its origin in both cases.

(D) [5 Points] Finally, use an appropriate small-signal model to calculate the voltage gain of this amplifier for an input bias such that the biased output voltage is equal to 0V. Use the parameters for the transistor given above. Compare what you obtain against the measurement results obtained in Part (B) above. Comment appropriately.

*As always, start this problem early to avoid any last minute crunch on the system.*